
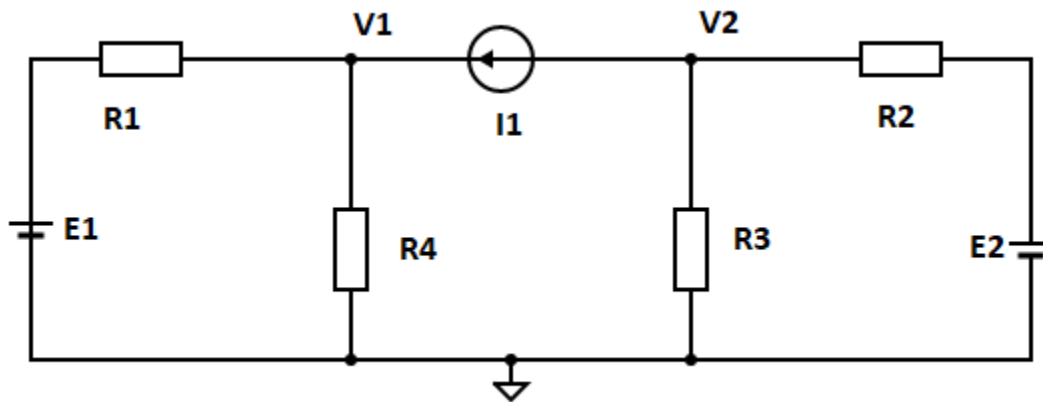


EE 1100 Basic Electrical Engineering
March – June 2023
Tutorial 2

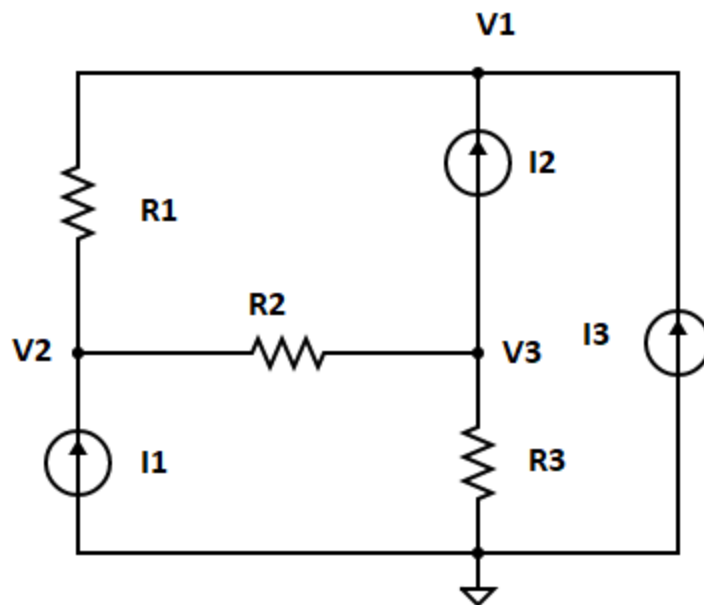
1. Find the expressions for voltages **V1** and **V2** using nodal analysis.




2. Find the expressions for voltages **V1**, **V2** and **V3** using nodal analysis.



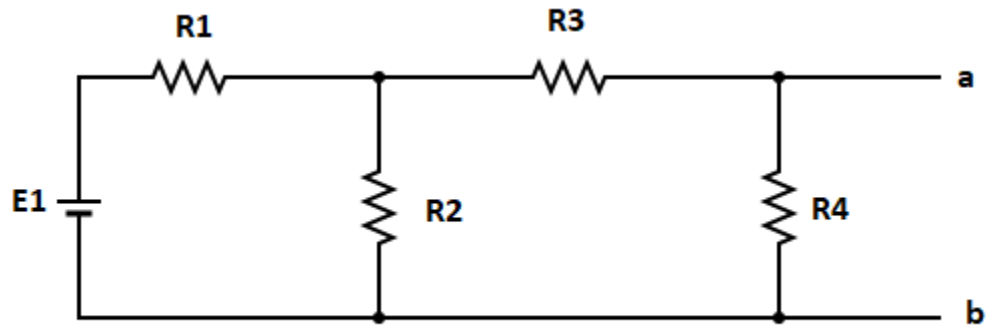3. Find Thevenin equivalent voltage and resistance across **a** and **b**, if $E1 = 20\text{ V}$, $R1 = 5\ \Omega$, $R2 = 4\ \Omega$, $R3 = 8\ \Omega$ and $R4 = 6\ \Omega$.



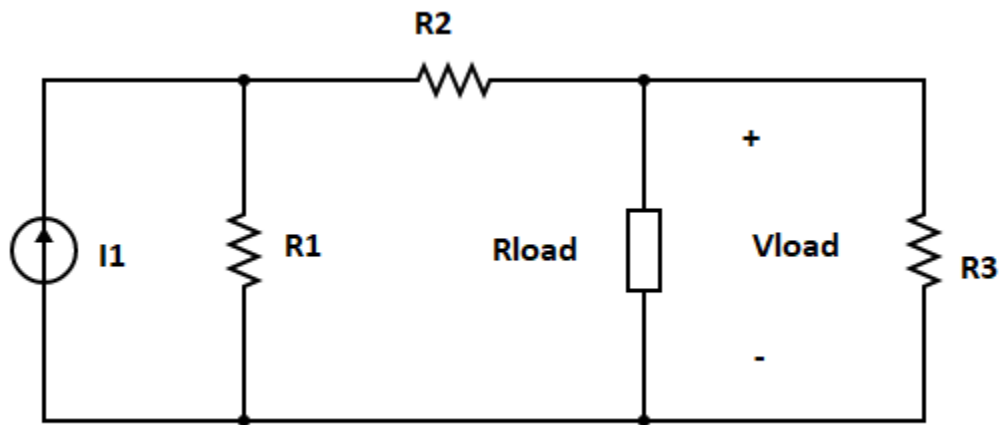4. Find voltage **Vload** by forming an equivalent Norton circuit across resistance **Rload**, given that $I1 = 5\text{ A}$, $R1 = 3\ \Omega$, $R2 = 7\ \Omega$ and $R3 = 2\ \Omega$.



5. In the following circuit,

- a. Calculate the value of R_{load} in terms of R_1 , R_2 and R_3 which will ensure that the maximum power gets transferred to the R_{load}
- b. Find the maximum power transferred to R_{load} , if $E_1 = 10\text{ V}$, $E_2 = 5\text{ V}$, $R_1 = 2\ \Omega$, $R_2 = 4\ \Omega$ and $R_3 = 10\ \Omega$.

