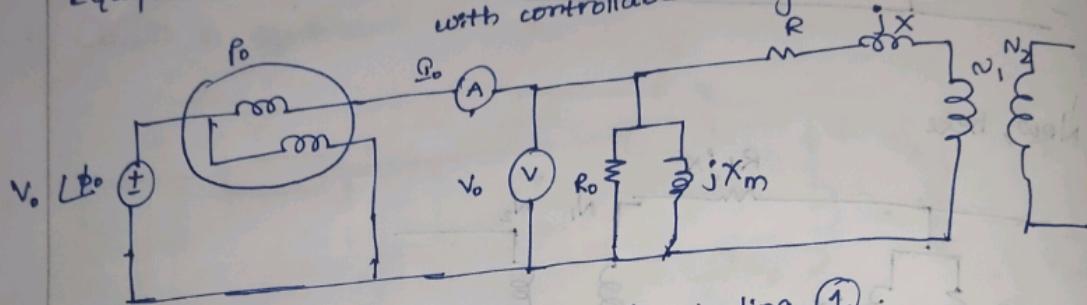


100

Open circuit test ::

Transformer is given.

Equipment required: Ammeter, Voltmeter, Wattmeter, Voltmeter, with controllable voltage.



V_o is equal to rated voltage of winding ①.

$$\text{and } P_o = V_o \left(\frac{V_o}{R_o} \right) = \frac{V_o^2}{R_o} \Rightarrow R_o = \frac{P_o}{V_o^2} \quad \text{and } R_o = \frac{V_o^2}{P_o}$$

$$I_o = \frac{V_o \sqrt{R_o^2 + X_m^2}}{R_o X_m}$$

$$\text{and } \Rightarrow \frac{V_o}{X_m} = \frac{R_o I_o}{\sqrt{R_o^2 + X_m^2}}$$


$$\Omega_o^2 = \frac{V_o^2 (R_o^2 + X_m^2)}{R_o^2 X_m^2}$$

$$\Omega_o^2 = V_o^2 \left(\frac{1}{X_m^2} + \frac{1}{R_o^2} \right)$$

$$\frac{V_o}{X_m} = \sqrt{\Omega_o^2 - \left(\frac{V_o}{R_o} \right)^2}$$


$$\Rightarrow X_m = \frac{V_o}{\sqrt{I_o^2 - \left(\frac{V_o}{R_o} \right)^2}}$$

Q1 Short circuit test:

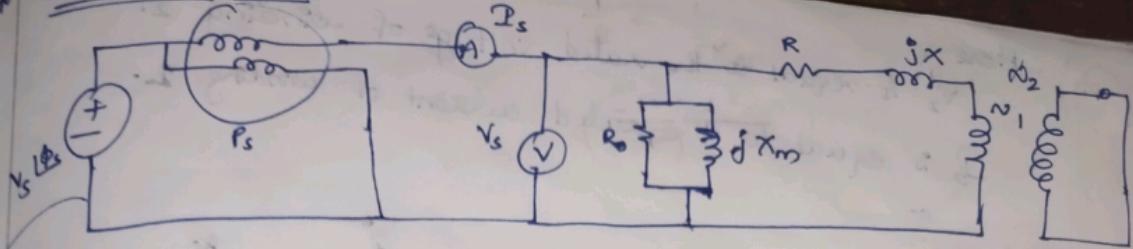

Q2 is equal to rated current of winding ①.


I_s approximated by

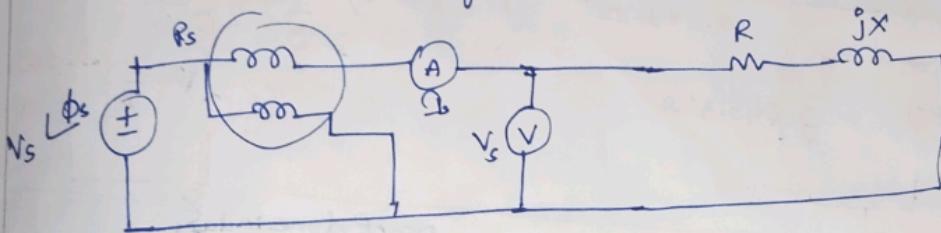

$$P_s = I_s^2 R \Rightarrow R = \frac{P_s}{I_s^2}$$

$$\frac{V_s}{P_s} = \sqrt{R^2 + X^2} \Rightarrow X = \sqrt{\left(\frac{V_s}{I_s}\right)^2 - R^2}$$

*Load:- Equipment that consumes power.

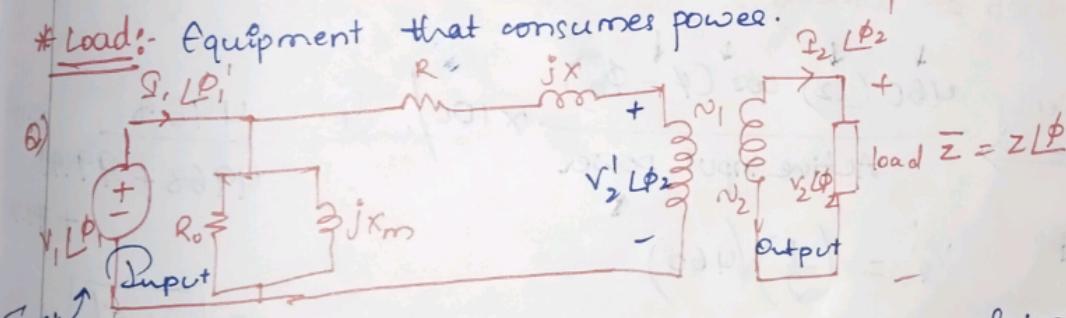

for this we can also measure the performance of transformer,
this called voltage regulation.

$$\text{Here } V_2' = \frac{N_1}{N_2} V_2$$

For a given power factor of the load, voltage regulation
 $= \frac{V_1 - V_2'}{V_2'} \times 100\%$


Here

V_2 is equal to the rated voltage of winding 2.

I_2 is equal to the rated current of winding 2.

* Efficiency:
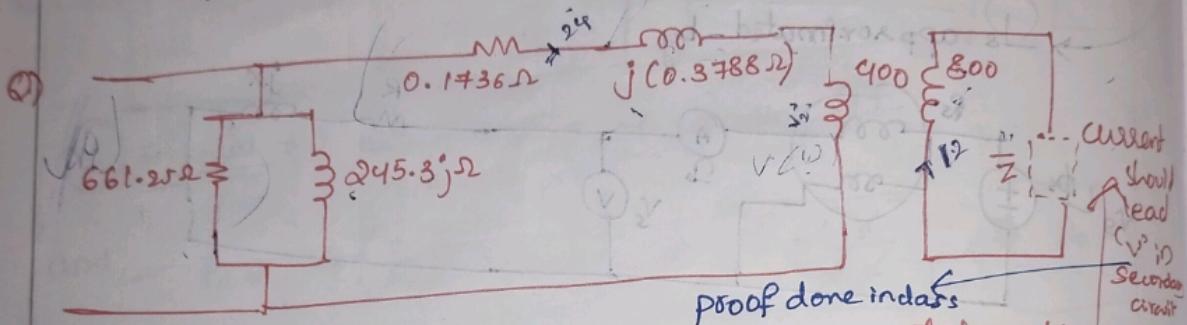
$$\frac{\text{Output active power}}{\text{Input active power}} \times 100\%.$$



for transformer with this equivalent circuit, rated voltage of winding '2' is 460V and rated current of winding '2' is 12A. Find pf of the load at which voltage regulation. At this pf, what is the efficiency with rated Voltage at terminals of winding '2' and rated current through the load

$$\text{efficiency} \Rightarrow \frac{460(12) \cos(\phi - \phi_2)}{\text{Active input power}} \times 100\%. \text{ So } \frac{4968}{4968 + 99.99} \times 100\% + 79.6\%$$

$$\text{and } V_2' = \left(\frac{1}{2}\right)(460)$$


$$V_2' = 230V$$

$$= 96.5\%$$

$$\text{So as regulation} = 0 \Rightarrow V_1 = 230V$$

$$\text{and hence Active input power} = V_1 I_1 \cos(\phi_1 - \phi_1')$$

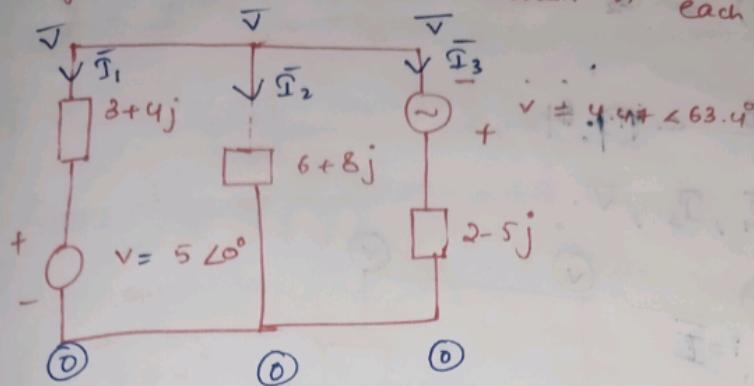(103) Using Kirchoff law, calculate current in each branch,



Sol:

$$(\bar{V} - 5\angle 0^\circ) = \bar{I}_1 (5) \angle 53^\circ$$

$$\bar{V} = \bar{I}_2 (10) \angle 53^\circ$$

$$\bar{V} + 4.47 \angle 63.4^\circ = \bar{I}_3 (2-5j)$$

$$\text{and } \bar{I}_1 + \bar{I}_2 + \bar{I}_3 = 0$$

$$\left(\frac{\bar{V} - 5}{5} e^{-i(53^\circ)} \right) + \left(\frac{\bar{V}}{10} e^{-i(53^\circ)} \right) + \left(\frac{\bar{V} + 4.47 \angle 63.4^\circ}{2-5j} \right) = 0$$

$$\left(\frac{\bar{V}}{5} - 1 \left(e^{-i(53^\circ)} \right) \right) + \left(\frac{\bar{V}}{10} \left(e^{-i(53^\circ)} \right) \right) + \frac{\bar{V}}{2-5j} + \frac{4.47 \angle 63.4^\circ}{2-5j} = 0$$

$$\frac{\bar{V}}{5} - 1 \angle -53^\circ + \frac{\bar{V}}{10} (1 \angle -53^\circ) + \frac{\bar{V}}{2-5j} \rightarrow 0.33 \angle 19.48^\circ = 0$$

$$(\rightarrow 0.33 \angle 19.48^\circ) + \frac{\bar{V}}{1} \left(\frac{1}{5} + \cancel{1 \angle 53^\circ} + \cancel{\frac{1}{2-5j}} \right) = 0$$

$$(0.2 \angle 0^\circ + 0.91 \angle 43.0^\circ) = 0$$


$$1.07 \angle -35.72^\circ$$

$$\bar{V} = +\frac{4.6}{1.07} \angle 69.84^\circ$$

(104)

$$\frac{V}{10} (\angle -53^\circ) = \bar{I}_2$$

$$\bar{I}_2 = \frac{+6.6}{10.7} \angle 17.84^\circ$$

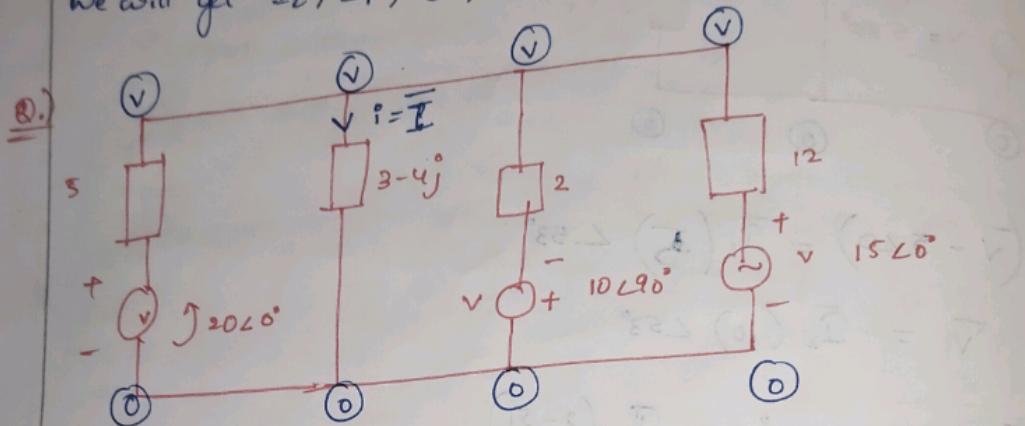we will get $\bar{I}_2, \bar{I}_1, \bar{I}_3, \bar{V}$.Sol.

$$\frac{\bar{V}}{3-4j} + \frac{\bar{V}-20}{5} + \frac{\bar{V}+10\angle 90^\circ}{2} + \frac{\bar{V}-15\angle 0^\circ}{12} = 0$$

$$\frac{\bar{V}}{5} (1 \angle +53^\circ) + \frac{\bar{V}}{5} - 4 + \left(\frac{\bar{V}}{2} \right) + (5j) + \left(\frac{\bar{V}}{12} \right) - \frac{5}{4} = 0$$

$$\frac{\bar{V}}{5} (1 \angle +53^\circ + 1 + \frac{30}{12} + \frac{15}{12}) + 5j - \frac{21}{4} = 0$$

$$\frac{\bar{V}}{5} (1 \angle +53^\circ + \frac{47}{12}) + 5j - \frac{21}{4} = 0$$

$$\bar{V} \left(1 \angle +53^\circ + \frac{4.58 \angle +20.90}{12} \right) = \frac{21}{4} - 5j$$

$$\boxed{\bar{V} = 8.02 \angle -33.7^\circ}$$

$$\frac{7.25}{2.32} \angle -63.67^\circ$$

So

$$\boxed{\bar{I} = \frac{8.02}{5} \angle -53.6^\circ = \bar{I}}$$

$$\boxed{\bar{I} = 1.604 \angle -53.6^\circ}$$

(105)
Q.

$$100\angle 0^\circ \text{ A}$$

Sol: (100)


So

hence

108

17-05-23

* Three phase AC-circuits:

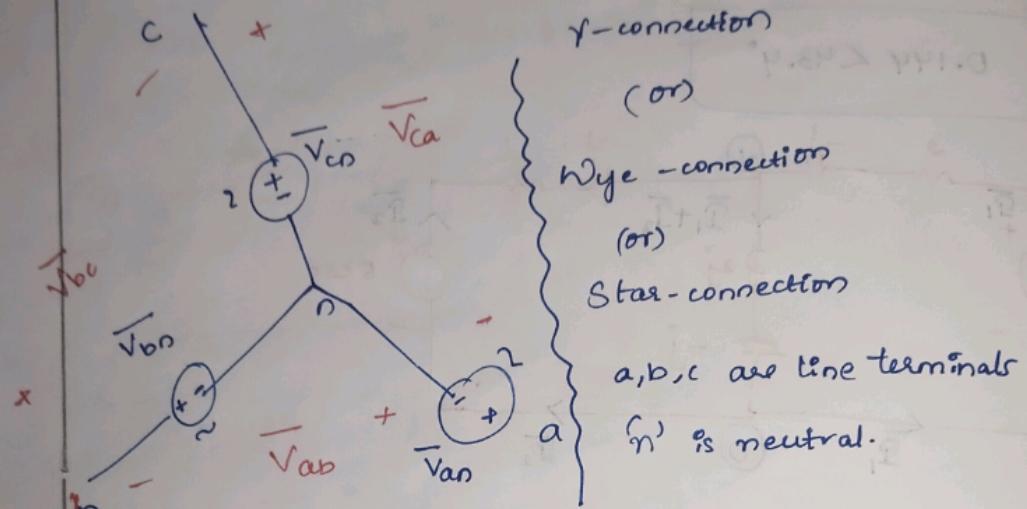

- ⇒ Voltage source with voltage \bar{V}_{an} is said to be in phase '(a)' or belong to phase '(a)'. Similarly for \bar{V}_{bn} for '(b)' and \bar{V}_{cn} for '(c)'.
- ⇒ \bar{V}_{an} , \bar{V}_{bn} , \bar{V}_{cn} are phase voltages.
- ⇒ \bar{V}_{ab} , \bar{V}_{bc} , \bar{V}_{ca} are called line-to-line voltages / line voltages.

let,

$$\bar{V}_{an} = V_p \angle 0^\circ, \quad \bar{V}_{bn} = V_p \angle -120^\circ, \quad \bar{V}_{cn} = V_p \angle 120^\circ$$

P : phase,


If three voltages are having same RMS value and if the modulus of phase difference b/w any two of these three voltages is 120° , then the three voltages are said to be balanced.

Now

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ = \sqrt{3} V_p \angle 30^\circ$$

$$109 \quad \bar{V}_{bc} = \bar{V}_{bn} - \bar{V}_{cn}$$

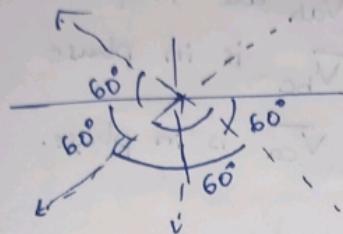
$$= V_p \angle -120^\circ - V_p \angle 120^\circ = \sqrt{3} V_p \angle -90^\circ$$




$$\bar{V}_{ca} = \bar{V}_{cn} - \bar{V}_{an}$$

$$= V_p \angle 120^\circ - V_p \angle 0^\circ$$

$$= \sqrt{3} V_p \angle +150^\circ$$

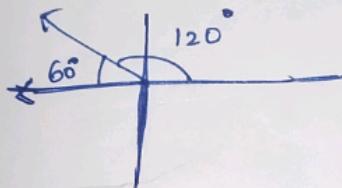

So

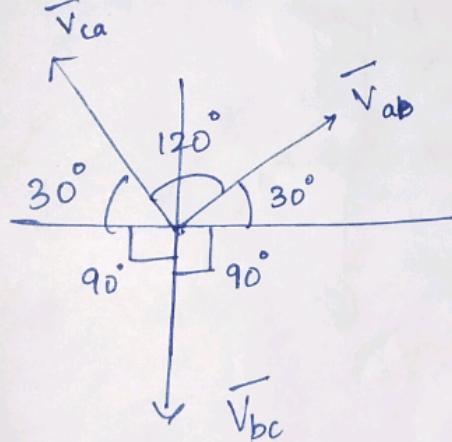

$$\text{let } V_l = \sqrt{3} V_p$$


$$\text{So } \bar{V}_{ab} = V_L \angle 30^\circ$$

$$\bar{V}_{bc} = V_L \angle -90^\circ$$

$$\bar{V}_{ca} = V_L \angle 150^\circ$$

(iv)

Delta Connection (Δ -connection)

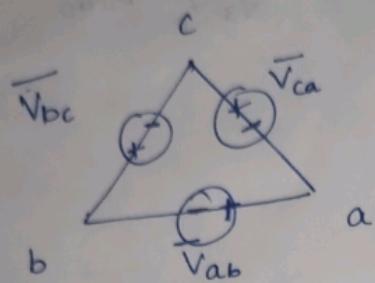

\bar{V}_{ab} is in phase

\bar{V}_{bc} is in phase

\bar{V}_{ca} is in phase.


$\Rightarrow a, b, c$ are the line terminals

$\Rightarrow \bar{V}_{ab}, \bar{V}_{bc}, \bar{V}_{ca}$ are phase voltages. We can also call them as line voltages.

continued from pg. 117.

Some imp questions:

(i)

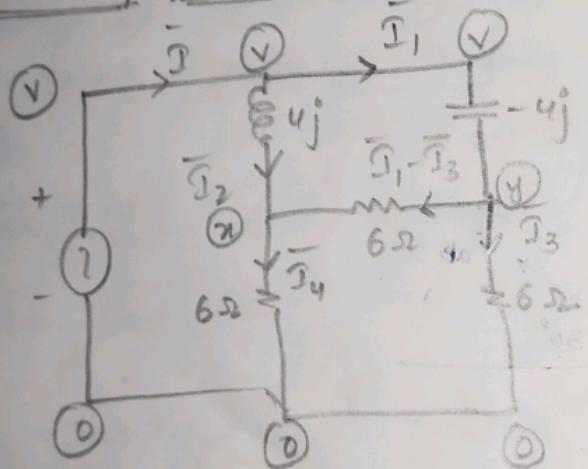

$$\bar{v} - \bar{z} = \bar{I}_2 (4j)$$

$$\text{and } \frac{\bar{v} - \bar{v}}{4j} + \frac{\bar{z} - \bar{y}}{6} + \frac{\bar{z}}{6} = 0$$

$$\frac{\bar{y} - \bar{v}}{-4j} + \frac{\bar{y} - \bar{z}}{6} + \frac{\bar{y}}{6} = 0$$

So add
 $\frac{\bar{x} + \bar{y}}{6}$

$\frac{\bar{x} + \bar{y}}{6}$

$\frac{\bar{x} + \bar{y}}{6}$

So
begin
let


so

\Rightarrow

\Rightarrow

so

\Rightarrow

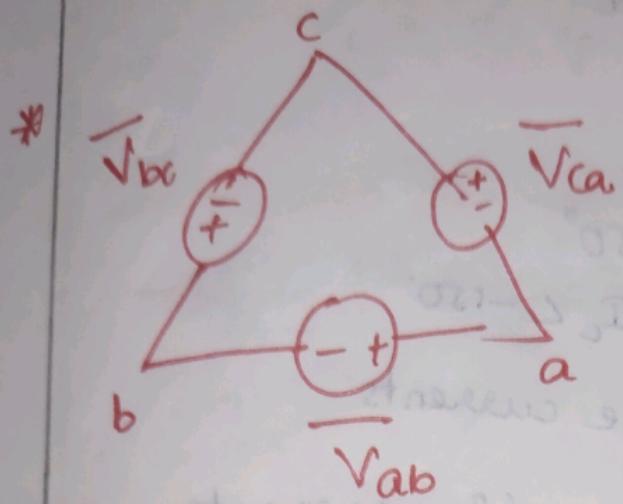

let $\bar{V}_{ab} = V_p \angle 0^\circ$

$$\bar{V}_{bc} = V_p \angle -120^\circ$$

$$\bar{V}_{ca} = V_p \angle 120^\circ$$

3 phase voltage source.


line voltage = phase voltage

V_p : RMS value of phase voltage

V_L : RMS value of line voltage.


*

Comparison:-

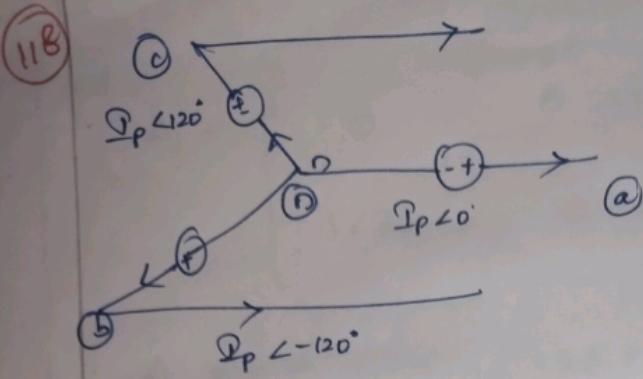

3 phase voltage source

phase
(currents)

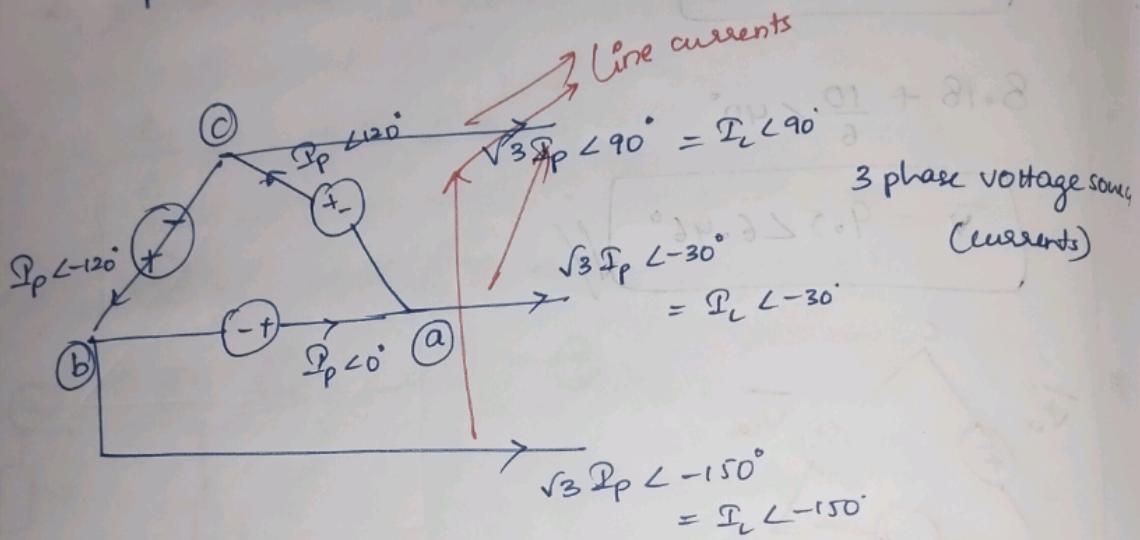

3 phase voltage source

(currents)

$\Rightarrow I_p < 0^\circ, I_p < -120^\circ, I_p < 120^\circ$ are phase currents.

$\Rightarrow \sqrt{3} I_p < 90^\circ, \sqrt{3} I_p < -30^\circ, \sqrt{3} I_p < -150^\circ$ are line currents.

\Rightarrow Line current RMS value = $\sqrt{3}$ (phase current RMS value)

$$I_L = \sqrt{3} I_p$$

Wye

$$V_L = \sqrt{3} V_p$$

$$I_L = I_p$$

where,

V_L = RMS value of line voltage

V_p = RMS value of phase voltage

I_L = RMS value of line current


I_p = RMS value of phase current

Delta

$$V_L = V_p$$

$$I_L = \sqrt{3} I_p$$


Impedances in star / or wye connection:-

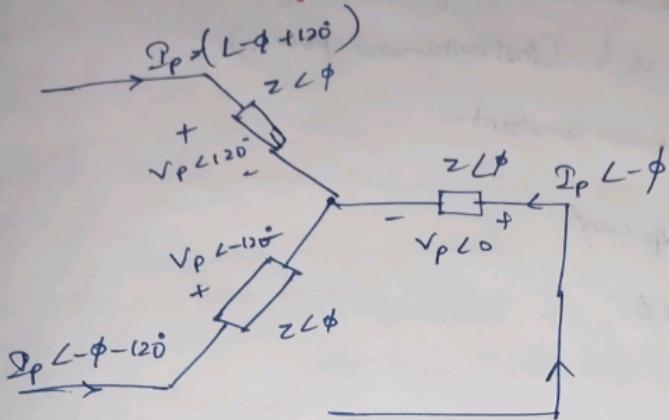

$$\text{Here } \underline{I}_L = \underline{I}_P$$

$$\sqrt{I} = \sqrt{3} V_p$$


Impedances in delta connection:-

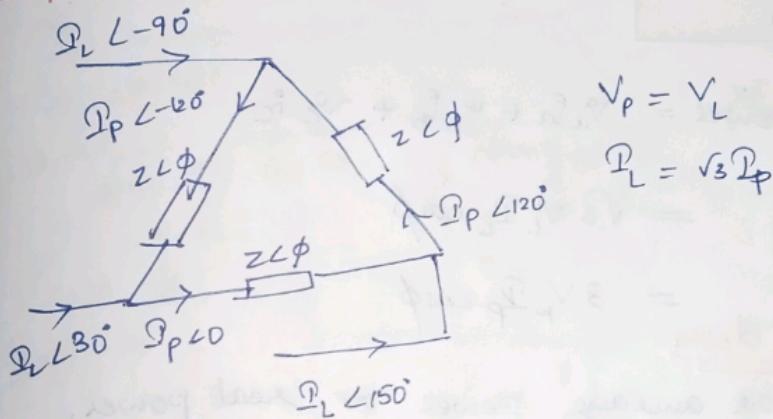

$$V_p = V_L$$

$$\underline{I}_L = \sqrt{3} \underline{I}_P$$

Instantaneous voltages:-

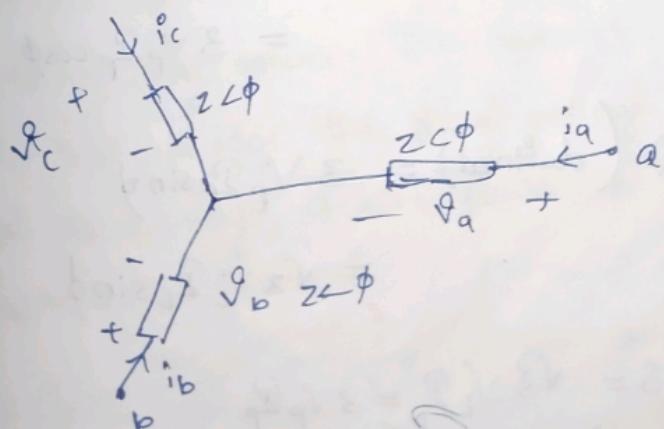

$$V_a = \sqrt{2} V_p \sin(\omega t)$$

$$V_b = \sqrt{2} V_p \sin(\omega t - 120^\circ)$$

$$V_c = \sqrt{2} V_p \sin(\omega t + 120^\circ)$$

$$i_a = \sqrt{2} I_p \sin(\omega t - \phi)$$

$$i_b = \sqrt{2} I_p \sin(\omega t - \phi - 120^\circ)$$

$$i_c = \sqrt{2} I_p \sin(\omega t - \phi + 120^\circ)$$

120) Instantaneous power consumed by the wye-connected impedances,


$$P = \sqrt{3} V_p I_p \cos \phi \quad (\text{instantaneous power})$$

$$= 3 V_p I_p \cos \phi \leftarrow \text{constant.}$$

$$= \sqrt{3} (\sqrt{3} V_p) I_p \cos \phi$$

$$= \sqrt{3} V_L I_L \cos \phi$$

Now,

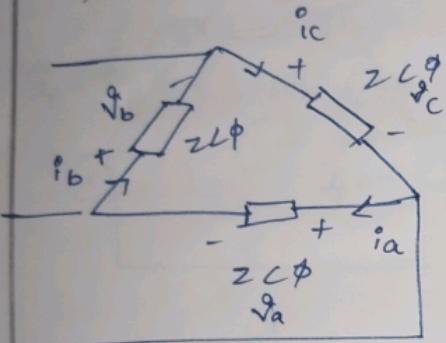

$$\text{Instantaneous power} = \sqrt{3} V_a i_a + \sqrt{3} V_b i_b + \sqrt{3} V_c i_c$$

$$= \sqrt{3} V_L I_L \cos \phi$$

$$= 3 V_p I_p \cos \phi$$

* For both wye & delta.

Active power or average power or real power,

$$P = P = \sqrt{3} V_L I_L \cos \phi$$

$$= 3 V_p I_p \cos \phi$$

$$\text{Reactive power, } Q \text{ (defined)} = 3 V_p I_p \sin \phi$$

$$= \sqrt{3} V_L I_L \sin \phi$$

$$\text{Apparent power, } S = \sqrt{3} V_L I_L = 3 V_p I_p$$

Solve

Complex

Now,

for,

$\sqrt{3} V_p$

$\sqrt{3} I_p$

$\sqrt{3} \phi$

$\sqrt{3} \omega$

$\sqrt{3} L$

$\sqrt{3} C$

$\sqrt{3} R$

$\sqrt{3} \phi_1$

$\sqrt{3} \omega$

so,

now

$\sqrt{3} L$

$\sqrt{3} C$

$\sqrt{3} R$

$\sqrt{3} \phi_2$

$\sqrt{3} \omega$

$\sqrt{3} L$

$\sqrt{3} C$

$\sqrt{3} R$

$\sqrt{3} \phi_3$

$\sqrt{3} \omega$

$\sqrt{3} L$

$\sqrt{3} C$

$\sqrt{3} R$

$\sqrt{3} \phi_4$

$\sqrt{3} \omega$

$\sqrt{3} L$

$\sqrt{3} C$

$\sqrt{3} R$



$\sqrt{3} \phi_5$

$\sqrt{3} \omega$


Complex power, $\bar{S} = P + jQ$

Now,

For,

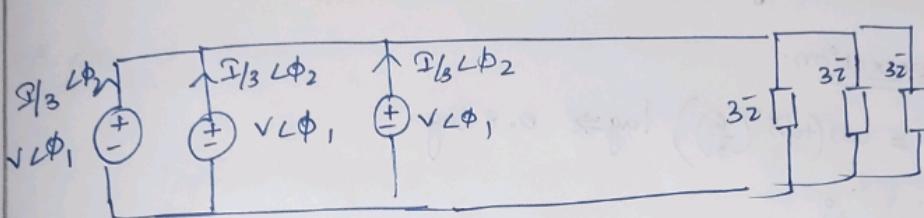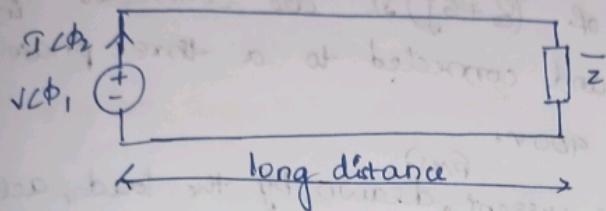

So,

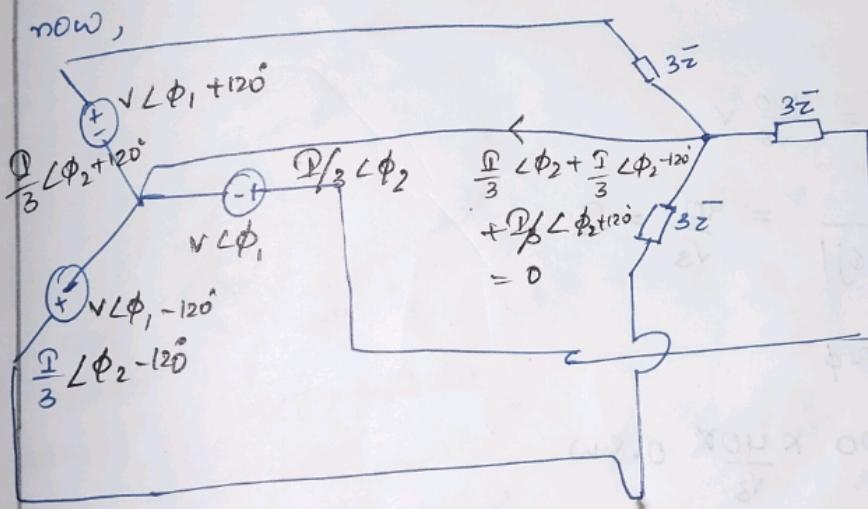

- Q) A star connected load is supplied from a 400V three phase voltage source. The current in each phase of load is 30A & lags the phase voltage by 30°. find RMS value of phase voltage, $\frac{I_{load}}{\text{Active power}}$ & reactive power consumed by load.

Solt $V_P = \frac{400}{\sqrt{3}} = 230.9$, Active power consumed by load $\Rightarrow 18000W = 3 \left(\frac{200}{\sqrt{3}} \right) (30) \left(\frac{\sqrt{3}}{2} \right)$

122) reactive power = $6\sqrt{3} \text{ kvar}$


$$= 6\sqrt{3} \times 10^3 \sqrt{\text{Ae}}$$

Q) Three identical impedances of $(8+6j)\Omega$ are connected in wye and then in delta and connected to a three phase voltage source of voltage 400V .

In each case find the line current drawn by the load, active power consumed by the load and pf.

Wye connection:
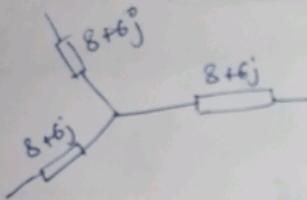
$$\text{pf} = \cos(\tan^{-1}\left(\frac{6}{8}\right)) \text{ lag} \Rightarrow 0.8 \text{ lag}$$



$$V_p = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} \text{ V}$$


$$I_p = \frac{V_p}{|8+6j|} = \frac{40}{\sqrt{3}} = I_L$$

$$P = \sqrt{3} V_p I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times \frac{40}{\sqrt{3}} \times 0.8 \text{ W}$$

$$= 12.80 \text{ kW}$$

Delta connection

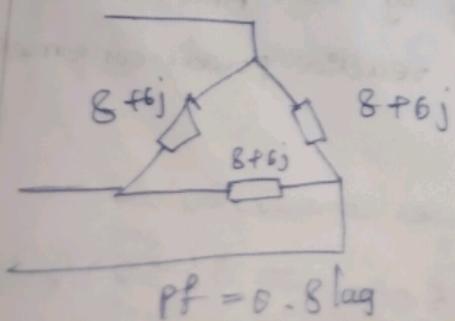

$$V_L = 400 = V_p$$

$$I_p = \frac{V_p}{|8+6j|} = 40$$

$$I_L = \sqrt{3} I_p = 40\sqrt{3}$$

(193)

$$\begin{aligned}
 P &= \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 40 \sqrt{3} \times 0.8 \\
 &= 3(12.80 \text{ kW}) \\
 &= 38.40 \text{ kW}
 \end{aligned}$$

* Three phase induction motor:

Rotating machine

stationary part — stator
Rotatory part — Rotor

Principle of operation:-


Cylindrical shape,

① Magnetic core.


$(\omega_1 - \phi) \text{ rad} / \text{s}$ $(\omega_1 + \phi) \text{ rad} / \text{s}$

② Conductors

③ Insulation

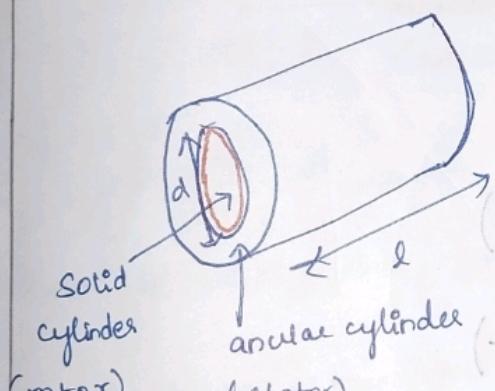


(Both are magnetic cores)

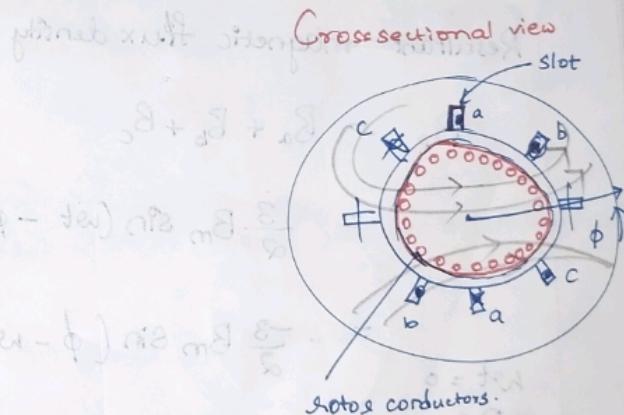

Coils, a, b, c form a
three phase winding

— stator winding

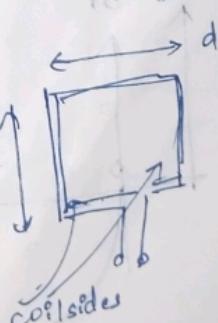

124

The stator winding is connected across a three phase voltage source.

Let the currents in the three coils be i_a, i_b, i_c . Let

$i_a = \sqrt{2} I \sin(\omega t)$ where ω is angular frequency of voltage source.

$$i_b = \sqrt{2} I \sin(\omega t - 120^\circ)$$

$$i_c = \sqrt{2} I \sin(\omega t + 120^\circ)$$

Flux density due to i_a , at any point on the inner surface of stator or outer surface of rotor, at an angle ϕ in the radial outward direction

$$B_a = B_m \sin(\omega t) \cos \phi$$

$$B_b = B_m \sin(\omega t - 120^\circ) \cos(\phi - 120^\circ)$$



$$B_c = B_m \sin(\omega t + 120^\circ) \cos(\phi + 120^\circ)$$

Resultant magnetic flux density

$$B_R = B_a + B_b + B_c$$


$$= \frac{3}{2} B_m \sin(\omega t - \phi)$$

$$= -\frac{3}{2} B_m \sin(\phi - \omega t)$$

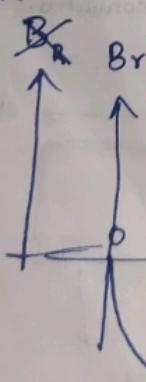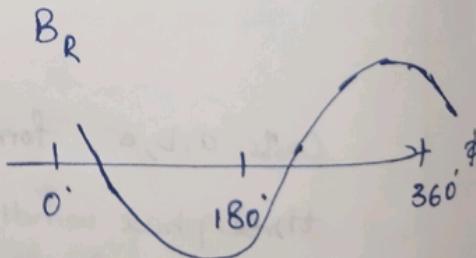 $\omega t = 0$  $\omega t = 20^\circ$ 

and after some more time,



$$\omega_t = 40^\circ$$

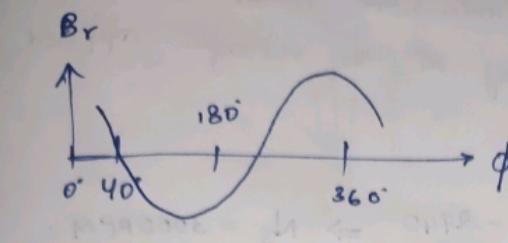

Rotating speed $\rightarrow \omega$ rad/s
 rotating magnetic field.

Initially rotor is at rest. Faraday's law, emf induced in the rotor conductors. Rotor current flows. Rotor conductors will carry current are placed in a magnetic field \Rightarrow they experience a force/torque. Rotor rotates in the dirⁿ of rotating magnetic field.

Fleming's left-hand rule

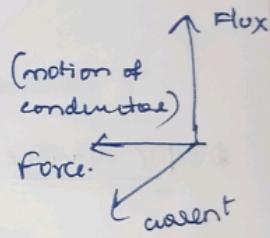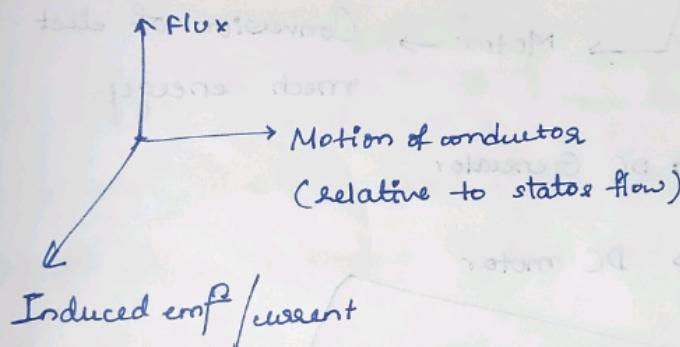

\Rightarrow Rotor at steady state rotates at a speed which is less than ω .

ω_r = speed of rotor in rad/s, $\omega_r < \omega$.

$$\text{Slip, } s = \frac{\omega - \omega_r}{\omega} = \frac{N_s - N_r}{N_s}$$

rpm :- revolutions per minute.

$$N_s = \frac{30}{\pi} \omega$$

$$N_r = \frac{30}{\pi} \omega_r$$

Speed of rotating magnetic field in RPM,

(Name given)

N_s : synchronous speed.

N_r : speed of rotor in RPM.

(126)

The speed of the rotor of an induction motor is 2940RPM, & the slip is 2%. Find the frequency of the voltage applied to the stator winding.

$$S = \frac{N_s - N_r}{N_s} \Rightarrow 0.02 = \frac{N_s - 2940}{N_s} \Rightarrow N_s = 3000 \text{ RPM}$$

$$\omega = \frac{N_s \pi}{30}, \text{ frequency of voltage applied to stator}$$

$$\text{winding} = \frac{\omega}{2\pi} = 50 \text{ Hz}$$

* Motor \rightarrow Rotating machine,


* Rotating machine $\xrightarrow{\text{Generator}}$ Conversion of mechanical to electrical energy.

$\xrightarrow{\text{Motor}}$ Conversion of elect to mech energy

* DC Machine:-

$\xrightarrow{\text{DC Generator}}$ (coil rotate or outside)


$\xrightarrow{\text{DC motor}}$

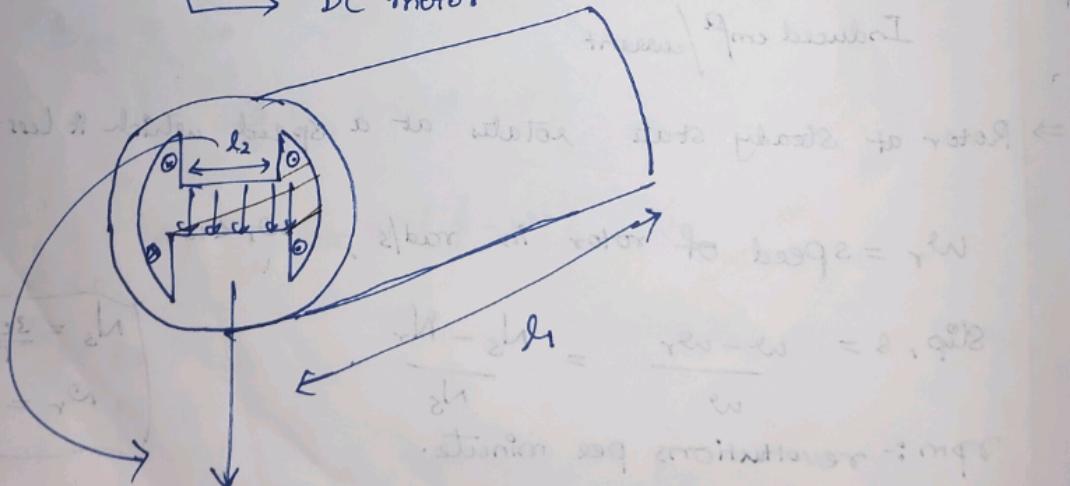


Electromagnets

Cross section:-

(plane \perp° to axis of cylinder)

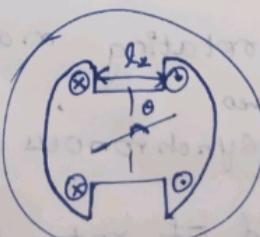

DC Generator:

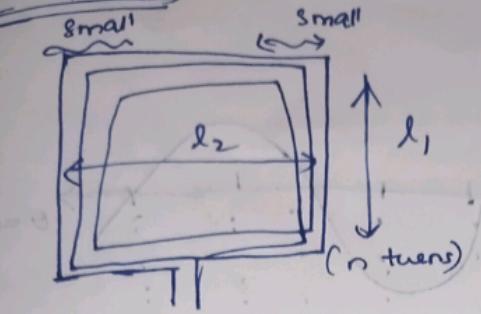


Flux linkage of coil = Number of turns \times Flux linking the coil.

Coil is placed between the two poles of electromagnet.

Cross-section:

(plane parallel to axis of cylinder)

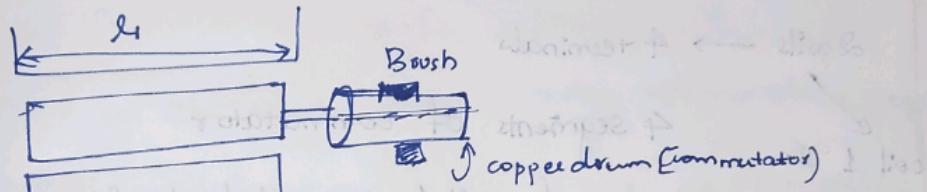

Coil is rotated at a speed ω (in rad/s). Let ϕ be the magnetic flux produced by the electromagnet.

θ : Angle made by coil w.r.t direction of flux.

flux linking the coil = $\phi \sin\theta$

$$\text{EMF induced in the coil} = n \frac{d}{dt} (\phi \sin\theta)$$

$$= n\phi \cos\theta \frac{d\theta}{dt}$$

$$= n\phi \cos\theta \omega$$


$\theta = \omega t$ (ω is kept const as we are only rotating)

$$V_e = \boxed{\text{EMF} = n\phi \omega \cos(\omega t)}$$

128


Rotating-coil, commutator

Stationary - Brushes.

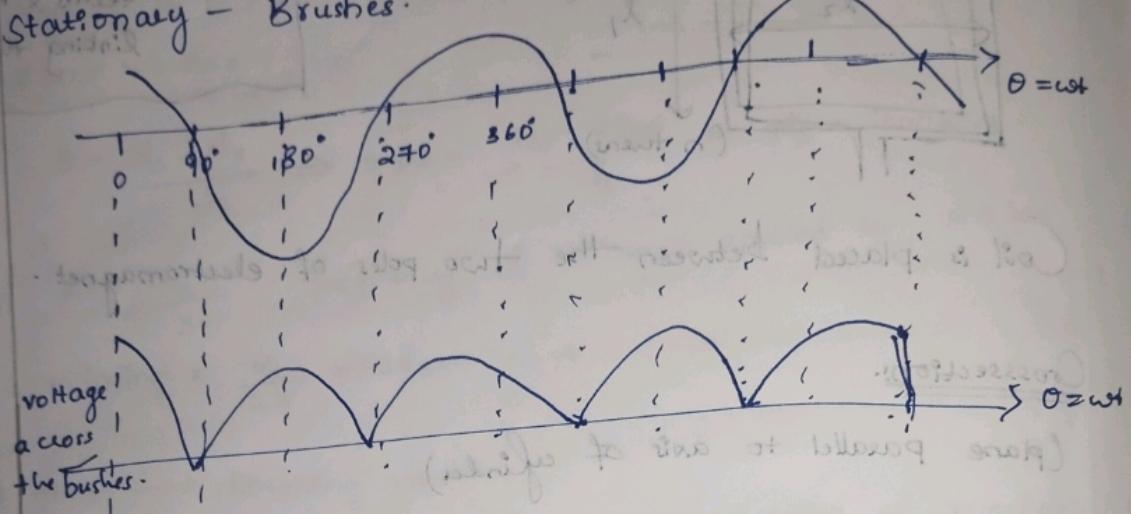2 coils \rightarrow 4 terminals


coil 1 & coil 2 → 4 segments of commutator

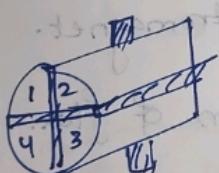coil 1 connected to segments 1 & 3
coil 2 connected to segments 2 & 4.



EMF in coil 1
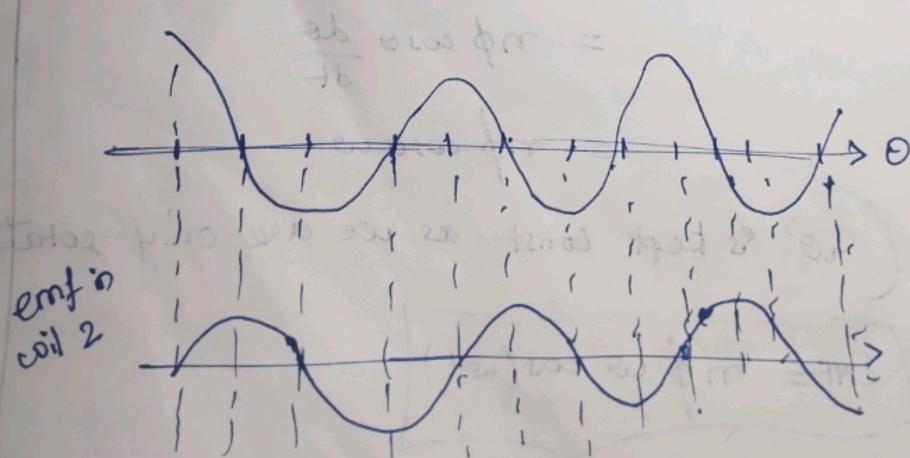
$$(emf_1)_{ab} = \text{line volt across } AB$$



voltage across brushes.

 \Rightarrow In p

So th

 \Rightarrow The l \Rightarrow Bru \Rightarrow Vol \Rightarrow

g


v

g


R

e

(129) DC Generators:

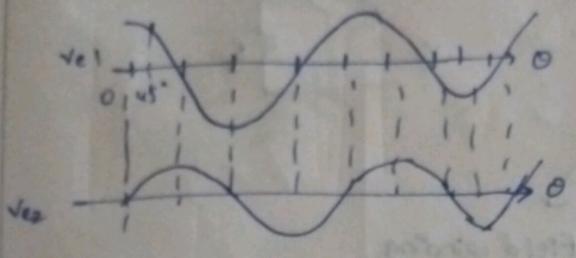

Voltage across brushes
with one coil

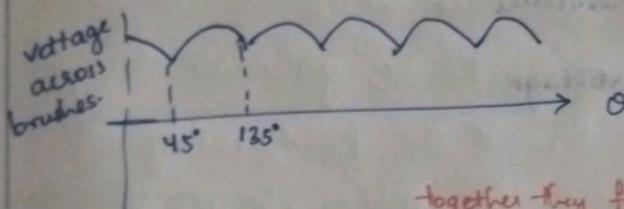

together they form "armature winding".

\Rightarrow In practice there are many coils & many commutator segments,


so that the voltage across the brushes is DC (constant).

\Rightarrow The load is connected across the brushes.

\Rightarrow Brushes are terminals of armature winding.

\Rightarrow Voltage across brushes is called EMF induced in armature winding.

\Rightarrow

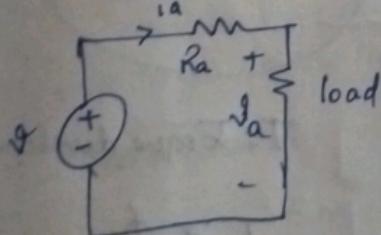

Subscript 'a' for armature.

v : EMF induced in armature winding.


v_a : armature terminal voltage.

R_a : armature resistance.


i_a : armature current.

$$v_a = v - i_a R_a$$


130

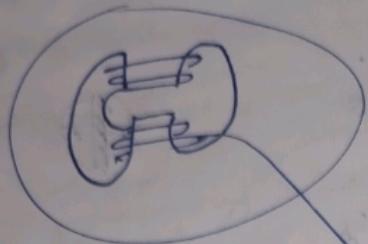

Field winding

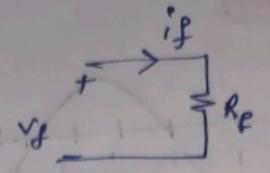

131

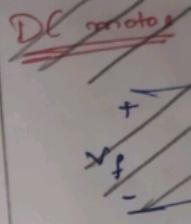

DC motor

 R_f : field winding resistance V_f : field winding voltage i_f : field current. $V \propto \phi$ where ' ϕ ' is magnetic flux N : speed of rotor in RPM $V \propto N$


$$\boxed{V \propto N\phi}$$

DC Machine

functions of 'N' depend

DC Generator

DC motor

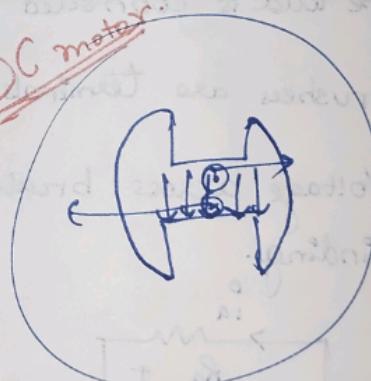 T : Torque developed

$$T \propto \phi$$




$$T \propto i_a$$

$$\boxed{T \propto \phi i_a}$$

all same
for
DC
motor
also

D

not po
of DC

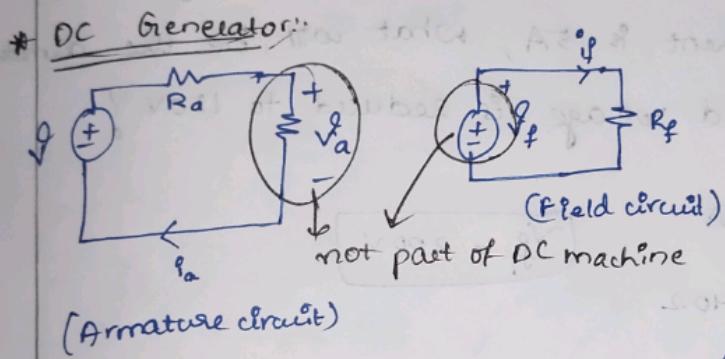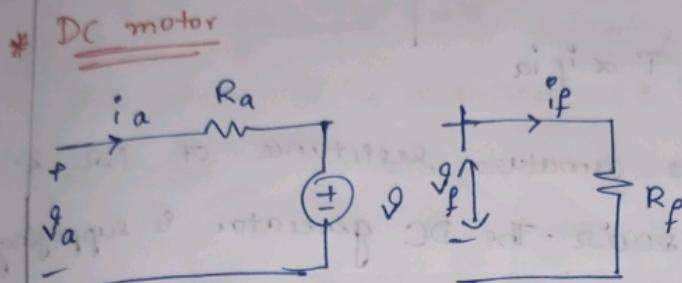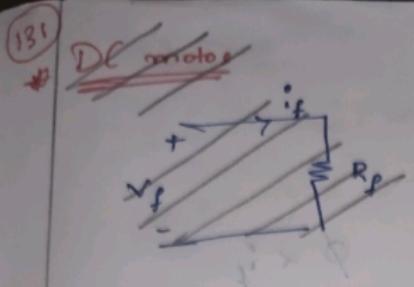

ψ : emf induced in armature

R_a : armature resistance

i_a : armature current

V_a : armature terminal voltage.

V_f : Voltage applied to field winding



i_f : field current

ψ : Magnetic flux produced by i_f

N : speed in RPM

(Assumption:- Effect of ψ on magnetic flux is negligible)

All same
for
DC
motor
also

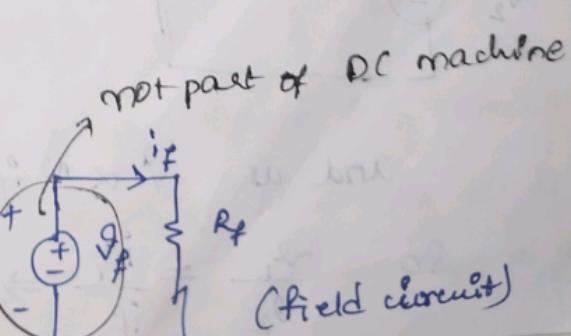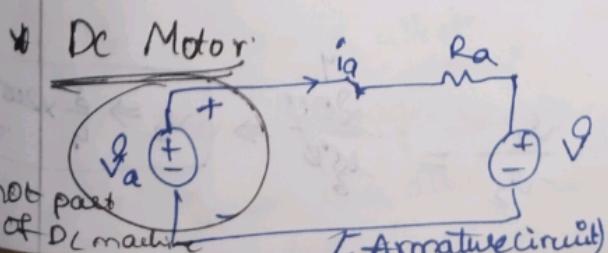

(132)

T: Torque developed


DC Generator & DC motor

$$\mathcal{V} \propto N\phi \Rightarrow \mathcal{V} \propto N i_f$$


DC motor

$$T \propto \phi i_a \Rightarrow T \propto i_f i_a$$

- Q) A DC generator has armature resistance of 1Ω & field resistance of 200Ω . The DC generator is supplying power to a 40Ω resistor. If the field voltage is $200V$, the armature current is $5A$, what will be the armature current if the field voltage is reduced to $150V$?

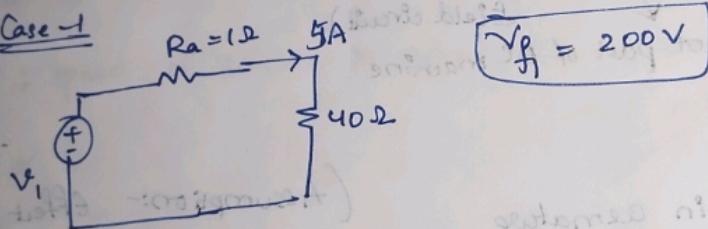Sol:Case 1

$$V_1 = 5(41) = 205V$$

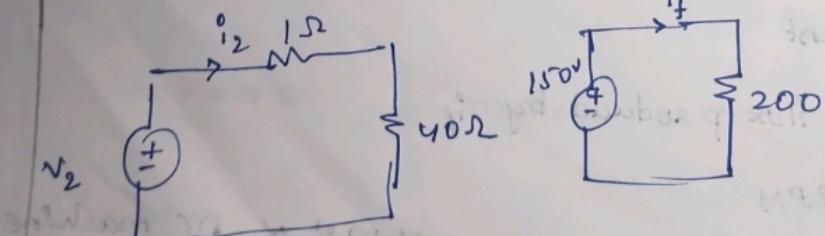Case 2and as $\mathcal{V} \propto N i_f$

$$\text{So } \frac{V_1}{V_2} = \frac{i_f}{i_f} \Rightarrow \frac{V_1}{V_2} = \frac{200}{150} \Rightarrow$$

$$V_2 = \frac{3}{4} \times 205$$

(133) and C

 $\frac{3}{4} C$ i_2

A D

1KW

800 F

80.

Q.)

133

and hence

$$\frac{3}{4} \times 265 = i_2 (4\pi)$$

$$i_2 = \frac{15}{4} A \Rightarrow 3.75 \text{ Amp.}$$

- (Q) A DC generator while running at 1000 RPM is supplying 1KW power to a 50Ω resistor & If speed is reduced to 800 RPM, what will be power supply. ($R_a = 1\Omega$)

so.

$$1000 = i_{a_1}^2 (50) \Rightarrow i_{a_1}^2 = 20 \Rightarrow v_1 = 51(\sqrt{20})$$

$$x = i_{a_2}^2 (50)$$

$$v_2 = \frac{N_2 i_{a_2}}{N_1 i_{a_1}} = \frac{N_2}{N_1}$$

$$\Rightarrow \frac{v_2}{228.1} = \frac{800}{1000}$$

$$v_2 = \sqrt{1}$$

~~$i_{a_1} = \frac{i_{a_2}^2}{x + R_a}$~~

~~$i_{a_2} = \frac{51}{51}$~~

~~$i_{a_2} = \frac{20}{x + R_a}$~~

~~$x = \frac{20}{51}$~~

~~$x = \frac{N_2^2}{N_1^2}$~~

~~$x = \frac{1}{4}$~~


and power = $\left(\frac{v_2}{51} \right)^2 (50) W$

- (Q) The armature winding of a DC motor is connected to a 240V voltage source. Armature resistance is 0.13Ω & armature current is 80A. Motor runs at 1400 RPM

$$\frac{3}{4} \times 205$$

(B4)

Find the torque developed.

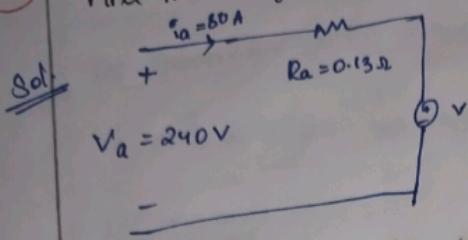

$V(i_a) = \text{mechanical Power}$

$$v = v_a - i_a R_a = 240 - 80(0.13) = 229.6V$$

$$N = 440 \text{ RPM} = 440 \times \frac{2\pi}{60}$$

$$\Rightarrow \frac{880\pi}{60}$$

$$\Rightarrow \frac{44\pi}{3}$$

$$T = \frac{(229.6)(80)(3)}{44\pi}$$

$$T = 398.6 \text{ Nm}$$

and $T_w = \text{mechanical power}$

* DC machines:-

$$v \propto N\phi \Rightarrow v = k_1 N \phi$$

$$T \propto \phi i_a \Rightarrow T = k_2 \phi i_a$$

$$\text{and as } v = \frac{T N \pi}{30}$$

$$k_1 = \frac{k_2 \pi}{30}$$

Q) A DC motor has armature resistance of 0.4Ω . The armature is connected to a $220V$ voltage source. The motor runs at 1500 RPM , when the armature current is $40A$. What will be

(B5) the spe speed

Case-1


N

220V

-

Q1. If the speed of the armature current is 40A. What will be the speed if armature current changes to 10A.

Case - 1

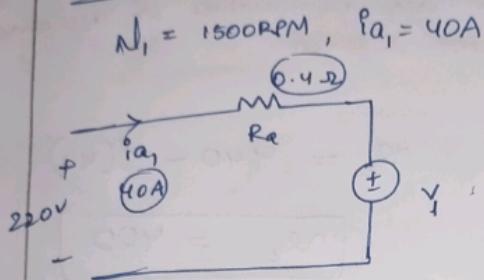


$$V_1 = 220 - 40(0.4)$$

$$V_1 = 204 \text{ Volts}$$

Case - 2
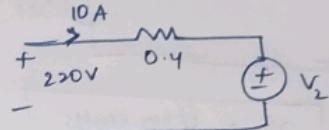
$$N_2 = ? \text{ RPM}, i_{a2} = 10 \text{ A}$$



$$V_2 = 220 - 10(0.4)$$

$$V_2 = 216 \text{ Volts}$$


$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\left(\frac{216}{204} \right) = \left(\frac{N_2}{1500} \right)$$

$$N_2 = 1588 \text{ RPM}$$


- Q2. A DC motor draws an armature current of 20A and runs at 1000 RPM, when the armature is connected to a 250V voltage source, armature resistance is 0.5Ω. If the speed is reduced to 500 RPM without torque change, what should be armature terminal voltage?

$$N = 1000 \text{ RPM}$$

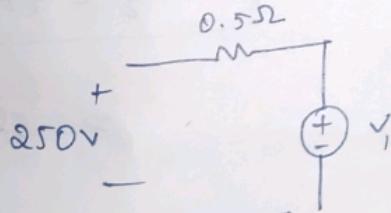

$$250 - i_a (0.5) = V_1$$

$$V - i_a (0.5) = \frac{V_1}{2}$$

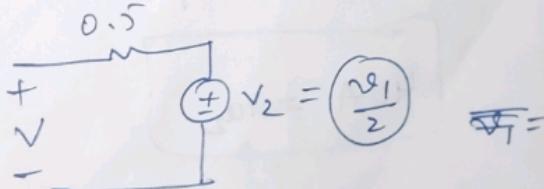

$$2V - i_a = 250 - \frac{i_a}{2}$$

$$2V = 250 + \frac{i_a}{2} \quad (2i_a = 20A) \\ \Rightarrow V = 130$$


mechanical power

armature
is at
be

Our commitment deeper. And our efforts greater.
This is my dream for Reliance and for India.

- (Q) A DC motor draws an armature current of 20A and runs at 500RPM, when armature is connected to 440V source. ($R_a = 1\Omega$) If the load reduces by 30%, and 'T' is decreased by 40%. Simultaneously what are new values of armature current & speed?

$$N = 500 \text{ RPM}$$

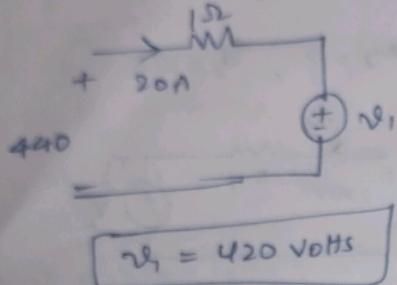

$$v_2 = 440 - 1(40)$$

$$v_2 = 400$$

$$\phi_2 = \frac{7\phi_1}{10}$$

$$\frac{T_1}{T_2} = \frac{\phi_1 i_{a1}}{\phi_2 i_{a2}} = \left(\frac{10}{7}\right) \frac{i_{a1}}{i_{a2}}$$

$$T_2 = \frac{14T_1}{10}$$

$$\frac{10}{14} = \frac{10}{7} \left(\frac{i_{a1}}{i_{a2}} \right)$$

$$\alpha = \frac{i_{a2}}{i_{a1}}$$

$$40A = i_{a2}$$

$$\frac{v_1}{v_2} = \frac{N_1 \phi_1}{N_2 \phi_2}$$

$$\frac{420}{400} = \frac{500}{N_2} \left(\frac{10}{7} \right)$$


$$N_2 = 476.19 \times \frac{10}{7} \text{ RPM}$$

$$= 680.2 \text{ RPM}$$

A
Q)

- The armature resistance and field resistance of a DC motor are 0.5Ω and 250Ω respectively. Both the armature & field windings are connected to a 250V voltage source. The motor

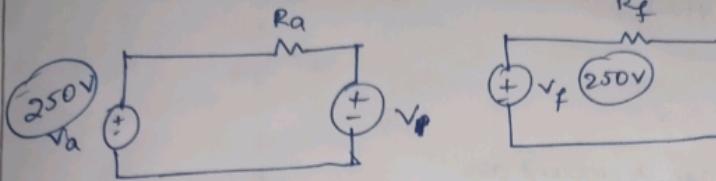(13) Is running at 600RPM by $i_a = 20A$. If 'N' is changed to 800RPM, 'I' same,
what is v_f . Rated armature current 250Ω 30A.



$$250 - 10 = 240$$

$$i_{f_1} = \frac{250}{250} = 1 \text{ Amp}$$

$$i_{a_1} = 20 \text{ A}$$

$$N_1 = 600 \text{ RPM}$$

$$N_2 = 800 \text{ RPM}$$

$$\tau_1 = \tau_2 \Rightarrow i_{f_1} i_{a_1} = i_{f_2} i_{a_2}$$

$$\Rightarrow 20 = \left(\frac{v_f}{250} \right) (i_{a_2})$$

$$\frac{v_f}{v_f} = \frac{N_1}{N_2} \frac{i_{f_1}}{i_{f_2}}$$

183.59

$$\frac{240}{250 - 30(0.5)} = \frac{600}{800} \quad \begin{array}{l} \cancel{i_{f_1}} \\ \cancel{i_{f_2}} \end{array} \rightarrow \frac{20}{i_{a_2}}$$

we get quadratic
in i_a and one
will be rejected
as $i_a \leq 30 \text{ A}$.

$$\left(\frac{240}{235} \right) \frac{800}{600} = \frac{1}{i_{f_2}}$$



and

$$\frac{v_f}{250} = i_{f_2}$$

$$v = 183.59 \text{ Volts}$$


Rectifier circuits

Diode - semiconductor device

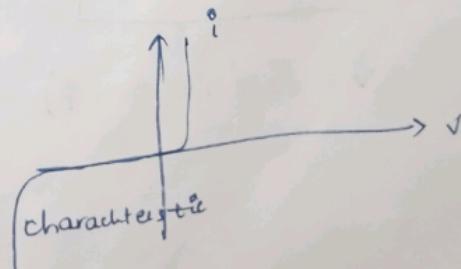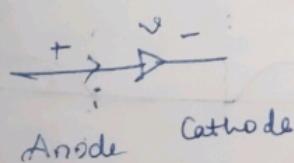

Our dreams have to be bigger. Our ambitions higher.


* Rectifiers.

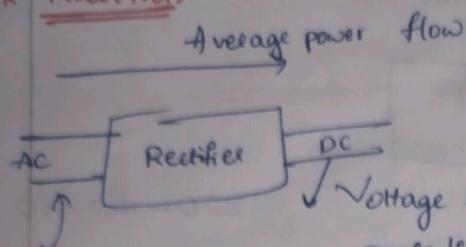



Voltage is
Sinusoidal
no comment on
current's nature

Voltage & current are
periodic & have a
nonzero avg value.



* Ideal diodes.


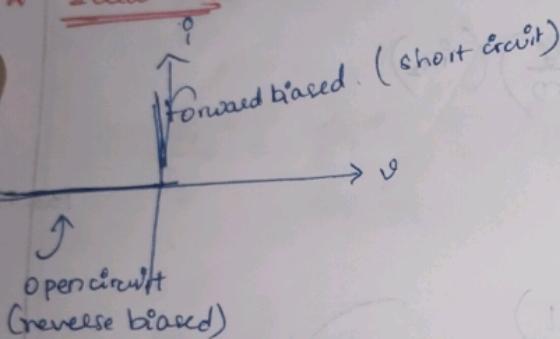


* Halfwave Rectifier.

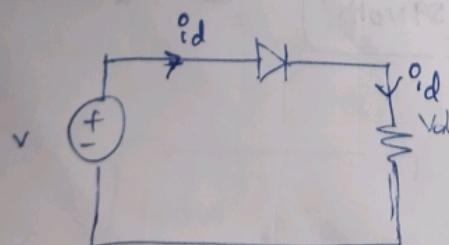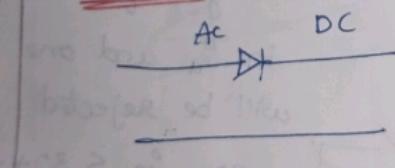


$$v = \sqrt{2} \sin(\omega t + \phi)$$

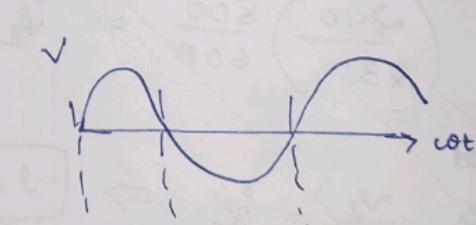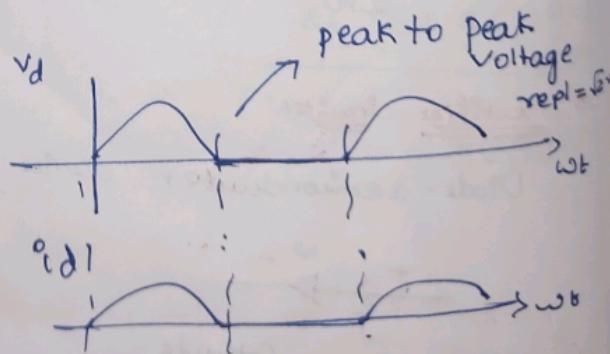

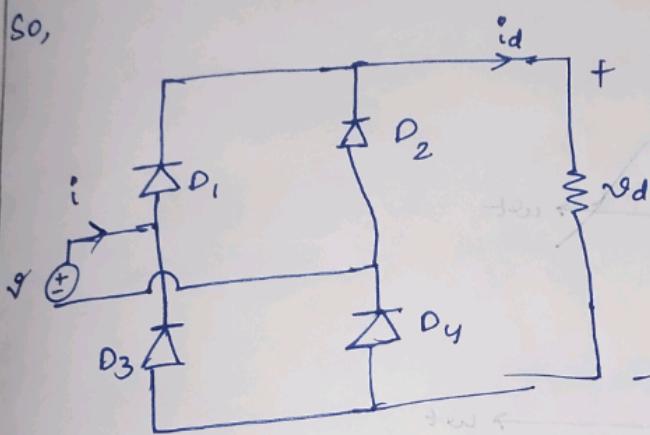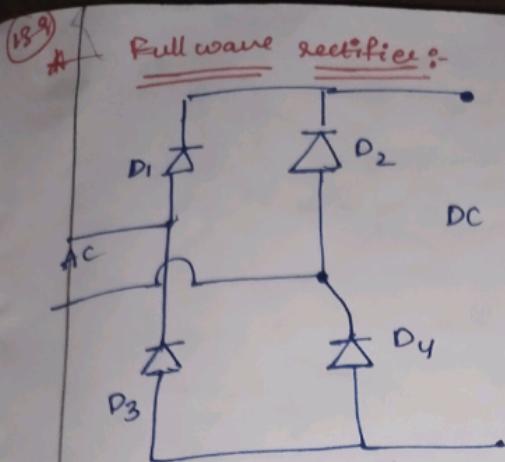


$$v = \sqrt{2} \sqrt{\sin(\omega t + \phi)}$$

A. With Q. And hence it is clear

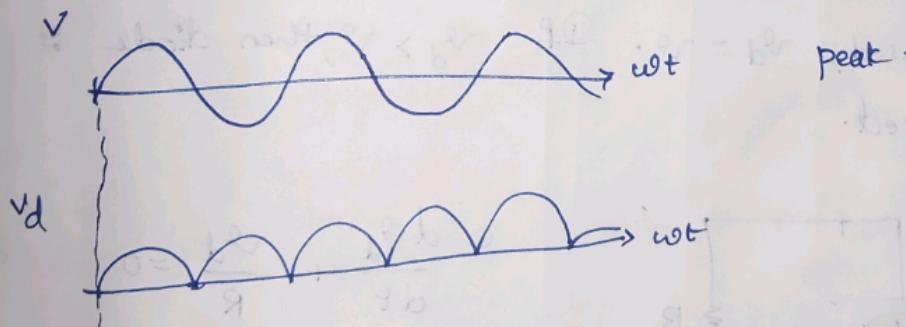

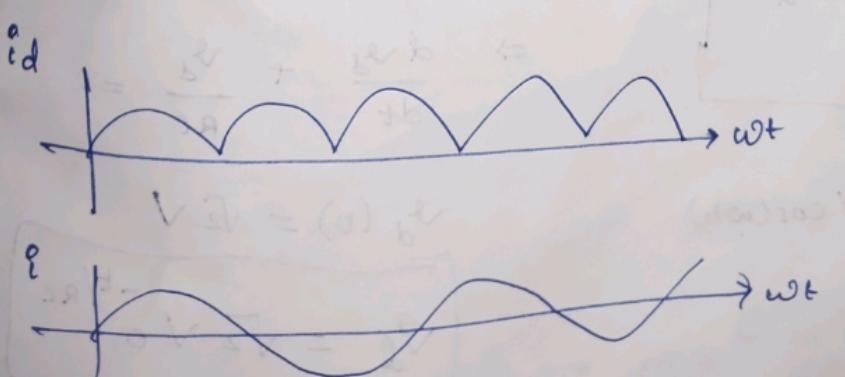peak to peak voltage repl
based on $\sqrt{2}$ = $\sqrt{2} V$




voltage repl = $\sqrt{2} v$

$\rightarrow \omega t$

ωt


MO

Peak to peak voltage repl:

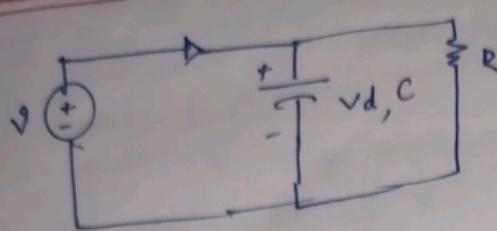


$$V = \sqrt{2} V \sin(\omega t)$$

$$v_d(0) = 0$$

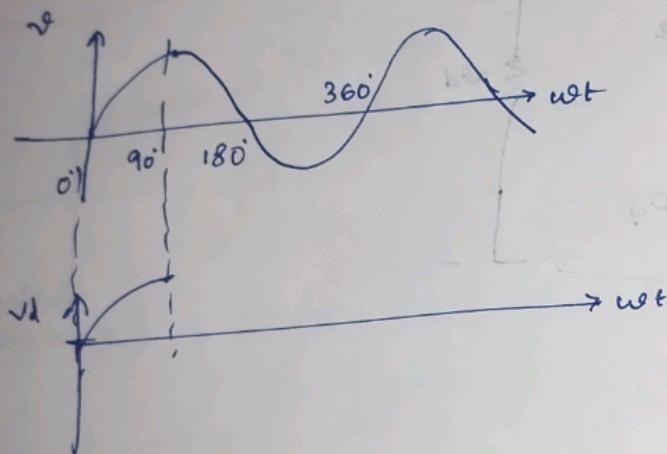

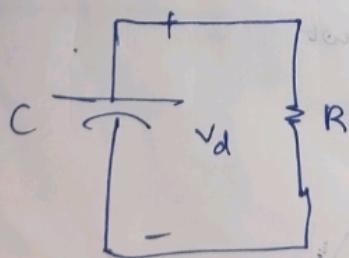If $V > v_d$ diode is forward biased. One diode is forward biased, $v_d = V$. If $v_d > V$, then diode is reverse biased.





$$C \frac{dv_d}{dt} + \frac{v_d}{R} = 0$$

$$\Rightarrow \frac{dv_d}{dt} + \frac{v_d}{RC} = 0$$

$$V = \sqrt{2} V \cos(\omega t)$$

$$v_d(0) = \sqrt{2} V$$

$$v_d = \sqrt{2} V e^{-t/RC}$$

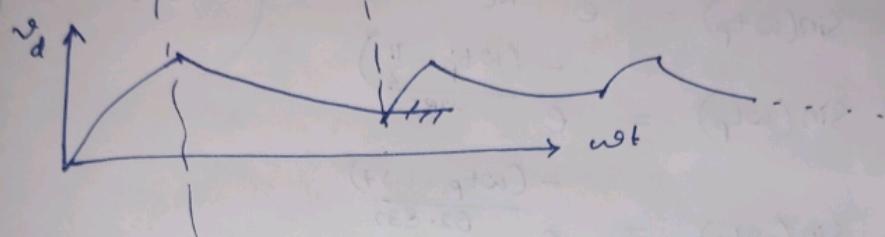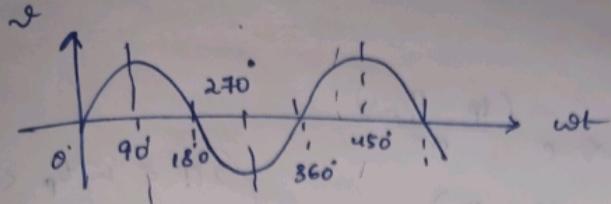

Q) $\sqrt{2} = 230$ Volts, Frequency = 50Hz, $R = 100\Omega$. Find 'C' such that peak-peak ripple is 20V.


Sol: $230\sqrt{2}$ is one peak.

$$(230\sqrt{2}) e^{-\frac{t}{100C}} = (230\sqrt{2}) \sin(2\pi(50)t)$$

and $230\sqrt{2} - 230\sqrt{2} \sin(100\pi t) = 20V$


$$\frac{230\sqrt{2} - 20}{230\sqrt{2}} = 230\sqrt{2} \sin(100\pi t)$$
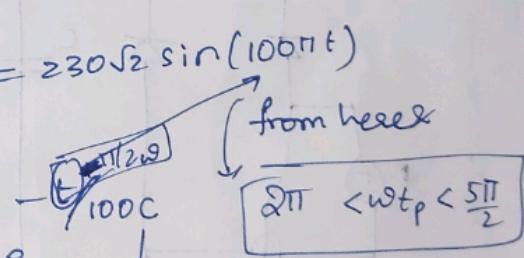
$$(230\sqrt{2} - 20) = (230\sqrt{2}) e^{-\frac{t}{100C}}$$



we get 'C'.

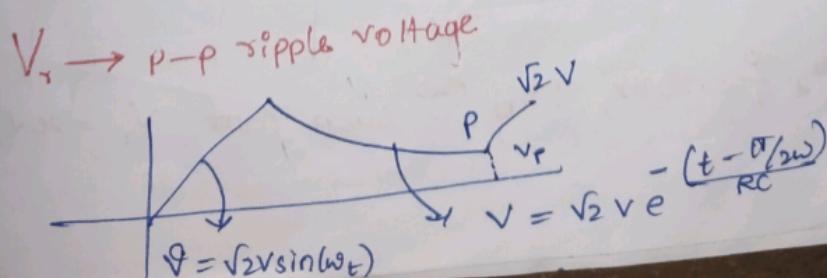Q) If in the previous problem $C = 2mF$, then what is the value of V_r \rightarrow p-p ripple voltage?



Our dreams have to be bigger. Our ambitions deeper. Our commitment deeper. And our efforts greater.

$$V_r = \sqrt{2} V - V_p$$


At $P \rightarrow$

$$\sqrt{2} V \sin(\omega t_p) = \sqrt{2} V e^{-\frac{(t_p - \pi/2\omega)}{RC}}$$

$$\sin(\omega t_p) = e^{-\frac{(t_p - \pi/2\omega)}{RC}}$$

$$\sin(\omega t_p) = e^{-\frac{(\omega t_p - \pi/2)}{\omega RC}}$$
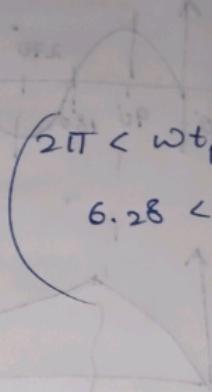
$$\sin(\omega t_p) = e^{-\frac{(\omega t_p - 1.57)}{62.832}}$$





$$\omega t_p = 7.429$$

$$V_p = \sqrt{2} V \sin(7.429)$$

$$= \sqrt{2} V (0.911)$$

$$V_r = \sqrt{2} V (0.089) = 28.95V$$

* Full wave rectifier :-


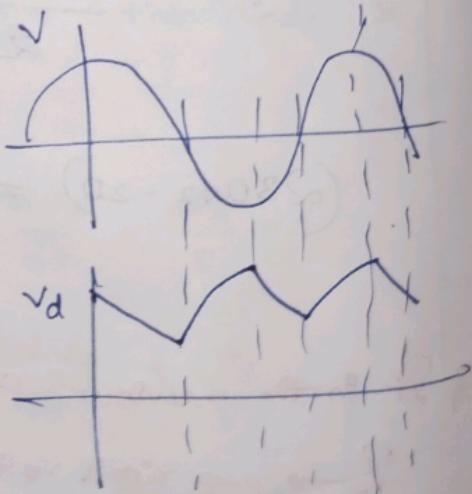
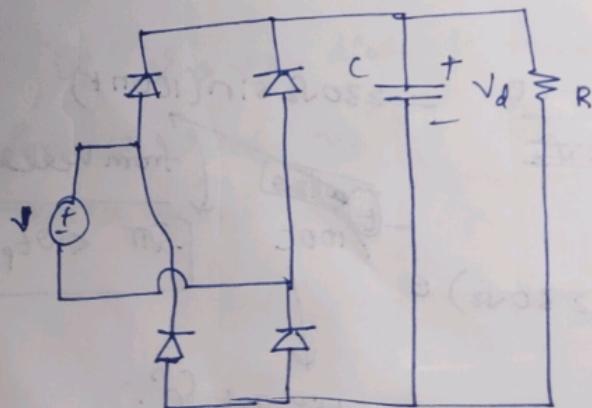


Q) $V = 230 \text{ Volts}$, $f = 50 \text{ Hz}$, Find C such that $V_r = 20V$,

$$R = 100\Omega$$

(143)

$$\left. \frac{5\pi}{2} < 7.85 \right)$$

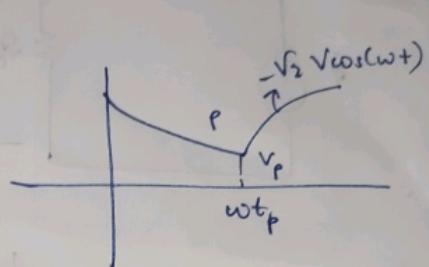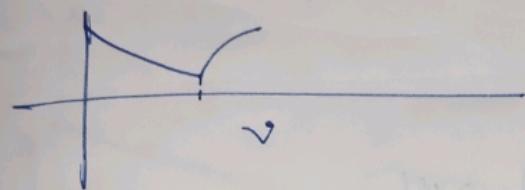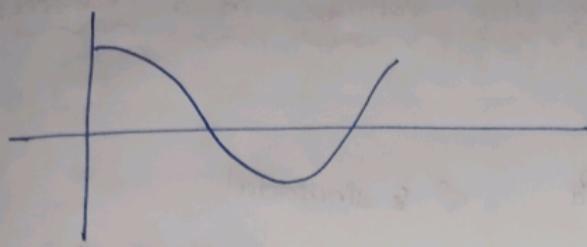

$$V_r = \sqrt{2}V - V_p$$

$$V_p = \sqrt{2}(230) - 20 = 305.27 \text{ V}$$

$$\sqrt{2} V e^{-\frac{t_p}{RC}} = -\sqrt{2} V \cos(\omega t_p)$$

$$e^{-\frac{t_p}{RC}} = -\cos(\omega t_p)$$

$$V_p = -\sqrt{2} V \cos(\omega t_p) = 305.27$$

$$\cos(\omega t_p) = -0.9385$$

$$\omega t_p = 2.789$$

$$\left(\frac{\pi}{2} < \omega t_p < \pi \right)$$

$$1.57 < \omega t_p < 3.14$$


$$e^{-\frac{2.789}{RC}} = 0.9385$$

$$-\frac{2.789}{\ln(0.9385) \cdot RC} = C$$

$$\Rightarrow C = 0.001399 F = 1.399 \text{ mF}$$


Our dreams have to be bigger. Our efforts greater.
TVS is my dream for Reliance.

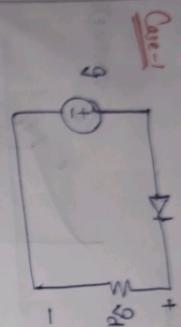Case 1
Average values of DC side voltage in a rectifier.



v_d is sinusoidal


$v_d = \sqrt{2} V_{rms}$

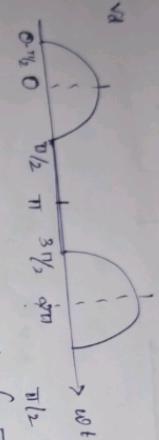

$$\text{Average value of } v_d = \frac{1}{\pi} \int_0^{\pi} \sqrt{2} V_{rms} \cos(\omega t) d(\omega t)$$


$$= \frac{\sqrt{2} V_{rms}}{\pi}$$

Average v_d

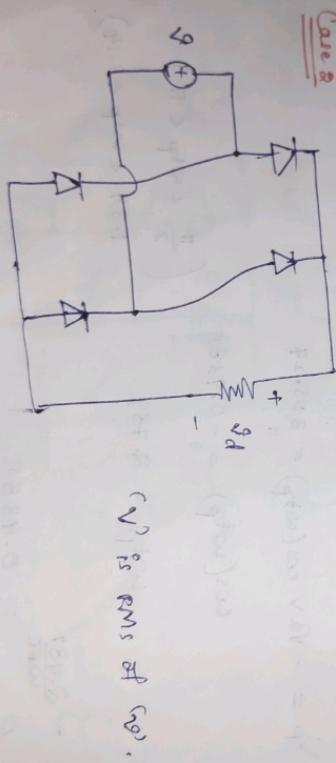

(v_d) is RMS of (v) .

Graph

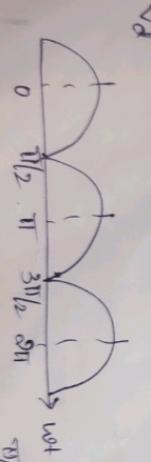

$$\text{Average value of } v_d = \left(\frac{1}{\pi/2} \right) \int_0^{\pi/2} \sqrt{2} V_{rms} \cos(\omega t) d(\omega t) = \frac{2\sqrt{2} V_{rms}}{\pi}$$

Now
Case




v_d is sinusoidal

$v_d = \sqrt{2} V_{rms}$


Rectifiers

Case-3

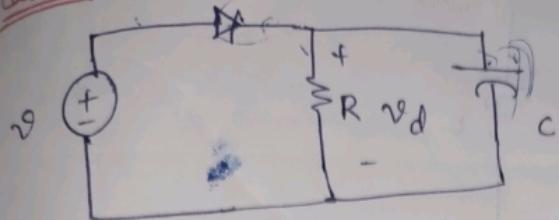

v is sinusoidal

$$v = \sqrt{2} V \cos(\omega t)$$

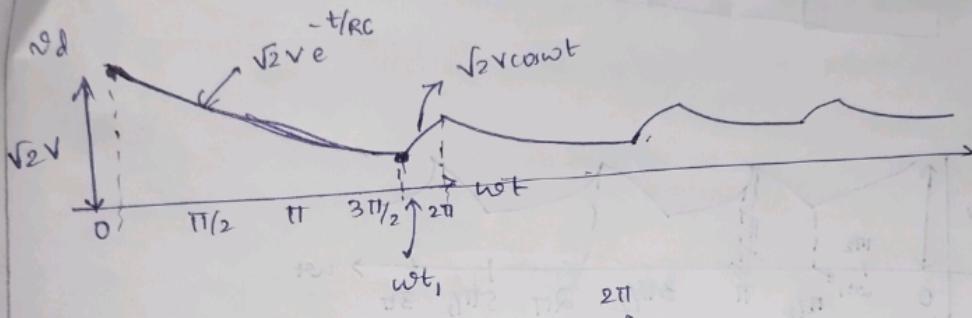

Average value of $v_d = \frac{1}{2\pi} \int_0^{2\pi} v_d d(\omega t)$

$$= \left(\frac{1}{2\pi} \right) \left(\int_0^{\omega t_1} \sqrt{2} \sqrt{e^{-t/RC}} (\omega dt) + \int_{\omega t_1}^{2\pi} \sqrt{2} \cos(\omega t) dt \right)$$



$$= \left(\frac{1}{2\pi} \right) \left((\sqrt{2} \times \omega) \left(\frac{-t}{RC} (-RC) \right)_0^{\omega t_1} + \sqrt{2} \omega (-\sin \omega t_1) \right)$$

$$\Rightarrow \frac{1}{\sqrt{2}\pi} \left((\omega \times RC) \left(1 - e^{-\frac{\omega t_1}{RC}} \right) - \omega \sin \omega t_1 \right)$$

$$\Rightarrow \frac{\sqrt{2}}{\sqrt{2}\pi} \left(\omega RC \left(1 - e^{-\frac{\omega t_1}{RC}} \right) - \sin \omega t_1 \right)$$

* New other case

Case-4

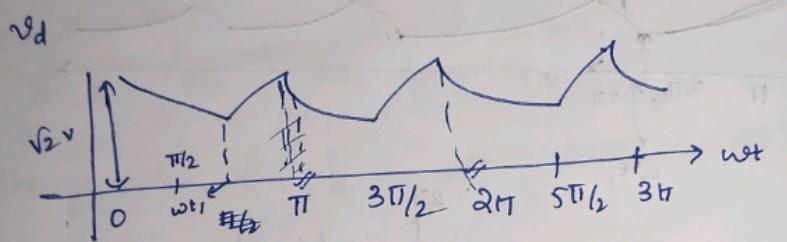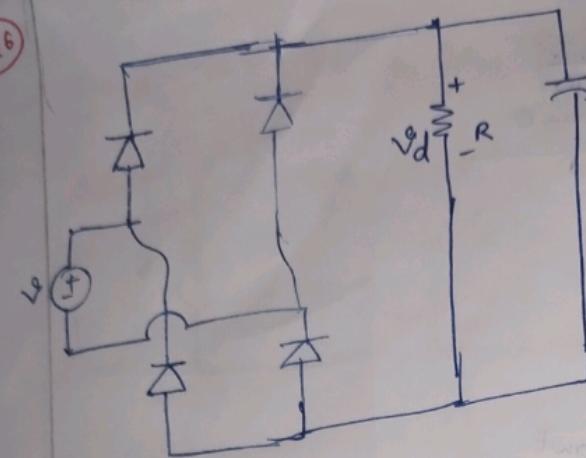

$$\text{Average value of } v_d = \frac{1}{\pi} \int_0^{\pi} v_d d(\omega t)$$

$$= \frac{1}{\pi} \left[\int_0^{\omega t_1} \sqrt{2} V e^{t/R_C} d(\omega t) + \int_{\omega t_1}^{\pi} (-\sqrt{2} V \cos(\omega t) d(\omega t)) \right]$$


$$= \frac{\sqrt{2}V}{\pi} \left[w_{RL} \left(1 - e^{-\frac{t}{T_{RL}}} \right) + \sin(\omega t_1) \right]$$


Operational amplifiers (Op amp)

Transistor (semiconductor device) - 3 terminals

→ Circuit consisting of many transistors, resistors & voltage sources.

Black box representation of op amp.

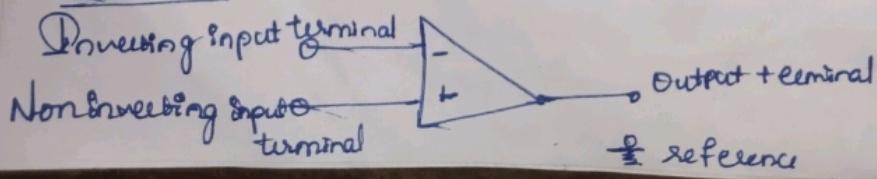

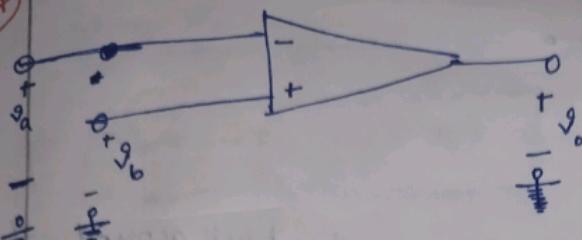

* Conditions:

There should be a circuit element or short circuit between the output terminal & inverting input terminal.

Typically:-


$$\textcircled{1} \quad \frac{V_o}{V_b - V_a} = 10^5$$

- \textcircled{2} Current that flows into or out of the input terminals is of the order of nano Amperes (10^{-9}) or less.


* Ideal op amp

$$\textcircled{1} \quad V_b \equiv V_a$$

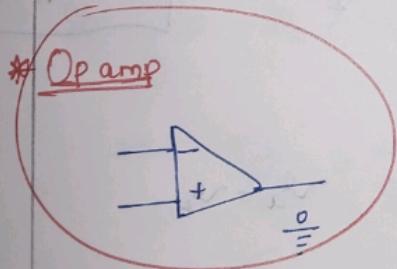- \textcircled{2} Current that flows into or out of the input terminals is zero.



* Inverting amplifier:-

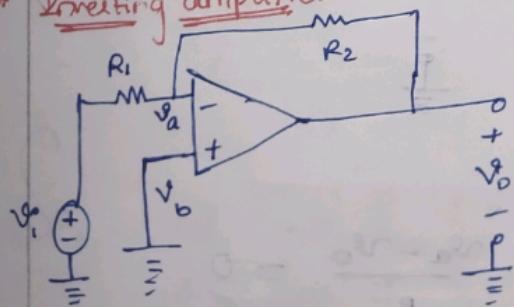


$$V_a = V_b = 0$$

$$\frac{V_a - V_i}{R_1} + \frac{V_a - V_o}{R_2} = 0$$


$$\Rightarrow V_o = -\frac{R_2}{R_1} V_i$$

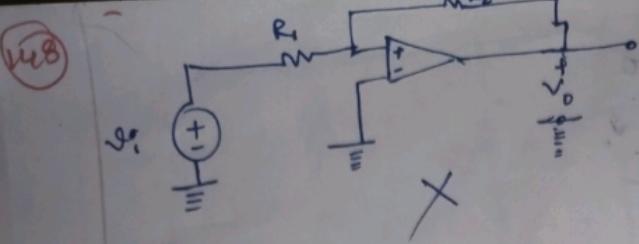Our dreams have to be bigger. Our ambitions too.



(We cannot analyse this circuit with the background that we have as there is no short or circuit element b/w inverting input terminal & output terminal)


* Non-inverting amplifiers:-

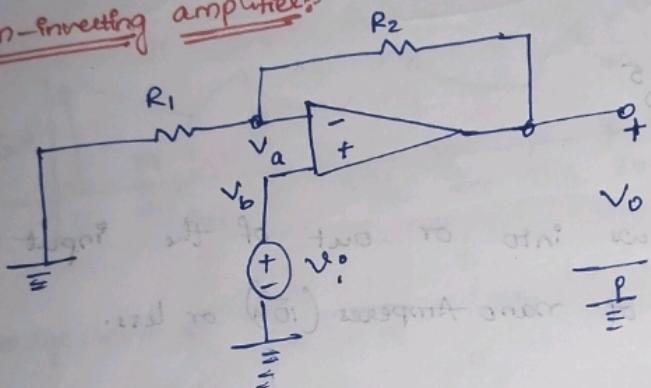

$$V_a = V_b = V_o$$

$$(KVL \text{ about } V_a) \frac{V_a}{R_1} + \frac{V_a - V_o}{R_2} = 0 \Rightarrow \frac{V_i}{R_1} + \frac{V_i - V_o}{R_2} = 0 \Rightarrow V_o = \frac{R_1 + R_2}{R_1} V_i$$

* Summing amplifiers:-

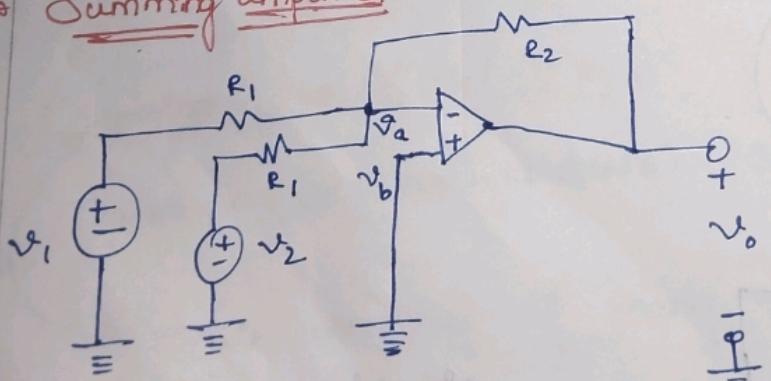

$$V_a = V_b$$


$$\text{Here } V_b = 0$$

$$(KVL \text{ about } V_a) \frac{V_a - V_1}{R_1} + \frac{V_a - V_2}{R_2} + \frac{V_a - V_o}{R_f} = 0$$

$$149 \quad \frac{v_1}{R_1} + \frac{v_2}{R_1} + \frac{v_o}{R_2} = 0$$

$$\Rightarrow v_o = -\frac{R_2}{R_1} (v_1 + v_2)$$

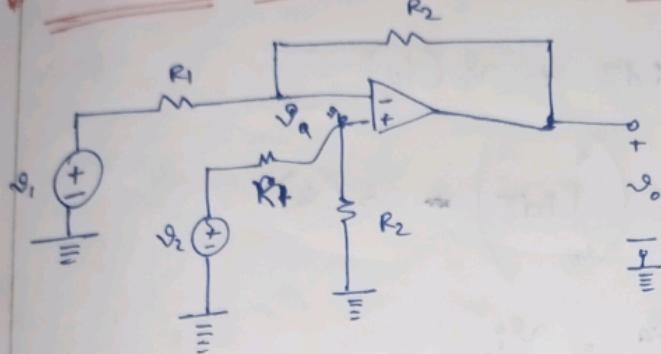Difference amplifier or differential amplifier :-



$$v_a = v_b$$

and (KVL about v_a)

$$\frac{v_a - v_1}{R_1} + \frac{v_a - v_o}{R_2} = 0 \Rightarrow v_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_1}{R_1} + \frac{v_o}{R_2}$$


$$\text{(KVL about } v_b) \frac{v_b - v_2}{R_1} + \frac{v_b}{R_2} = 0 \Rightarrow v_b \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v_2}{R_1}$$

$$\text{So as } v_a = v_b$$

$$\Rightarrow \frac{v_b}{R_1} + \frac{v_o}{R_2} = \frac{v_2}{R_1}$$

$$\Rightarrow v_o = (v_2 - v_1) \left(\frac{R_2}{R_1} \right)$$

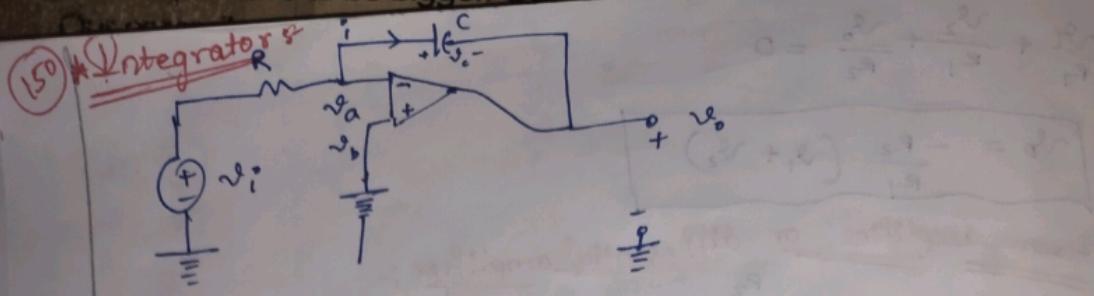So, $v_o > 0$ if $v_2 > v_1$
 $v_o < 0$ if $v_2 < v_1$




$$v_a - v_o = \frac{1}{C} \int_{t_0}^t i d\tau + v_c(t_0)$$

$$v_a = 0 \Rightarrow v_o = -\frac{1}{C} \left(\int_{t_0}^t i d\tau \right) + v_c(t_0)$$

and as $i = \frac{v_i - v_a}{R} = \frac{v_i}{R}$

So $v_o = -\frac{1}{RC} \int_{t_0}^t v_i d\tau + v_c(t_0)$

* Differentiator

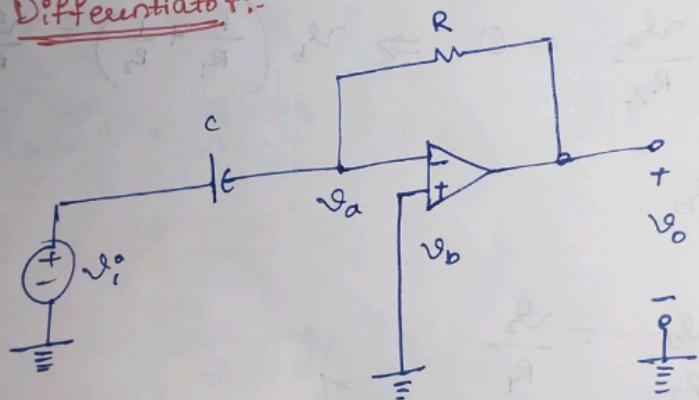


$$v_a = v_b = 0$$

$$i = \frac{v_a - v_o}{R} = -\frac{v_o}{R}$$

$$i = C \frac{d v_o}{dt}, \quad v_o = -RC \frac{d v_i}{dt}$$


Q1

Buffer or voltage follower:-

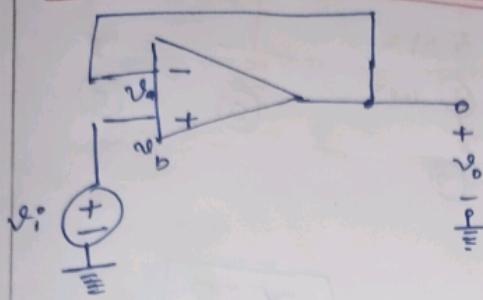

$$v_a = v_o = v_b = v_i$$

Q2

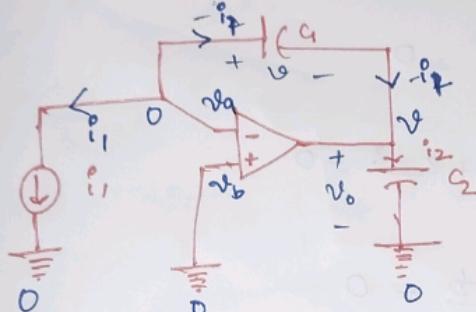


Find expressions for $\frac{i_2}{i_1}$ in terms of C_1 & C_2

Sol.

$$v_a = v_b = 0 \quad \text{so} \quad -i_1 = C_1 \frac{dv}{dt}$$

$$\begin{aligned} \int i_2 dt &= -v \\ \frac{q}{C_1} &= -v \\ \int i_2 dt &= \frac{q}{C_2} \\ &\text{so} \quad i_2 = C_2 \frac{d v_o}{dt} \\ &\text{so} \quad \frac{C_1}{C_2} = -\frac{i_1}{i_2} \end{aligned}$$

Q3

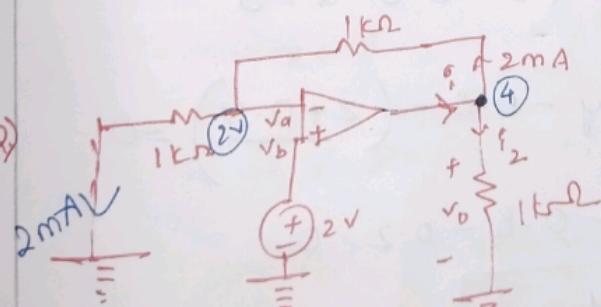

find i

$$i_2 = 4 \text{ mA}$$

$$i = 6 \text{ mA}$$


Sol.

$$v_a = v_b = 2V \text{ and}$$

$$\frac{v_o}{1} + 2 - i = 0$$

"Our dreams have to be bigger. Our ambitions deeper. Our commitment deeper. And our efforts more intense."

153

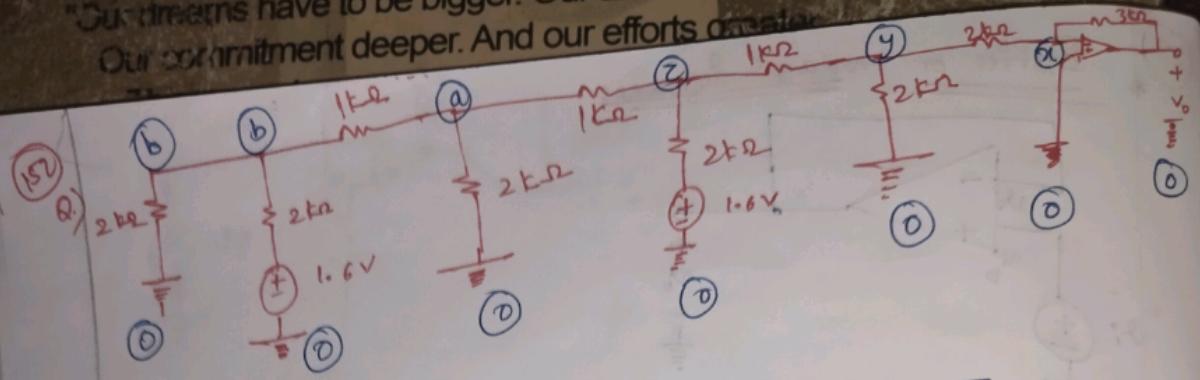

Find v_o .

Sol:

$$\frac{x - v_o}{3} + \frac{x - y}{2} = 0$$

$$x = 0$$

$$\text{as } v_a = v_b = 0$$

$$\frac{y - z}{1} + \frac{y}{2} + \frac{y - x}{2} = 0$$

$$\frac{z - y}{1} + \frac{z - 1.6}{2} + \frac{z - a}{1} = 0$$

$$\frac{a}{2} + \frac{a - z}{1} + \frac{a - b}{1} = 0$$

$$\frac{b - a}{1} + \frac{b - 1.6}{2} + \frac{b}{2} = 0$$

$$b - a + b - 0.8 = 0$$

$$2b - a = 0.8$$

$$2a + \frac{a}{2} - \left(\frac{0.8 + a}{2} \right) = z$$

$$2a - 0.4 = z$$

$$z - y + \frac{z}{2} + z - 0.8 - a = 0$$

$$2z + \frac{z}{2} - y - 0.8 - \left(z + 0.4 \right) = 0$$

$$2z - y - 0.8 - 0.2 = 0$$

$$2z - y = 1$$

$$y - z + y = 0$$

$$2y - 2z = 0$$

$$2z - y = 1$$

$$3y = 1$$


$$Y = Y_3$$

$$z = \frac{2}{3}$$

$$-\frac{v_0}{3} + 0 - \frac{1}{6} = 0$$

$$\frac{20}{3} + \frac{1}{6} = 0$$

$$v_0 = -0.5 v_0 \text{ Hz.}$$

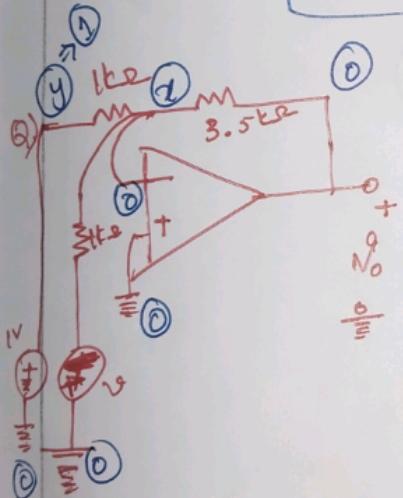

If $\mathcal{V}_0 = 0$, find (\mathcal{V}) .

$$\frac{x+y}{1} + \frac{x-y}{1} + \frac{2x}{7} = 0$$


$$x+2 + x-1 + \frac{2x}{7} = 0$$

$$y + 2x \left(\frac{6}{7} \right) = 1$$

$$\text{as } x \geq 0$$

$$2^0 = 1$$

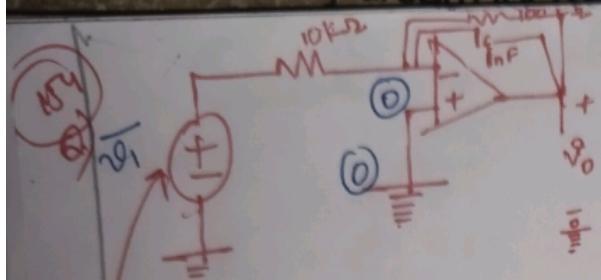Our dreams have to be bigger. Our ambitions higher.
 Our commitment deeper. And our efforts greater.
 This is my dream for Reliance.




$$v = \sqrt{2} \sin(2\pi ft)$$

(t) is time, (f) is Hz.

All voltages and currents are sinusoidal. find (f) such that RMS of v_0 is 1V.

Sol/

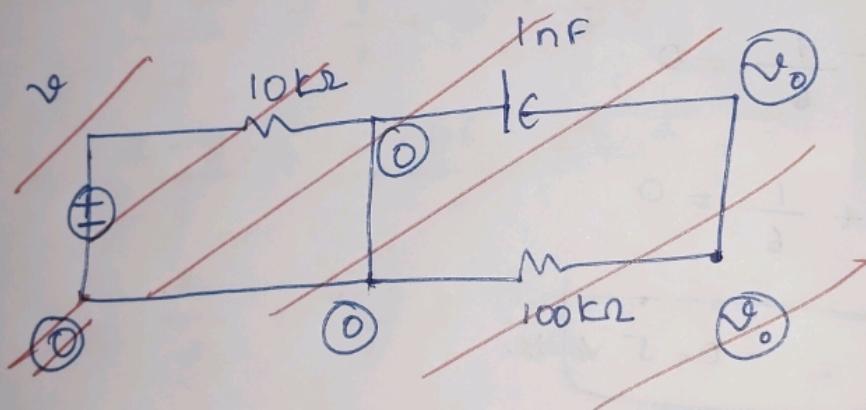

$$\frac{-j}{\omega C} \Rightarrow \frac{-j}{\omega (10^9)} \Rightarrow \frac{-j (10^9)}{\omega}$$

$$\frac{\omega(j)}{-10^9(j)^2 + \frac{10}{10^9}} = \frac{1}{Z_{eff}}$$


$$\frac{\omega j + 10^4}{10^9} = \frac{1}{Z_{eff}}$$

$$(j\omega - 28) - (1) \left(\frac{1}{10^9}\right)$$

$$v = \sqrt{2} \sin(2\pi f t)$$

t is time, f is freq.

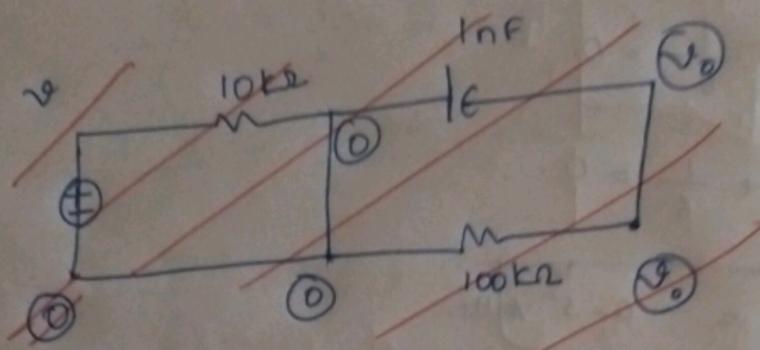All voltages and currents are sinusoidal. Find f such that RMS of v_0 is 1V.



$$\frac{-j}{\omega C} \Rightarrow \frac{-j}{\omega (10^9)} \Rightarrow -j \frac{10^9}{\omega}$$

$$\frac{\omega(j)}{-10^9(j)^2 + \frac{10^4}{10^9}} = \frac{1}{Z_{eff}}$$

$$\frac{(\omega j + 10^4)}{10^9} = \frac{1}{Z_{eff}}$$

$$(v - v_0) = (1) \frac{10^9}{\omega j + 10^4}$$

$$v_a = v_b = 0$$

$$80 \left(\frac{\overline{v}_1}{10k\Omega} \right) = \left[\frac{\overline{v}_0}{\frac{100 (-j \frac{10^9}{2\pi f}) k\Omega}{100 (-j)(10^4)/2\pi f}} \right]$$

W5

$$\text{and } |\bar{v}_1| = |\bar{v}_0|$$

so,

$$(0 \times 10^3) = \left| \frac{\left(100 \times 10^3 \right) \left(-j \times \frac{10^9}{2\pi f} \right)}{100 \times 10^3 - j \left(\frac{10^9}{2\pi f} \right)} \right|$$

$$f = 15.84 \text{ kHz}$$