

g-04-2023 (lecture-12)

$$\frac{dx}{dt} + ax + b = 0$$

$$x(t_0) = c$$

a, b, c are real constants. What is $x(t)$ for $t > t_0$?

$$\begin{aligned} x e^{\int a dt} &= \int -b e^{\int a dt} dt \\ x e^{at} &= -b \int e^{at} dy \\ x e^{at} &= -b e^{at} + K \end{aligned}$$

at $t = t_0$

$$x = c$$

$$\Rightarrow c e^{at_0} = \left(-\frac{b}{a}\right) e^{at_0} + K$$

$$\Rightarrow K = e^{at_0} \left(c + \frac{b}{a}\right)$$

$$\text{So } \Rightarrow x = \left(-\frac{b}{a}\right) + e^{-at} \left[e^{at_0} \left(c + \frac{b}{a}\right)\right]$$

$$\Rightarrow x = -\frac{b}{a} + \left(\frac{b}{a} + c\right) e^{-a(t-t_0)}$$

Second order differential eq.

$$\frac{d^2x}{dt^2} + a \frac{dx}{dt} + bx + c = 0$$

$$x(t_0) = d, \quad \frac{dx}{dt} \Big|_{t=t_0} = f$$

a, b, c, d, f

$$a^2 - 4b = 0$$

$$x(t) =$$

Now Case

for

$$a^2 - 4b$$

$$x(t)$$

$$a^2 -$$

$$x(t)$$

H-04
Note:

$$e^{xt}$$

51. If a, b, c, d, f are real constants. What is $x(t)$ for $t > t_0$?

$$a^2 - 4b = 0$$

$$x(t) = e^{at/2} [c_1 + c_2 t] - \frac{c}{b}$$

Now Cases to get c_1, c_2

for $t = t_0$

$$\left. \begin{array}{l} x(t_0) = d \\ \frac{dx}{dt} \Big|_{t_0} = f \end{array} \right\} \text{Solve for } c_1, c_2$$

$$a^2 - 4b < 0$$

$$x(t) = \frac{-c}{b} e^{-at/2} \left[c_1 \cos \left(\frac{\sqrt{4b-a^2}}{2} t \right) + c_2 \sin \left(\frac{\sqrt{4b-a^2}}{2} t \right) \right]$$

\downarrow get c_1, c_2 by given conditions

$$a^2 - 4b > 0$$

$$x(t) = e^{-at/2} \left[c_1 e^{\frac{\sqrt{a^2-4b}}{2} t/2} + c_2 e^{-\frac{\sqrt{a^2-4b}}{2} t/2} \right] - \frac{c}{b}$$

\downarrow get c_1, c_2 by given conditions.

11-04-23

* NOTE: $\frac{dy}{dt} + fy = 0$ (f is a real number) $\rightarrow ①$

$e^{\alpha t}$ is one of soln.

$$\frac{d(e^{\alpha t})}{dt} + fe^{\alpha t} = \alpha e^{\alpha t} + fe^{\alpha t} = 0$$

$$\Rightarrow \alpha = -f$$

So we got one thing that $e^{\alpha t}$ satisfies ①

Suppose
satisfies
Now,

$$\frac{d^2x}{dt^2}$$

Defin

$$\frac{d^2}{dt^2}$$

80,

and

So,

Ω_r

(57) $\boxed{K e^{-ft}} \quad (\text{Case -2})$
 LHS of ① = $K e^{-ft}(-f) + K f(K e^{-ft}) = 0$

hence $K e^{-ft}$ satisfies ①. $\boxed{0 = d^2y - f_0}$

Now,

$$\frac{dx}{dt} + ax + b = 0 \rightarrow ②$$

$$\text{define } y = x + \frac{b}{a} \Rightarrow x = y - \frac{b}{a}$$

$$\frac{d(y - \frac{b}{a})}{dt} + a(y - \frac{b}{a}) + b = 0 \Rightarrow \frac{dy}{dt} + ay = 0 \rightarrow ③$$

So $K e^{-at}$ satisfies ③

$$\boxed{y(t) = K e^{-at}}$$

$$\boxed{x(t) = K e^{-at} - \frac{b}{a}}$$

$$0 > d^2y - f_0$$

12-04-2020

$$0 < d^2y - f_0$$

$$\frac{d^2y}{dt^2} + g \frac{dy}{dt} + hy = 0 \rightarrow ①$$

where (g) & (h) are real constants.

Let's see $K e^{at}$ is a possible soln or not, (allowing K, a to be non real also)

$$\frac{d^2(K e^{at})}{dt^2} + g \frac{d(K e^{at})}{dt} + h K e^{at} = 0$$

$$\Rightarrow K \alpha^2 e^{at} + g K \alpha e^{at} + h K e^{at} = 0$$

$$\Rightarrow K e^{at} (\alpha^2 + g\alpha + h) = 0$$

If provided $\alpha^2 + g\alpha + h = 0$,

let α_1 & α_2 be roots of $\alpha^2 + g\alpha + h = 0$

(53) Suppose $\alpha_1 \neq \alpha_2$, $k_1 e^{\alpha_1 t}$ & $k_2 e^{\alpha_2 t}$ satisfy (1) & (2) $k_1 e^{\alpha_1 t} + k_2 e^{\alpha_2 t}$
 satisfies (1)

Now,

$$\frac{d^2x}{dt^2} + a \frac{dx}{dt} + bx + c = 0 \rightarrow (2)$$

a, b, c are real constants

$$\text{Define } y = x + \frac{c}{b} \Rightarrow x = y - \frac{c}{b}$$

$$\frac{d^2y}{dt^2} + a \frac{dy}{dt} + by = 0 \rightarrow (3)$$

So, from our previous arguments, $k_1 e^{\alpha_1 t} + k_2 e^{\alpha_2 t}$ satisfies eq (3)

and where α_1, α_2 are roots of $a^2 + ax + b = 0$

So,

$$x(t) = k_1 e^{\alpha_1 t} + k_2 e^{\alpha_2 t} - \frac{c}{b} \quad \text{satisfies (2)}$$

Initial conditions :-

$$x(t_0) = d, \quad \left. \frac{dx}{dt} \right|_{t=t_0} = f \rightarrow (4)$$

Initial value problem :- (2) & (4)

$$k_1 e^{\alpha_1 t_0} + k_2 e^{\alpha_2 t_0} - \frac{c}{b} = d \rightarrow (5)$$

$$k_1 \alpha_1 e^{\alpha_1 t_0} + k_2 \alpha_2 e^{\alpha_2 t_0} - \frac{c}{b} f \rightarrow (6)$$

Suppose $\alpha_1 \neq \alpha_2$

If $a^2 - 4b > 0$ then α_1, α_2 are real

If $a^2 - 4b < 0$ then α_1, α_2 are complex conjugate

Let $\alpha_1, \alpha_2 = u + jv$, where u, v are real

$$\alpha_2 = u - jv \quad (j = +\sqrt{-1})$$

(54) & (55)

$$K_1 e^{(u+jv)t} + K_2 e^{(u-jv)t} - \frac{c}{b} = d$$

17-04-23

Now,

for

$$\frac{d^2x}{dt^2} + a \frac{dx}{dt} + bx + c = 0$$

$$\left\{ \begin{array}{l} a^2 - 4bc < 0 \\ \end{array} \right.$$

$K_1 e^{\alpha_1 t} + K_2 e^{\alpha_2 t} - \frac{c}{b}$ satisfies the equation. Here α_1, α_2 are complex conjugate. \rightarrow (1)

Qs there a real $x(t)$ that satisfies the above equation?

let $K_1 = l_1 + jl_2$, $K_2 = l_3 + jl_4$ where l_1, l_2, l_3, l_4 are real.

Now, substitute Substitute in eq (1)

and imaginary part after substitution is

$$(l_1 - l_3) e^{ut} \sin(vt) + (l_2 + l_4) e^{ut} \cos(vt)$$

Make $l_1 = l_3$ and $l_2 = -l_4$

i.e k_1 & k_2 are complex conjugate of each other.

Then solution is $\operatorname{Re} [K_1 e^{\alpha_1 t} + K_2 e^{\alpha_2 t} - \frac{c}{b}]$

$$= l_1 e^{ut} \cos(vt) - l_2 \sin(vt) + l_1 e^{ut} \cos(vt)$$

$$- l_2 e^{ut} \sin(vt) - \frac{c}{b}$$

$$= 2l_1 e^{ut} \cos(vt) - 2l_2 e^{ut} \sin(vt) - \frac{c}{b}$$

$$= C_1 e^{ut} \cos(vt) + C_2 e^{ut} \sin(vt) - \frac{c}{b}$$

Now,

if $a^2 - 4b = 0$

$$\frac{d^2y}{dt^2} + g \frac{dy}{dt} + hy = 0$$

$$a^2 + g\alpha + h = 0$$

roots are $\frac{-g \pm \sqrt{g^2 - 4h}}{2}$

$$g^2 - 4h = 0$$

roots are $\frac{-g}{2}, \frac{-g}{2} = \frac{V}{R}$

$$\alpha = -g/2$$



$k_1 e^{\alpha t}$ satisfies ①.

$\alpha < 0$



and $k_2 t e^{\alpha t}$ ← does this satisfy ①?

[Yes].

So $k_1 e^{\alpha t} + k_2 t e^{\alpha t}$ is also solution.

so for $\frac{d^2x}{dt^2} + a \frac{dx}{dt} + bx + c = 0 \rightarrow ②$

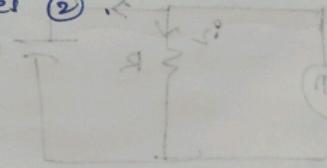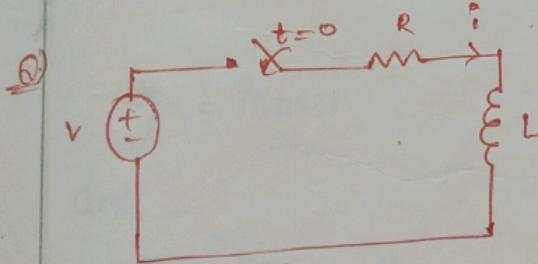$k_1 e^{\alpha t} + k_2 t e^{\alpha t} - \frac{c}{b}$ satisfies ②



Find $i(t)$ at $t > 0$.

$$V = iR + L \frac{di}{dt} = R \left(\frac{\sin \theta}{\theta} \right)$$


$$V - iR = L \frac{di}{dt} \Rightarrow -\frac{Rdt}{L} = -\frac{di}{V - iR} \Rightarrow -\frac{Rt}{L} = \ln |V - iR|$$

$$e^{-\frac{Rt}{L}} = 1 - \frac{iR}{V} \Rightarrow i = (1 - e^{-\frac{Rt}{L}}) \frac{V}{R}$$


$$Q_0 \quad i(t) = \frac{V}{R} \left(1 - e^{-\frac{Rt}{L}} \right)$$

Note: $\frac{L}{R}$ has dimension of time.

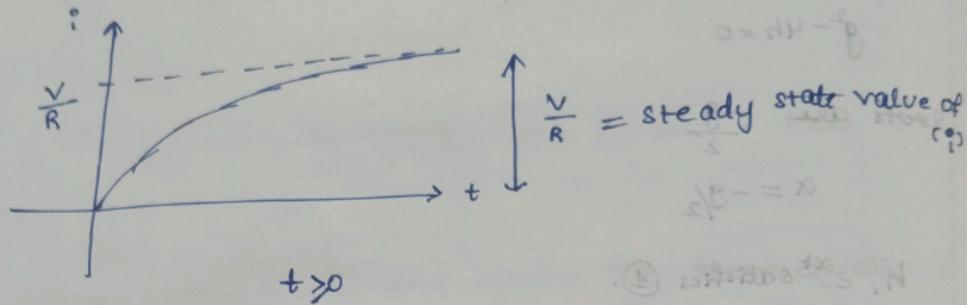$\frac{L}{R}$ is time constant of given circuit.




6)

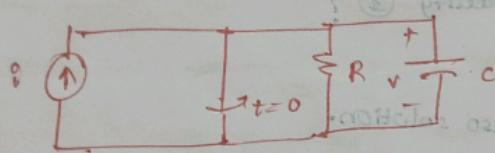

Find $v(t)$ at $t > 0$.

for $t > 0$

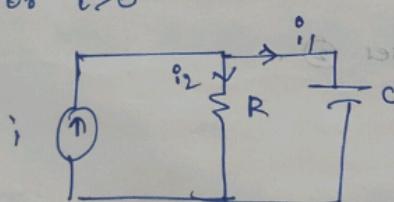

$$\Rightarrow i_2 R = \frac{\int i_1 dt}{C}$$

$$\Rightarrow \boxed{\left(\frac{di_2}{dt} \right) R = \frac{i_1}{C}}$$

$$\Rightarrow \boxed{i_2 + \frac{1}{RC} \frac{di_2}{dt} = i_1}$$

$$RC \frac{di_2}{dt} = i - i_2$$

$$-\frac{di_2}{i - i_2} = -\frac{dt}{RC}$$

$$\left(\ln(i - i_2) \right)_{i_0}^{i_f} = -\frac{t}{RC}$$

and


$$i = \frac{V}{R} + C \frac{dv}{dt}$$

$$\frac{dv}{dt} + \frac{V}{RC} - \frac{i}{C} = 0$$

$$\text{and } v(0) = 0$$

$$v(t) = iR - iR e^{-t/RC}$$

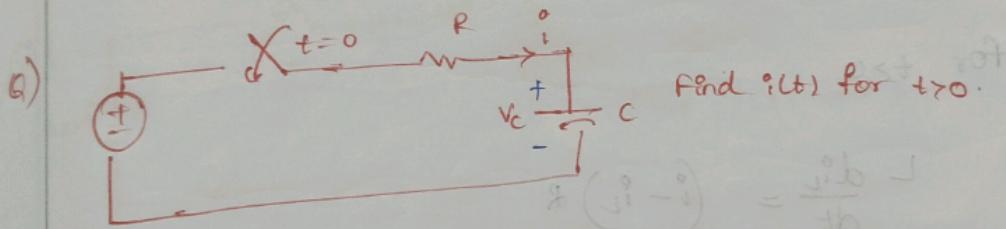here RC is the time constant of the circuit.



$$\frac{V}{R} = i_{\text{initial}}$$

and

$$V = iR + \frac{q}{C}$$

$$V = \frac{dq}{dt}$$


$$\Rightarrow -\frac{t}{RC} = \ln \left(\frac{i_0}{V/R} \right) \quad \left[\frac{-di}{i} = \frac{dt}{RC} \right]$$

$$(i_0 - i) R = \frac{q}{C}$$

$$\Rightarrow 0 - R \frac{di}{dt} = \frac{i}{C}$$


$$\frac{V}{R} e^{-\frac{t}{RC}} = i_f$$

time const
of circuit.

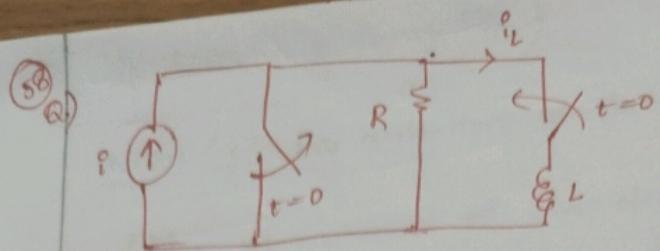

Find i_L as $f(t)$ for $t > 0$.

for $t < 0$

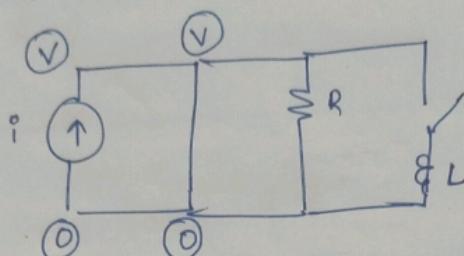

& hence

$$i_L(0^-) = 0$$

for $t > 0$

~~initially $i_L(0) = 0$~~

$$-i_R - i_L = (t) V$$

$$L \frac{di_L}{dt} = (i - i_L) R$$

$$L \frac{di_L}{dt} = R(i - i_L)$$

$$-(\frac{d(i_L)}{i - i_L}) = -\frac{R}{L} dt$$

$$\ln \left(\frac{|i - i_L|}{i_L} \right) = -\frac{Rt}{L}$$

$$e^{-\frac{Rt}{L}} = \frac{|i - i_L|}{i_L}$$

$$59) |i - i_L| = |i| e^{-Rt/L}$$

$$\therefore i(1 - e^{-Rt/L}) = i(t)$$

Solution of the differential equation:-

$x(t) \leftarrow \text{solution}$

Steady state value of $x(t) = \lim_{t \rightarrow \infty} x(t)$


$x(t) = \text{transient expression} + \text{steady state expression.}$

In steady state, all derivatives are zero.

$$\frac{dx}{dt} + ax + b = 0. \quad \text{In steady state} \quad x = \frac{-b}{a}$$

$$\frac{d^2x}{dt^2} + a \frac{dx}{dt} + bx + c = 0$$
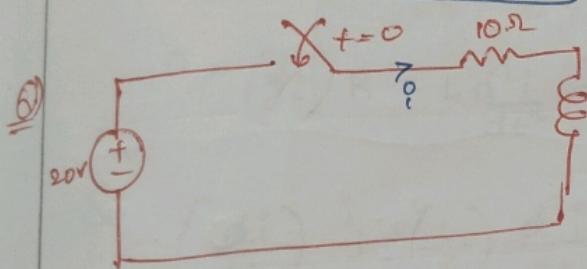
$$\text{In steady state} \quad x = \frac{-c}{b}$$



Find $i(t)$ for $t > 0$.

$$V_A - 10i - \frac{L di}{dt} = V_B$$

$$20 = 10i + 5 \frac{di}{dt}$$

$$4 = 2i + \frac{di}{dt}$$


$$\text{and } i(0) = 0$$

$$\frac{di}{dt} = 4 - 2i \Rightarrow \frac{-2 di}{4 - 2i} = -2 dt$$

$$\ln \left| \frac{4 - 2i}{2} \right| = -2t$$

$$2 - 2e^{-2t} = i$$

$$2(1 - e^{-2t}) = i$$

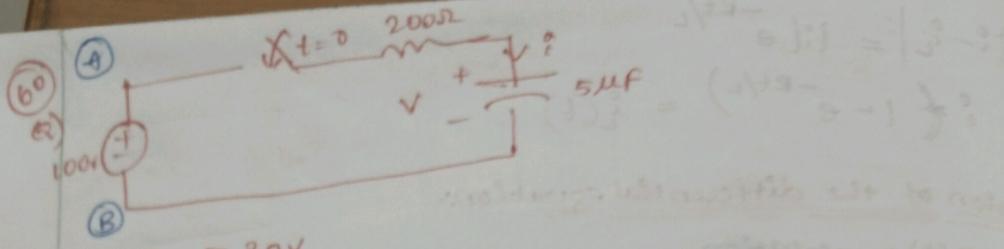

$$V(0) = 30V$$

$i(t) = ?$ for $t > 0$, also find $V(t)$ for $t > 0$.

$$V_A - 200i - V = V_B$$

$$100 = 200i + V$$

$$0 = 200 \frac{di}{dt} + \frac{i}{5 \times 10^6} \quad (100 = 200i_0 + 30)$$

$$0 = 2 \frac{di}{dt} + \frac{i}{5 \times 10^4} \quad \left(\frac{7}{20} = i_0 \right)$$

$$0 = 2 \frac{di}{dt} + i(2 \times 10^3)$$

$$\frac{di}{dt} = -1000i$$

$$\left[\ln(i) \right]_{\frac{7}{20}}^{i(t)} = -1000t$$

$$\Rightarrow \boxed{\frac{7}{20} e^{-1000t} \text{ Amp} = i(t)}$$

$$\frac{dv}{dt} = \frac{i}{C}$$

$$\frac{dv}{dt} = \frac{7}{20 \times 5 \times 10^6} e^{-1000t}$$

$$V - 30 = \frac{7}{10^4} \left(\frac{e^{-1000t}}{-1000} \right)_0^t$$


(61)

$$V - 30 = (-2 \times 10^4) \left(\frac{e^{-1000t}}{1000} - \frac{1}{1000} \right)$$

$$V - 30 = +70 \left(1 - e^{-1000t} \right)$$

$$V = 100 - 70 e^{-1000t} \text{ Volts.}$$

Q:

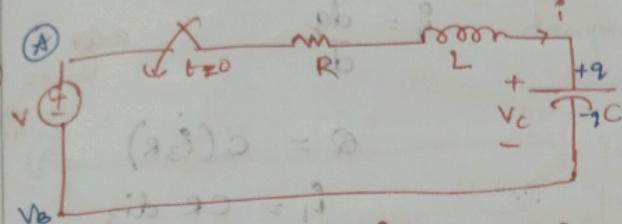

Find the expression for $i(t)$ for $t > 0$.

Sol:

$$V_A - iR - L \frac{di}{dt} - \frac{q}{C} = V_B$$

$$V = iR + L \frac{di}{dt} + \frac{q}{C}$$

$$0 = \left(\frac{di}{dt} \right) R + L \frac{d^2i}{dt^2} + \frac{i}{C}$$

$$\text{So } \left(\frac{di}{dt} \right) + \left(\frac{L}{R} \right) \frac{d^2i}{dt^2} + \frac{i}{RC} = 0$$


$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0 \quad (1)$$

$$i(0^+) = 0$$

$$\text{and } V_A - \left(\frac{di}{dt} \right)_{at t=0} - V_C(0) = V_B$$

$$V = V_C(0) + \left(\frac{di}{dt} \right)_{at t=0}$$
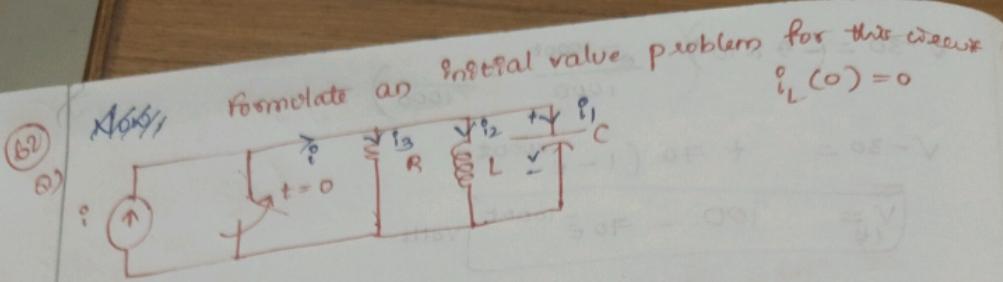
$$\frac{V - V_C(0)}{L} = i'(0) \text{ and } i(0) = 0$$



Sol:

At $t > 0$

$$i = i_1 + i_2 + i_3$$

$$i_3 R = L \frac{di_2}{dt} = \frac{q}{C}$$

$$i = RC \frac{d^2 i_2}{dt^2} + i_2 + i_3$$

$$i = (RC) \left(\frac{L}{R} \right) \frac{d^2 i_2}{dt^2} + i_2 + \frac{L}{R} \frac{di_2}{dt}$$

$$i = LC \frac{d^2 i_2}{dt^2} + \frac{L}{R} \frac{di_2}{dt} + i_2$$

So

$$\boxed{\frac{d^2 i_2}{dt^2} + \frac{1}{RLC} \frac{di_2}{dt} + \frac{i_2 - i}{LC} = 0}$$

$$\text{Now, } i_2(0^+) = 0$$

$$i_2'(0^+) = \frac{\sqrt{at}}{L} = 0 \quad (\text{as } i_L(0) = 0)$$


and other form is,

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = 0$$

$$V(0) = 0, \quad \frac{dV}{dt} \Big|_{t=0^+} = \frac{i}{C}$$

NOTE:

Roots
Roots
Roots

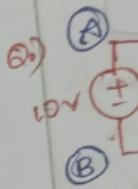

Find i_L

V_A

10

0


So

$\frac{dV}{dt} = 0$

NOTE:

- Roots are real & distinct \rightarrow Overdamped response
 Roots are complex conjugate \rightarrow Undeveloped circuit
 Roots are equal & real. \rightarrow Underdeveloped response

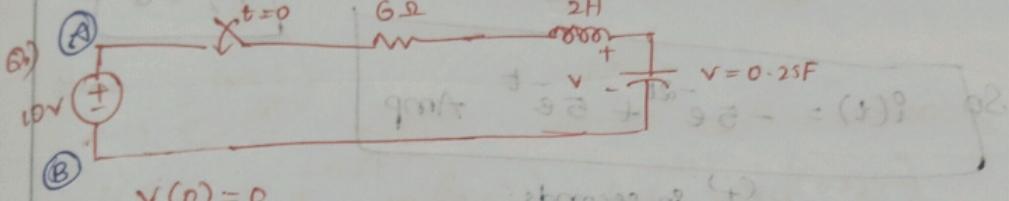$2 + j\omega + j\zeta\omega = 1 \Rightarrow \omega = 1$
 $\zeta = 1 \Rightarrow$ Critically damped & Critically damped response.



$$V(0) = 0$$

Find $i(t)$ for $t > 0$


$$V_A - 6i - 2\frac{di}{dt} - v = V_B$$

$$10 = 6i + 2\frac{di}{dt} + v$$

$$0 = 6\frac{di}{dt} + 2\frac{d^2i}{dt^2} + 4i$$

$$Q = 0.25V$$

$$i = \frac{dv}{(dt)(4)}$$

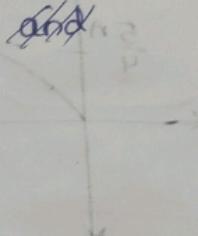

$$(i) So, \frac{d^2i}{dt^2} + 3\frac{di}{dt} + 2i = 0$$

$$y^2 + 3y + 2 = 0$$

$$-3 \pm \sqrt{9-8} = -3 \pm 1 = -2, -1$$

So it is overdamped circuit

$$i(t) = k_1 e^{-2t} + k_2 e^{-t}$$

$$\text{and } i(0) = 0 \Rightarrow$$

$$k_1 + k_2 = 0$$

$$64) \quad iD = 6i + 2 \frac{di}{dt}$$

$$5 = \left(\frac{di}{dt} \right)_{t=0}$$



and

$$K_1(-2) + K_2(-1) = 5 \Rightarrow -2K_1 + K_1 = 5$$

$$K_1 = -5 \quad K_2 = 5$$

$$\text{So } i(t) = -5e^{-2t} + 5e^{-t} \text{ Amp}$$

t in seconds.

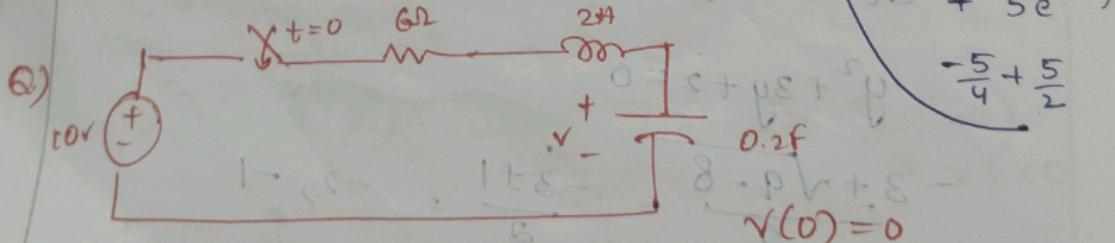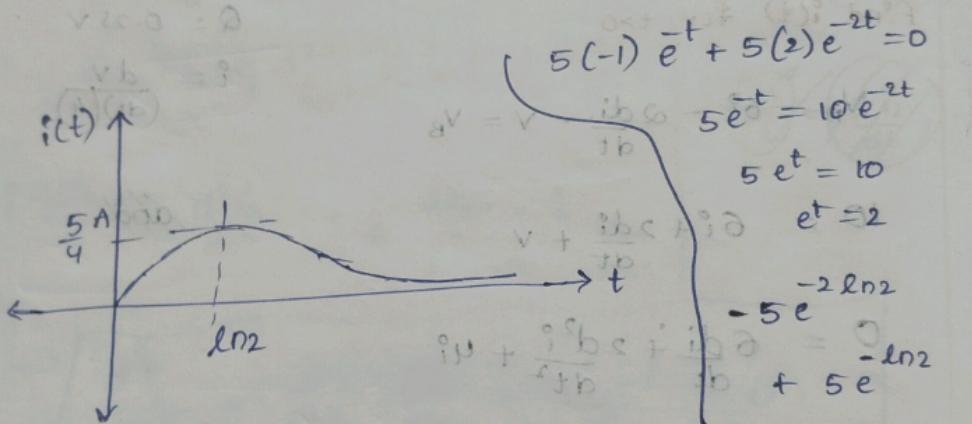

$$10 = 6i + 2 \frac{di}{dt} + v \quad \text{beginning } i = (0.2) \frac{dv}{dt}$$

$$0 = 6 \frac{di}{dt} + 2 \frac{d^2i}{dt^2} + 5v + 0.2 \frac{dv}{dt} \quad \text{beginning } i = (0)$$

$$65) \quad \frac{d^2i}{dt^2} + 3v^2 + 3$$

$$-3 +$$

$$3$$

$$80$$

$$B_T$$

$$i(0) = 2 \frac{d}{dt}$$

$$80$$

$$68 \quad \frac{d^2i}{dt^2} + \frac{3di}{dt} + \frac{5}{2}i = 0$$

$$y^2 + 3y + \frac{5}{2} = 0$$

$$\frac{-3 \pm \sqrt{9 - 10}}{2}$$

$$\frac{3 \pm i}{2}$$

It is undamped situation.

$$80 \quad \begin{array}{l} -(-2+i) \\ B_1 e^{-2t} \end{array}$$

$$i(t) = \frac{P_0}{R} + \frac{B_2 e^{-2t}}{R} + \frac{B_3 e^{-2t}}{R}$$

$$i(t) = c_1 e^{-1.5t} \cos(0.5t) + c_2 e^{-1.5t} \sin(0.5t)$$

$$i(0) = 0$$

$$* \frac{di}{dt} \Big|_{t=0^+} = ⑤$$

$$c_2(0.5)$$

$$80 \quad c_1(-1.5) + c_2(-1.5) = 5$$

$$\cancel{c_1 + c_2} \quad \boxed{c_1 = 0}$$

$$\boxed{c_2 = 10}$$

So,


$$10 e^{-1.5t} \sin(0.5t) A = i(t)$$

$$10 e^{-1.5t} (0.5) \cos(0.5t)$$


$$10(0.5) \cancel{\sin(0.5t)}$$

$$+ 10 \sin(0.5t)(-1.5)e^{-1.5t}$$
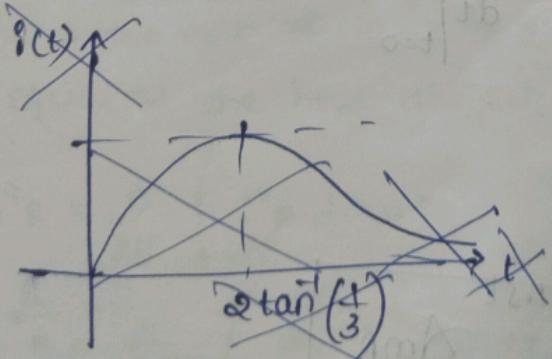
$$0.5 \cos(0.5t) 3 \\ = 1.5 \sin(0.5t) \\ \tan(\frac{\pi}{2}) = \frac{Y}{3}$$



66

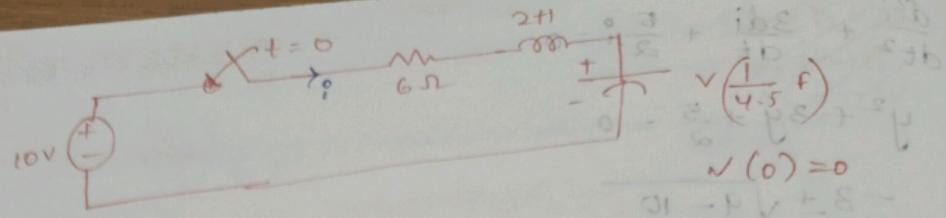

$$6i + \frac{2di}{dt} + \frac{9}{4}i = 10$$

$$6\frac{di}{dt} + \frac{2d^2i}{dt^2} + \frac{9}{4}i = 0$$

$$\frac{d^2i}{dt^2} + \frac{3}{2}\frac{di}{dt} + \frac{9}{4}i = 0$$

$$y^2 + 3y + \frac{9}{4} = 0 \Rightarrow (y+3)(y+\frac{1}{2}) = 0 \Rightarrow y_1 = -3, y_2 = -\frac{1}{2}$$

$$\frac{-3 \pm \sqrt{9-9}}{2}$$

$$\frac{-3}{2} = y$$

and hence

$$i = \frac{-3}{2}t$$

$$i(t) = (A + Bt)e^{\frac{-3}{2}t}$$

$$i(0) = 0$$

$$A = 0$$

$$(f) i(0) \& i'(0) = 0 \Rightarrow \frac{d}{dt}(A + Bt)e^{\frac{-3}{2}t} \Big|_{t=0} = 0 \Rightarrow B = 0$$


$$(t=0) \& (z=0)$$

$$\frac{di}{dt} \Big|_{t=0} = 5$$

$$B = 5$$

$$B = 5$$

$$i(t) = 5t e^{-1.5t} \text{ Amp}$$

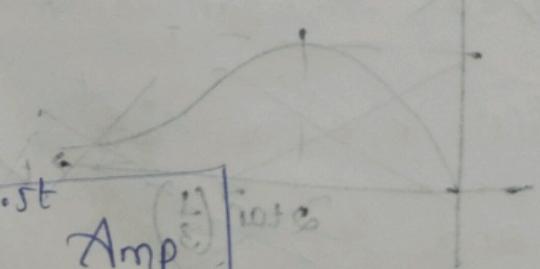

6.1 AC circuits :- All voltages & all currents vary sinusoidally with time.

$$I_m \sin(\omega t + \phi) = i$$

(where i is a periodic function) solve w.r.t t $\rightarrow \frac{d^2}{dt^2}$

here I_m, ω, ϕ are real constants

I_m : max or peak value of i RMS based

ω : angular frequency in rad/s

$$\omega = 2\pi f \text{ where } f \text{ is frequency in Hz}$$

ϕ = phase angle.

$$\frac{m^2}{s^2} = \Omega$$

* $\Rightarrow i_D$ (DC current)

i_D : rated current

R : resistance

$$\text{power} = i_D^2 R$$

\Rightarrow A conductor is designed to carry i_D based on amount of heat dissipated.

Now,

$$i = I_m \sin(\omega t + \phi)$$

Average heat dissipated,

Q) If this conductor is required to carry AC current $i = I_m \sin(\omega t + \phi)$ What is the value of I_m such that the average heat dissipated is equal to the heat dissipated due to flow of current i_D ?

$$i_D^2 R = \frac{1}{2\pi} \int_0^{2\pi} i^2 R d(\omega t)$$

$$i_D^2 R = \frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2(\omega t + \phi) R d(\omega t)$$

(66)


$$\Omega_m = \sqrt{2} i_0$$

$\frac{\Omega_m}{\sqrt{2}}$ ← RMS value (root mean square value)

denoted by \bar{I} (i.e. go substituting in ωm^2)

$$\frac{\Omega_m}{\sqrt{2}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 d(\omega t)}$$
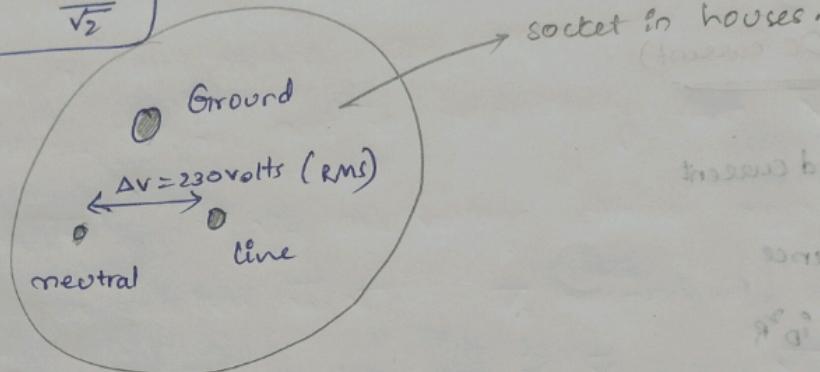
$$\boxed{\bar{I} = \frac{\Omega_m}{\sqrt{2}}}$$



$$v^{\theta} = \sqrt{2} V \sin(\omega t + \phi)$$

RMS value of the instantaneous voltage.

⇒ A sinusoidally varying quantity is called phasor. $\bar{I} = ?$

* Phasor representation using a complex number:

$$\text{phasor } v \rightarrow \sqrt{V} e^{j\phi} = V e^{j\phi} = \overline{V} \angle \phi$$

Polar form.

$$\sqrt{V} e^{j\phi} = V \cos \phi + j V \sin \phi \quad (\text{rectangular form})$$

$$\Rightarrow v = \Omega_m (\sqrt{2} V (\cos \omega t + j \sin \omega t))$$

(69)

$$\begin{aligned} \bar{V}_1 &= ? \\ \bar{V}_2 &= ? \end{aligned}$$

let
let
let

Q. 1
what?

$$\bar{V} (\sqrt{V^2 + V^2}) \sqrt{2}$$

⇒
⇒
⇒

measured below: 0°

oscilloscope: 0°

$$V^2 = 180^2$$

0°

69

$$\mathcal{V}_1 = \sqrt{2} V_1 \sin(\omega t + \phi_1)$$

$$\mathcal{V}_2 = \sqrt{2} V_2 \sin(\omega t + \phi_2)$$

$$\text{let } \bar{\mathcal{V}}_1 = V_1 \angle \phi_1, \bar{\mathcal{V}}_2 = V_2 \angle \phi_2$$

$$\text{let } \mathcal{V} = \mathcal{V}_1 + \mathcal{V}_2$$

Q9 Is \mathcal{V} is a phasor? If so, what is the RMS value of \mathcal{V} and what is the phase angle of \mathcal{V} ?

$$\frac{\sqrt{2} V_1 \sin(\omega t + \phi_1)}{\sqrt{V_1^2 + V_2^2}} + \frac{\sqrt{2} V_2 \sin(\omega t + \phi_2)}{\sqrt{V_1^2 + V_2^2}} = \mathcal{V}$$


$$\Rightarrow \sqrt{2} \left(\sqrt{V_1^2 + V_2^2} \right) \left[\sin(\omega t + \phi_1 + \phi) \right] = \mathcal{V}$$

$$\Rightarrow \tan \phi = \frac{V_1}{V_2}$$

$$\Rightarrow \mathcal{V} = \sqrt{2} V_1 \sin(\omega t + \phi_1) + \sqrt{2} V_2 \sin(\omega t + \phi_2)$$

$$\mathcal{V} = \sqrt{2} \left[V_1 \sin \omega t \cos \phi_1 + V_1 \cos \omega t \sin \phi_1 + V_2 \sin \omega t \cos \phi_2 + V_2 \cos \omega t \sin \phi_2 \right]$$

(or)

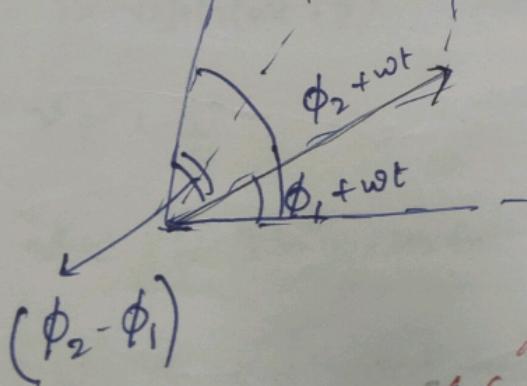

~~magnitude = $\sqrt{V_1^2 + V_2^2 + 2V_1 V_2 \cos(\phi_2 - \phi_1)}$~~

~~(So) $\frac{V}{\sqrt{V_1^2 + V_2^2 + 2V_1 V_2 \cos(\phi_2 - \phi_1)}} = \frac{V}{R}$~~

so,

$$\frac{V}{R} = \text{RMS value} \cdot (\phi_2 - \phi_1)$$

$$\text{phasor } V = \sqrt{V_1^2 + V_2^2 + 2V_1V_2 \cos(\phi_2 - \phi_1)} \quad (10) \quad \sin(\omega t + \phi_1 + \omega t + \phi_2)$$

$$\text{phasor } V = \sqrt{V_1^2 + V_2^2 + 2V_1V_2 \cos(\phi_2 - \phi_1)} \quad \sin(\omega t + \phi_2 - \text{phase angle})$$



$$\text{phase angle} = \tan^{-1} \left(\frac{V_1 \cos(\omega t + \phi_1) + V_2 \cos(\omega t + \phi_2)}{V_1 \sin(\omega t + \phi_1) + V_2 \sin(\omega t + \phi_2)} \right)$$

$V = \sqrt{(V_1 + iV_2)^2} = \sqrt{V_1^2 + V_2^2}$ is a phasor.

- * If V_1 & V_2 are phasors then $V_1 + V_2$ are represented by complex numbers \bar{V}_1 , \bar{V}_2 and \bar{V} respectively then $\bar{V} = \bar{V}_1 + \bar{V}_2$
- * If v_1, v_2, \dots, v_n are voltage phasors represented by complex numbers $\bar{v}_1, \bar{v}_2, \dots, \bar{v}_n$ respectively and if v_1, v_2, \dots, v_n satisfy KVL then $\bar{v}_1, \bar{v}_2, \dots, \bar{v}_n$ also satisfy KVL: $(\omega + j\omega)v_1 + (\omega + j\omega)v_2 + \dots + (\omega + j\omega)v_n = 0$

If i_1, i_2, \dots, i_n are current phasors represented by complex numbers $\bar{i}_1, \bar{i}_2, \dots, \bar{i}_n$ respectively and i_1, i_2, \dots, i_n satisfy KCL then $\bar{i}_1, \bar{i}_2, \dots, \bar{i}_n$ also satisfy KCL.

Resistance:

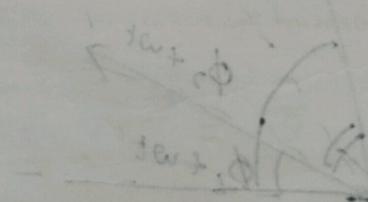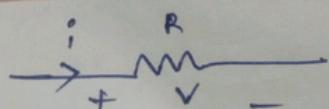

$$V = \sqrt{2} V \sin(\omega t + \phi)$$

$$i = \frac{V}{R} = \sqrt{2} \frac{V}{R} \sin(\omega t + \phi)$$

$$= \sqrt{2} I \sin(\omega t + \phi) \quad \text{where } I = \frac{V}{R}$$


$$v \rightarrow \sqrt{L}\phi = \bar{V}$$

$$i \rightarrow I_L\phi = \bar{I}$$


$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{V}}{\bar{I}} = R$$

and because $R_1 L \theta_1, R_2 L \theta_2 = R_1 R_2 L \theta_1 + \theta_2$

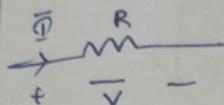
$$\frac{R_1 L \theta_1}{R_2 L \theta_2} = \frac{R_1}{R_2} (\theta_1 - \theta_2)$$



phasor diagram:

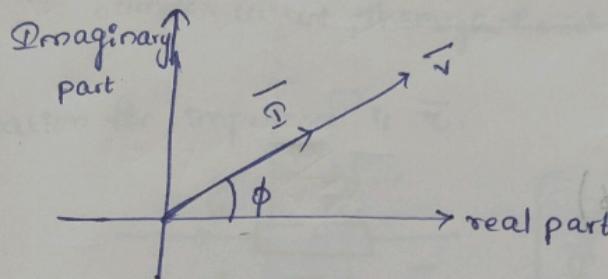

* Inductance:

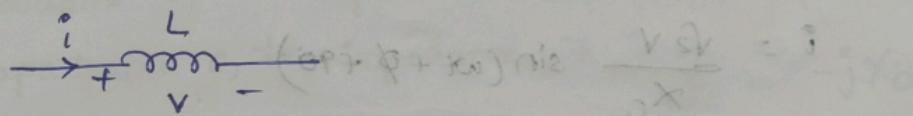

$$\text{let } i = \sqrt{2} I \sin(\omega t + \phi)$$


$$v = L \frac{di}{dt}$$

$$v = L (\sqrt{2} I) (\omega) \cos(\omega t + \phi) = \sqrt{2} (I \omega L) \sin(\omega t + \frac{\pi}{2} + \phi)$$

So $\boxed{V = \Phi \omega L}$ and hence, $V = \Phi X_L$

and here $X_L = \omega L$ (inductive reactance)
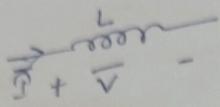
$$\textcircled{2} \quad \frac{\bar{V}}{\bar{I}} = \frac{V}{I} \mid L 90^\circ = X_L \mid 90^\circ = jX_L$$



phasor diagram




$$j - 10 - 10 \mid \frac{10}{j} = \frac{10}{j}$$

$$\bar{V} = \phi \bar{V} \leftarrow v$$

$$\bar{I} = \phi \bar{I} \leftarrow ?$$

$$\textcircled{3} \quad \frac{V}{I} = \frac{V}{\bar{I}} = \frac{V}{I}$$


phasor diag

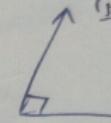

* Impedance

Impedance

* Capacitance:

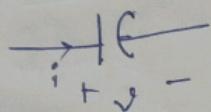


$$\text{let } v = \sqrt{2} V \sin(\omega t + \phi)$$

$$\text{then } i = C \frac{dv}{dt}$$

$$i = C \sqrt{2} V \omega \cos(\omega t + \phi)$$

$$i = \frac{\sqrt{2} V}{X_C} \sin(\omega t + \phi + 90^\circ)$$
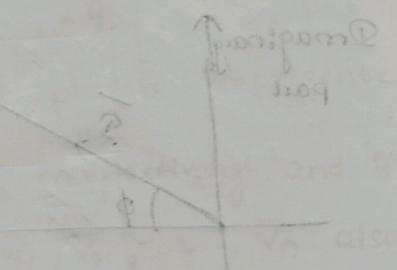
$$\text{where } X_C = \frac{1}{\omega C}$$



X_C is capacitive reactance

$$i = \sqrt{2} I \sin(\omega t + \phi + 90^\circ)$$

$$\text{where } \frac{I}{X_C} = \frac{V}{\omega C}$$

$$\text{so } \frac{V}{I} = X_C \text{ and } \frac{V}{I} = \frac{1}{\omega C} \Rightarrow X_C \mid -90^\circ \Rightarrow -jX_C$$

$$\omega C = V$$

Note


for

for

for

*

(a) phasor diagram

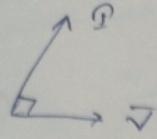

(constant phase)

(constant)

$$X \bar{I} + R \bar{I} = \bar{V}$$


* Impedance:

Impedance of a circuit element (R, L, C)


$$= \left[\frac{\bar{V}}{\bar{I}} \right]$$

= ratio of complex voltage across the circuit element to the complex current through the circuit element.

Notation for impedance is \bar{Z} .

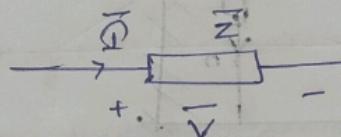
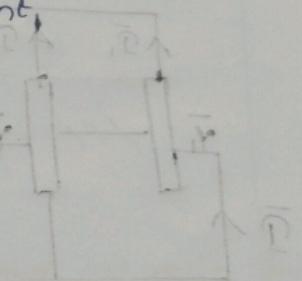
$$\left[\frac{\bar{V}}{\bar{I}} \right] = \bar{Z}$$




for resistance R , the impedance $\bar{Z} = R$

for inductance L , the impedance $\bar{Z} = j\omega L = jX_L$

for capacitance C , the impedance $\bar{Z} = \frac{j}{\omega C} = -jX_C$

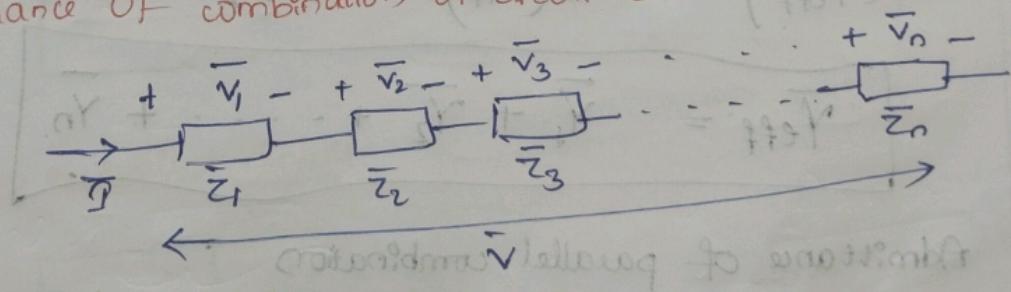* Impedance of combination of circuit elements:



$$\bar{V} = \bar{V}_1 + \bar{V}_2 + \dots + \bar{V}_n =$$

$$\bar{I} \bar{Z}_{\text{eff}} = \bar{I} \bar{Z}_1 + \bar{I} \bar{Z}_2 + \dots + \bar{I} \bar{Z}_n \Rightarrow \bar{I} \bar{Z}_{\text{eff}} = \bar{I} (\bar{Z}_1 + \bar{Z}_2 + \dots + \bar{Z}_n)$$

So $\bar{z} = \xrightarrow{\text{Real part}} R + jX$ (Imaginary part) $\xrightarrow{\text{Reactance}}$
 (notation)

DC circuit
(All voltages
currents a

* Admittances


Admittance = $\frac{1}{\text{Impedance}}$

Notation is \bar{y}

$$\bar{y} = G + jB$$

G: conductance

B: susceptance

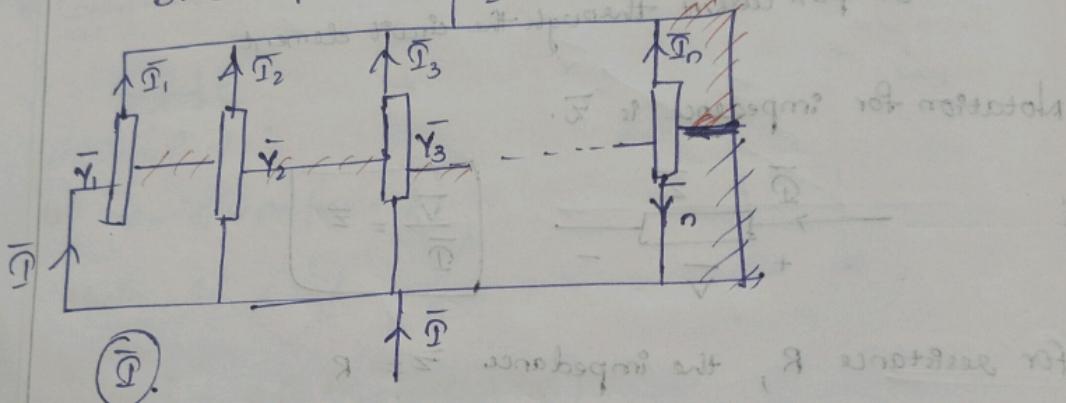

$$\bar{v}(Y_{\text{eff}}) = \bar{v}(Y_1) + \bar{v}(Y_2) + \dots + \bar{v}(Y_n)$$

$$Y_{\text{eff}} = Y_1 + Y_2 + \dots + Y_n$$

Admittance of parallel combination

$$= Y_1 + Y_2 + \dots + Y_n$$

1.

2.

3.

4.

5.

* complex

* Super






AC c

* The

* 18



DC circuit

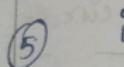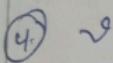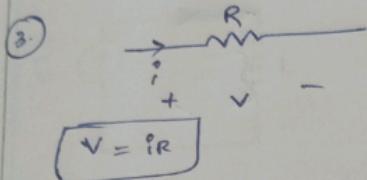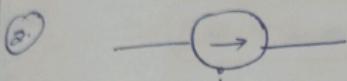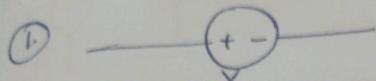(All voltages and all currents are constants)



AC circuit

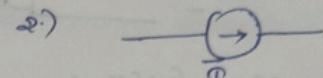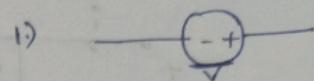(All voltages and all currents are phasors)



$$(A + j\omega) \text{ nA} \sqrt{2} \angle \frac{\pi}{2}$$

$$(V + j\omega) \text{ mV} \sqrt{2} \angle \frac{\pi}{2}$$


$$4) \quad \bar{V}$$

$$5) \quad \bar{I}$$

* complex voltages & currents satisfy KCL, KVL.

* Superposition theorem, Thevenin thm & Norton thm are valid for AC circuits.

* Thevenin equivalent circuit:

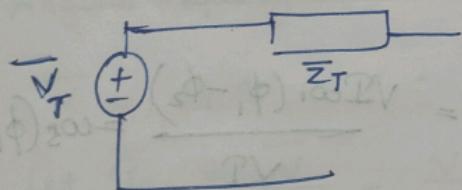


$$PV = 3 \text{ V}$$

$$= 3 \text{ V}$$


$$= 3 \text{ V}$$

$$1 = 3 \text{ V} \geq 0$$

* Norton equivalent circuit:

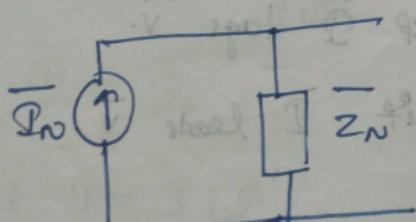

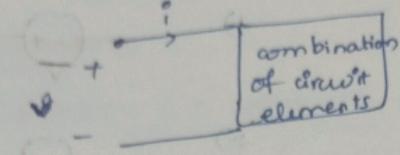26 Let (\bar{V}) be the phasor voltage across a combination of circuit elements, and let (\bar{I}) be the current phasor through this combination of circuit elements.



$$v = \sqrt{2} V \sin(\omega t + \phi_1)$$

$$i = \sqrt{2} I \sin(\omega t + \phi_2)$$

$$v \rightarrow \bar{V} = \sqrt{V} \phi_1$$

$$i \rightarrow \bar{I} = \sqrt{I} \phi_2$$

* Instantaneous power consumed by combination of circuit elements

$$p = v i = \sqrt{2} V \sin(\omega t + \phi_1) \sqrt{2} I \sin(\omega t + \phi_2)$$

$$= \sqrt{I} \cos(\phi_1 - \phi_2) - \sqrt{I} \cos(2\omega t + \phi_1 + \phi_2)$$

$$\text{Average power, } P = \sqrt{I} \cos(\phi_1 - \phi_2)$$

$$\text{Apparent power, } S = \sqrt{I}$$

$$\text{Power factor} = \frac{\text{Average power}}{\text{Apparent power}} = \frac{\sqrt{I} \cos(\phi_1 - \phi_2)}{\sqrt{I}} = \cos(\phi_1 - \phi_2)$$

$0 \leq \text{power factor} \leq 1$

We say "lagging power factor" if \bar{I} lags \bar{V} .


We say "leading power factor" if \bar{I} leads \bar{V} .

U type Powerfactor is 0.9 lag.

U Power factor is 0.8 lead.

ation of
through

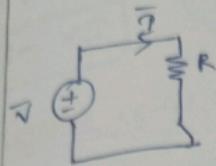
If \bar{I} is in phase with \bar{V} we have "unity power factor".



$$\bar{V} = \sqrt{L}\phi \text{ Then } \bar{I} = \frac{\bar{V}}{R} = \frac{\sqrt{L}\phi}{R} = I L\phi$$

$$\text{where } I = \frac{V}{R}.$$

$$P = V I = S$$

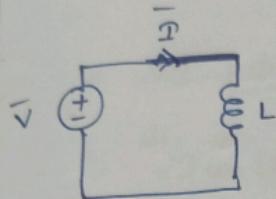

$$V = \sqrt{L}\phi$$


$$\text{Then } \bar{I} = \frac{\bar{V}}{j\omega L} = \frac{\sqrt{L}\phi - 90^\circ}{\omega L} = \bar{I} L\phi - 90^\circ$$

Angular frequency = ω

$$\text{so } P = V I \cos(90^\circ)$$

$$P = 0$$

$$S = V I$$

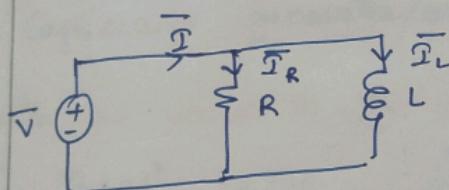

$$\phi = (\text{op-}) \omega D V = 90^\circ$$

$$D V = 2$$

Angular frequency = ω

$$\bar{V} = \sqrt{L}\phi$$

$$\text{Let } \bar{I}_R = \frac{\bar{V}}{R} = \frac{V}{R} L\phi = I_R L\phi$$


$$\bar{I}_L = \frac{\bar{V}}{j\omega L} = \frac{V}{\omega L} L\phi - 90^\circ = I_L L\phi - 90^\circ$$

$$\bar{I} = \bar{I}_R + \bar{I}_L$$

$$\text{Let } \bar{I} = I L\phi' \quad (\text{so } V = I R) \quad \text{op-} \bar{I} \bar{I} = \bar{D}$$

So,


④

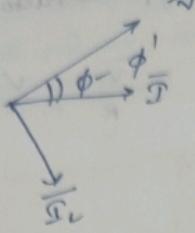

Average power consumed by combination of (R) & L

$$P = \sqrt{I} \cos(\phi - \phi')$$

$$\boxed{P = \sqrt{I_R} V}$$

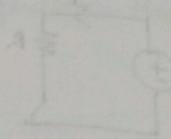


⑤

$$P=0$$

$$S = \sqrt{I}$$

* Complex pe

$$\bar{S} = \bar{I}$$

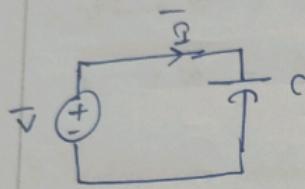

$$\bar{V} = \bar{V} \phi$$



$$\bar{I} = \sqrt{wC} \angle \phi + 90^\circ$$

$$\bar{I} = I \angle \phi + 90^\circ$$

Angular frequency = ω

$$P = \sqrt{I} \cos(-90^\circ) = 0$$

$$\boxed{S = \sqrt{I}}$$

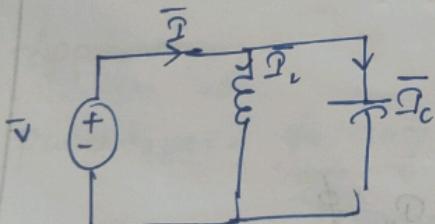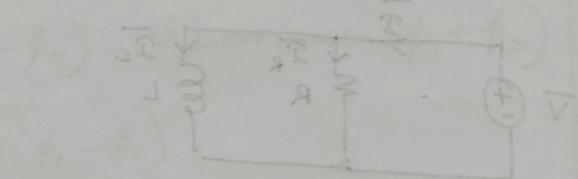

Angular frequency = ω

$$\bar{V} = \sqrt{L} \phi$$

$$\bar{I}_L = I_L \angle \phi - 90^\circ \quad \left(I_L = \frac{V}{\omega L} \right) \quad \bar{I} + \bar{I}_L = \bar{I}$$

$$\bar{I}_C = I_C \angle \phi + 90^\circ \quad \left(I_C = \sqrt{wC} \right) \quad \bar{I} + \bar{I}_C = \bar{I}$$

①

②

$$P=0$$

$$S = \sqrt{P}$$

(L and C have opposite effects on S)

* Complex power consumed by the combination of circuit elements.

$$\bar{S} = \sqrt{\bar{I}}^*$$

(R, L, C → passive circuit elements)


$$= \sqrt{V\phi}, I \angle -\phi_2$$

$$= \sqrt{V} I \angle \phi_1 - \phi_2$$

$$= \sqrt{V} I \cos(\phi_1 - \phi_2) + j \sqrt{V} I \sin(\phi_1 - \phi_2)$$

$$= P + jQ$$

Q is called reactive power.

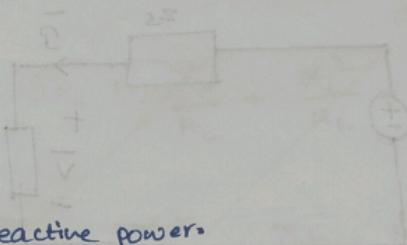

⇒ Inductance consumes/draws reactive power.

⇒ Capacitance generates/supplies reactive power.

* Find the values in the polar form and rectangular form:

$$\textcircled{1} \quad \frac{10 \angle 45^\circ \quad 20 \angle 30^\circ}{35 \angle 75^\circ} = \frac{40}{35} \angle 10^\circ$$

$$= 5.714 \angle 10^\circ$$

and in rectangular form 5.714.


$$\textcircled{2} \quad (0.5 \angle 30^\circ - 0.8 \angle 3.13^\circ) \quad 0.707 \angle -45^\circ$$

$$\Rightarrow (0.5)(0.707) \angle -15^\circ - 0.8(0.707) \angle 3.13^\circ$$

$$\Rightarrow 0.3535 \angle -15^\circ - 0.5656 \angle 18.13^\circ$$

$$\Rightarrow 0.341 + j(-0.914) - 0.56$$


80. Maximum power transfer theorem

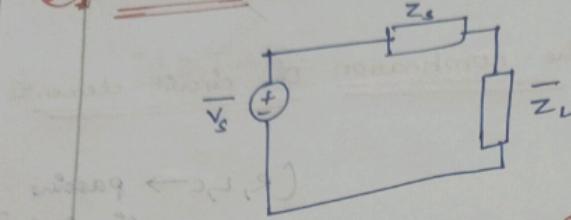

\bar{V}_s and \bar{Z}_s are fixed. (with $\operatorname{Re}(\bar{Z}_s) \neq 0$)

⇒ The value of \bar{Z}_L which maximises the average power transferred to it is \bar{Z}_s^* (conjugate of \bar{Z}_s)

Proof:

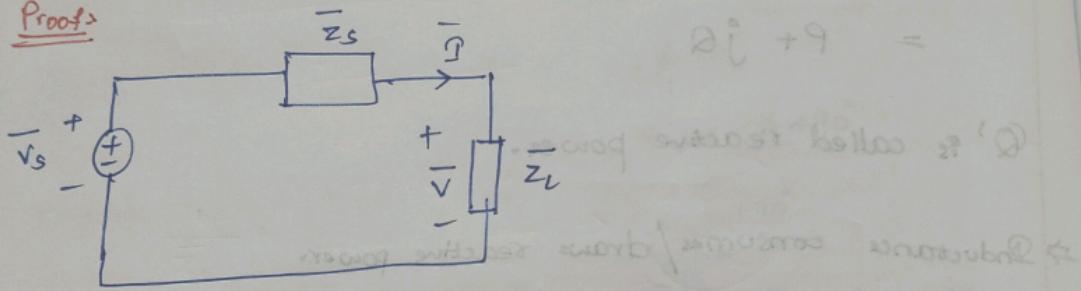

Let $\bar{V}_s = V_s$ $\text{Lo} \leftarrow$ without loss of generality

$$\text{Let } \bar{Z}_s = R_s + jX_s, \bar{Z}_L = R_L + jX_L$$

$$\text{Let } \bar{\varnothing} = \varnothing \text{ Lo}$$

Average power transferred to \bar{Z}_L

$$P = \operatorname{Re}(\bar{V}\bar{I}^*) = \operatorname{Re}(\bar{I}\bar{Z}_L\bar{I}^*)$$

$$= \operatorname{Re}[\bar{I} \angle \varnothing (R_L + jX_L) \bar{I} \angle -\varnothing]$$

$$= \operatorname{Re}[\bar{I}^2 (R_L + jX_L)] = \bar{I}^2 R_L$$

$$\bar{I} = \frac{\bar{V}_s}{\bar{Z}_s + \bar{Z}_L} = \frac{V_s}{R_s + jX_s + R_L + jX_L}$$

$$\textcircled{1} = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$P = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

maximise $\frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$ Practical basis

Here $X_L = -X_s$

as X_L independent on R_L

\uparrow
minimise

$$\frac{(R_s + R_L)^2 + (X_s + X_L)^2}{R_L}$$

\uparrow and hence $(R_s + R_L)^2$ min

\uparrow
minimise
 \uparrow
minimise

$$\frac{R_s^2}{R_L} + R_L + 2R_s + \frac{X_s^2}{R_L} + \frac{X_L^2}{R_L} + 2X_s X_L$$

and

$$\frac{R_s^2}{R_L} + R_L + 2R_s \text{ min}$$


$$\frac{R_s^2}{R_L} + R_L \geq 2\sqrt{R_s^2}$$

$$\frac{R_s^2}{R_L} + R_L \geq 2R_s \quad (\text{min at } R_s^2 = R_L^2 \Rightarrow R_s = R_L)$$

and hence for whole expression to be min,

$$\left. \begin{array}{l} R_s = R_L \\ X_s = -X_L \end{array} \right\} \Rightarrow \boxed{\frac{-\star}{Z_s} = \frac{-\bar{Z}_L}{Z_L}}$$


Hence proved.

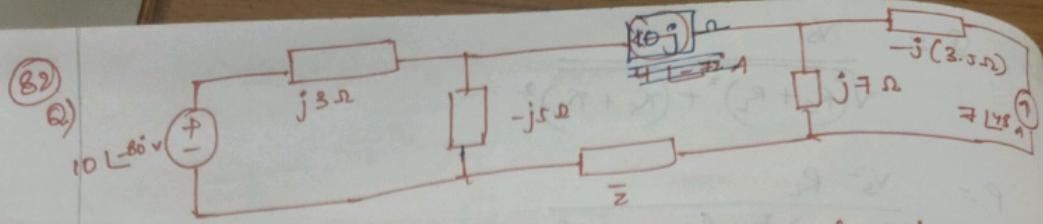

Find \bar{Z} that maximise average power transferred to it.


Hint: Do you need calculator?

Sol.

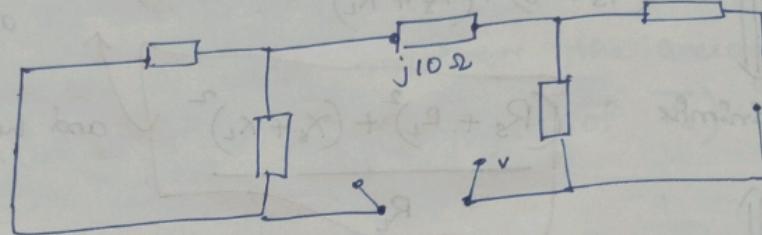

Sol.
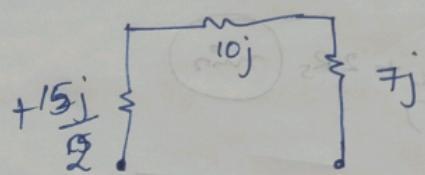
$$\frac{1}{\bar{Z}_1} = \frac{+j}{5} - \frac{j}{3} \Rightarrow \frac{-2j}{15}$$



$$+15j \over 2$$

So, $(17 + 7.5)j \Rightarrow 17j / 2j / 15$

$$\bar{Z} = -(24.5)j \Rightarrow 17 - 6.13j$$

$$17 \over 15 \over 8 \over 15 \over 20 \over 15 \over 15 \over 80 \over 4 \over (0.13)$$

But it is not correct!!!

(We will come to this later)

$$V_1 = 106 \text{ sin}$$


$$V_2 = 13\sqrt{2}$$

$$\theta = -25^\circ$$

$$\text{find } \theta_{RM}$$

$$10 \angle 30^\circ$$

$$\text{Nod}$$

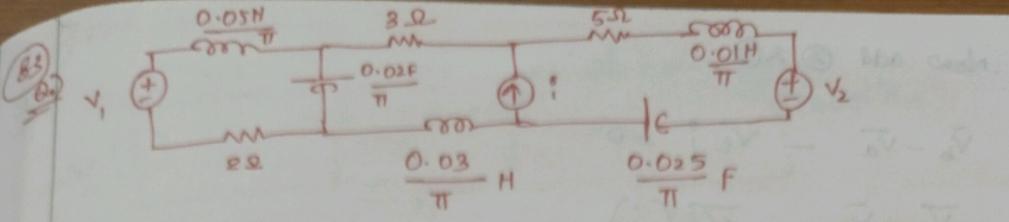


$$v_1 = 10\sqrt{2} \sin(100\pi t + 30^\circ) V$$

$$v_2 = 13\sqrt{2} \cos(100\pi t + 15^\circ) V$$

$$i = -25\sqrt{2} \sin(100\pi t - 80^\circ) A$$

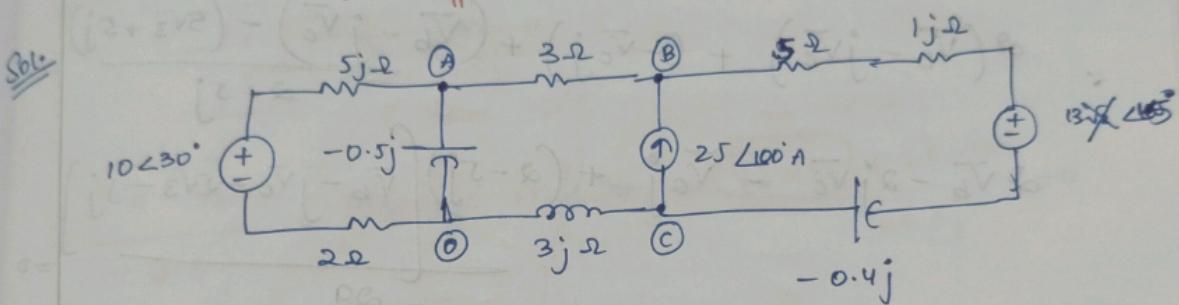find i_{rms} through $\frac{0.02 F}{\pi}$



$$\frac{-j}{\frac{0.02}{\pi}(100\pi)} = \frac{-j}{2}$$

Nodal analysis (at node 'a')

$$\frac{\bar{V}_a}{-0.5j} + \frac{\bar{V}_a - \bar{V}_b}{3j} + \frac{\bar{V}_a - 10\angle 30^\circ}{2+5j} = 0 \quad \text{--- (1)}$$

Nodal analysis (at node 'b')

$$\frac{\bar{V}_b - \bar{V}_a}{3} - 25\angle 100^\circ + \frac{\bar{V}_b - \bar{V}_c - 13\sqrt{2}\angle 15^\circ}{5+0.6j} = 0 \quad \text{--- (2)}$$

Nodal analysis (at node 'c')

$$\frac{\bar{V}_c}{3j} + 25\angle 100^\circ + \frac{\bar{V}_c - \bar{V}_b + 13\sqrt{2}\angle 15^\circ}{5+0.6j} = 0 \quad \text{--- (3)}$$

(84)

Now add ② & ③

$$\bar{V}_b - \bar{V}_a - \bar{V}_c j^{\circ} = 0$$

$$\bar{V}_b - \bar{V}_a = \bar{V}_c (j)$$

$$+ 2\bar{V}_a j + \bar{V}_a - \bar{V}_b + \frac{\bar{V}_a - 10 \angle 30^\circ}{2+5j} = 0 \quad (\text{from eqn ①})$$

$$2(\bar{V}_b - j\bar{V}_c) + (-\bar{V}_c j) + \frac{(\bar{V}_b - j\bar{V}_c) - (5\sqrt{3} + 5j)}{2+5j} = 0$$


$$2\bar{V}_b - 2j\bar{V}_c - \bar{V}_c j + (2-5j) \left[\bar{V}_b - j\bar{V}_c - 5\sqrt{3} - 5j \right] = 0$$

$$\cancel{58\bar{V}_b - 58j\bar{V}_c - 29\bar{V}_c j} + \cancel{2\bar{V}_b - 2j\bar{V}_c - 10\sqrt{3} - 10j} \\ - \cancel{5\bar{V}_b j} - \cancel{5\bar{V}_c} + \cancel{25j\sqrt{3}} - 25 = 0$$

$$(60 - 5j)\bar{V}_b + (-5 - 89j)\bar{V}_c = (25 + 10\sqrt{3}) + (25\sqrt{3} - 10j)$$

Now find \bar{V}_a , \bar{V}_b , \bar{V}_c using calculator.

Q2

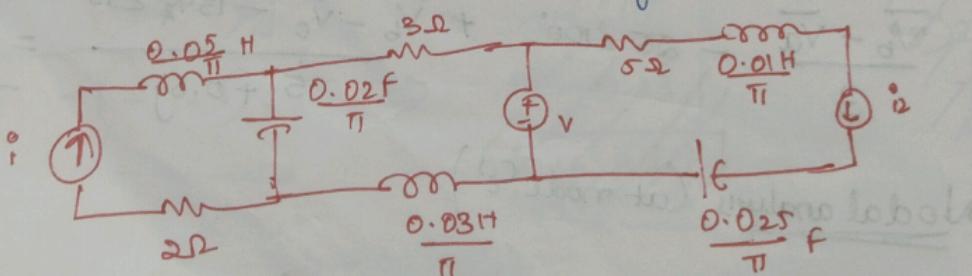


$$i_1 = 10\sqrt{2} \sin(100\pi t + 80^\circ) A$$


$$i_2 = 13\sqrt{2} \cos(100\pi t + 15^\circ) A$$

$$V_{12} = 25\sqrt{2} \sin(100\pi t - 80^\circ) V$$

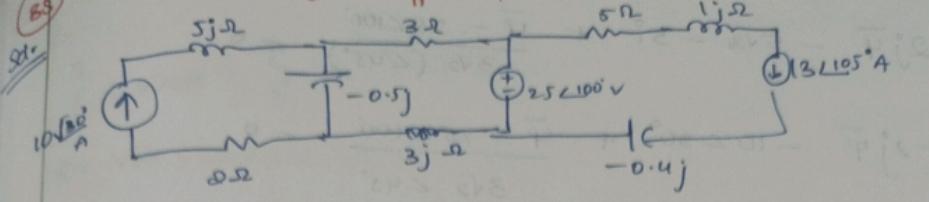BS find items through $\frac{0.02F}{\pi}$ capacitor



It can be charged to

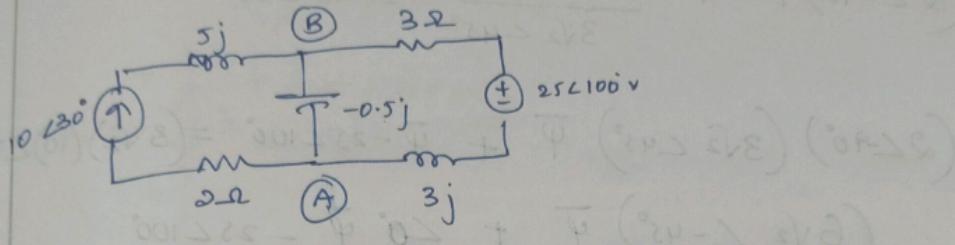

$$\frac{\bar{V}_A - \bar{V}_B}{-0.5j} + 10 \angle 30^\circ + \frac{\bar{V}_A - \bar{V}_B + 2.5 \angle 100^\circ}{3+3j} = 0$$

$$2(\bar{V}_A - \bar{V}_B)j + 10 \angle 30^\circ + \frac{\bar{V}_A - \bar{V}_B + 2.5 \angle 100^\circ}{3+3j} = 0$$

and

$$\frac{\bar{V}_B - \bar{V}_A}{-0.5j} + (-10 \angle 30^\circ) + \frac{\bar{V}_B - \bar{V}_A - 2.5 \angle 100^\circ}{3+3j} = 0$$

$$+ 2j(\bar{V}_B - \bar{V}_A) + (-10 \angle 30^\circ) + \frac{\bar{V}_B - \bar{V}_A - 2.5 \angle 100^\circ}{3+3j} = 0$$

$$\text{Take } \bar{V}_B - \bar{V}_A = \bar{\Psi}$$

$$2j\bar{\Psi} - 10 \left(\frac{\sqrt{3}}{2} + j\frac{1}{2} \right) + \frac{\bar{\Psi} - 2.5 \angle 100^\circ}{3+3j} = 0$$

find $\bar{\Psi}$ and $\left| \bar{\Psi} \right| = \text{P}_{\text{rms}}$ through asked capacitor

(86)

$$2j\bar{\Psi} - 5\sqrt{3} - 5i + \frac{\bar{\Psi} - 25\angle 100^\circ}{3\sqrt{2}\angle 45^\circ} = 0$$

$$-2j\bar{\Psi} - 10\angle 30^\circ + \frac{\bar{\Psi} - 25\angle 100^\circ}{3\sqrt{2}\angle 45^\circ} = 0$$

$$(2\angle -90^\circ)\bar{\Psi} + \frac{\bar{\Psi} - 25\angle 100^\circ}{3\sqrt{2}\angle 45^\circ} = 10\angle 30^\circ$$

$$(2\angle -90^\circ)(3\sqrt{2}\angle 45^\circ)\bar{\Psi} + \bar{\Psi} - 25\angle 100^\circ = (3\sqrt{2})(10)\angle 75^\circ$$

$$(6\sqrt{2}\angle -45^\circ)\bar{\Psi} + 10\angle 30^\circ\bar{\Psi} - 25\angle 100^\circ = 30\sqrt{2}\angle 75^\circ$$

$$\bar{\Psi} = \frac{30\sqrt{2}\angle 75^\circ + 25\angle 100^\circ}{1 + 6\sqrt{2}\angle -45^\circ}$$

$$\bar{\Psi} = -4.083 + 5.871i$$

$$|\bar{\Psi}| = 7.151$$

and hence $\Phi_{rms} = (7.151)(2)$

$$\Phi_{rms} = 14.302 \text{ Amp}$$

* NOTE:

$$S = P + jQ$$

(P) : Average power

(or) Active power

(or) Real power

Q: Reactance

S: Power

P: Volt.

Power factor

Q) A

Sol:

Q: Reactive power

$$S = \text{Watt} \quad \text{and} \quad S = (\bar{V} \times \bar{I}) = VA$$

Q: Volt-ampere-reactive (Var)

power factor = Average power
Apparent power

$$\bar{V} \bar{I} = R + jX = Z \angle \phi$$


$$\begin{aligned} &= \frac{\sqrt{R^2 + X^2}}{\sqrt{R^2 + X^2}} \cos \phi = \frac{(i\omega + \mu)}{(i\omega + \mu)} \frac{(i + s) \omega}{(i\omega - \mu)} \\ &= \frac{R}{\sqrt{R^2 + X^2}} = \frac{V_{\text{rms}}}{(i\omega) s} \end{aligned}$$

Q) A series RL circuit consumes 384 W active power at 0.8 power factor (when connected to 120 V 60 Hz voltage source).

Find R, L .

Sol:

$$P = 384 \text{ W}$$

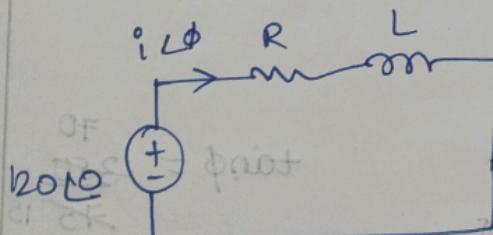

$$P = 120 \bar{I} \cos \phi$$

$$384 = 120 \bar{I} (0.8) \Rightarrow \bar{I} = 4 \text{ Amp}$$

$$i = \frac{V_{\text{rms}}}{Z} \text{ and } i = i \text{ rms}$$

$$P = i^2 R$$

$$384 = 16 \cdot R$$

$$R = 24 \Omega$$

$$\text{and } 0.8 = \frac{R}{\sqrt{R^2 + X^2}}$$

we get X

\therefore we get V

(88) and $P_F \frac{R}{\sqrt{R^2 + X^2}} = 0.8 \angle 0^\circ$

Q) The current through the series combination of two passive circuit elements is $(8 - 10j)$ A and the voltage across the series combination is $(50 + 25j)$ V. What are the circuit elements? Find the pf of the series combination. Find active & reactive powers consumed by series combination.

Sol:

$$\frac{50 + 25j}{8 - 10j} = \underline{Z}$$

R, L, C

$$\frac{25(8 + j)}{2(4 - 5j)} \frac{(4 + 5j)}{(4 + 5j)} = \frac{25(8 + 4j + 10j - 5)}{2(16 + 25)} \\ = \frac{25(3 + 14j)}{2(41)}$$

$$= \frac{25}{82} (3 + 14j)$$

and $R = \frac{25}{82} \Omega = 4.38 \angle 77.905^\circ$

$$\omega L j = \frac{175}{41} j$$

and $\mu_s = 1.88$

$\sqrt{\mu_s} = 1$



$\tan \phi = \frac{75}{82}$

$\tan \phi = \frac{70}{350} = \frac{14}{75} = \frac{14}{3}$

$\cos \phi = \frac{75}{82} = 0.9$

$\sin \phi = \frac{75}{82} = 0.9$

$\mu_s = 1.88$

$\sqrt{\mu_s} = 1$

$\tan \phi = 1$

$\sin \phi = 1$

$\cos \phi = 1$


and $P_f = \cos(7.905^\circ) \approx 0.21$ (lag)
 (Imp to be written)

and $\bar{S} = (\bar{P} + j\bar{Q}) = \bar{V} \bar{I}^* = (50 + 2j)(8 + 10j)$

$$20 + = 150 + 700j$$

$$P = 150 \text{ W}$$

$$Q = 700 \text{ VAR.}$$

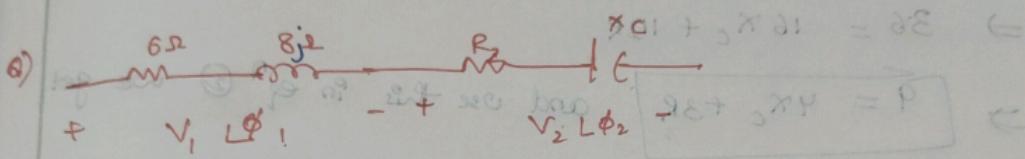

$$V_1 = 3V_2 \quad \& \quad V_1 \angle \phi_1 + V_2 \angle \phi_2 = 240 \angle \phi \text{ V}$$

$$|\phi_1 - \phi_2| = 90^\circ$$

Find R_1, X_C .

Sol. $V_1 = \bar{I} \sqrt{6^2 + B^2}$

$$V_2 = \bar{I} \sqrt{R^2 + X_C^2}$$


$$10 = 3 \sqrt{R^2 + X_C^2}$$

$$\sqrt{V_2^2 + 9V_2^2} = 240$$

$$\sqrt{10} V_2 = 240$$

$$V_2 = 24 \sqrt{10}$$

and

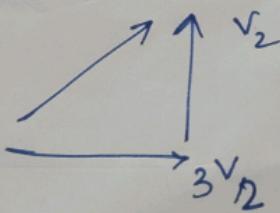

$$V_1 = \frac{B\sqrt{10}}{\sqrt{10}}$$

$$\bar{I} = \frac{72}{\sqrt{10}}$$

$$240 = (\bar{I}) \left(\sqrt{R^2 + (Bj + X_C)^2} \right)$$

$$\text{and } \frac{10 \cdot 240 \sqrt{10}}{72 \sqrt{10}} \Rightarrow \sqrt{R^2 + (Bj + X_C)^2}$$

(90)

$$\frac{100(10)}{9} = (6+R)^2 + (8+X_C)^2 \rightarrow ①$$

$$\Rightarrow \frac{100}{9} = (6+R)^2 + X_C^2 \rightarrow ②$$

$$\Rightarrow \frac{100}{9}(q) = 36 + 12R + 16X_C$$

$$\frac{36}{16} + X_C = \frac{1}{4} + \frac{1}{2}(5)$$

$$\Rightarrow 36 = 16X_C + 12R$$

$$\Rightarrow q = 4X_C + 3R$$

and use this in eqn ② we get

$$X_C & R$$

$$OPE = \sqrt{V_P + V_C}$$

$$OPE = \sqrt{10}$$

$$OPE = \sqrt{10}$$


$$OPE = \sqrt{10}$$

$$\frac{SF}{10} = 1$$

$$\sqrt{V_P + V_C} = V$$

$$\sqrt{V_P + V_C} = V$$

$$\sqrt{V_P + V_C} = 0$$

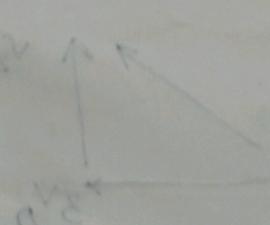

$$(N + S) + (V_P + V_C) = OPE$$

(91)