

**EE 1100 Basic Electrical Engineering**  
**Mar-June 2023**

**Tutorial-4**  
**Single Phase AC Circuits (a)**

- 1) For the circuit shown in Figure 1 below , find the expression for  $i(t)$  .

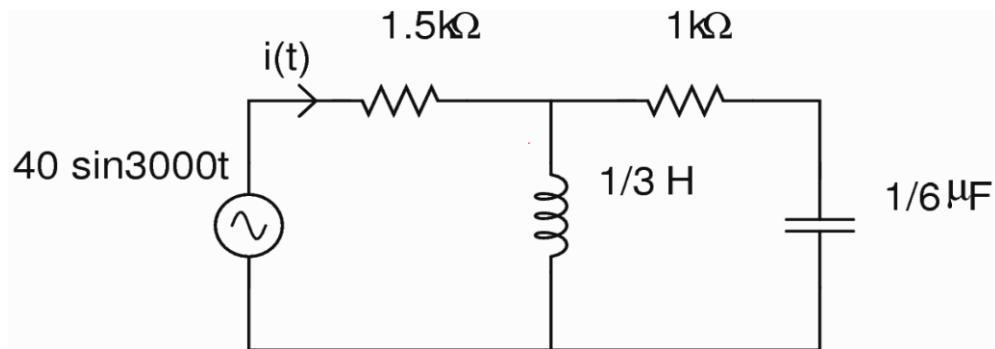


Figure:1

- 2) Find the steady state current  $i(t)$  in below figure 2.

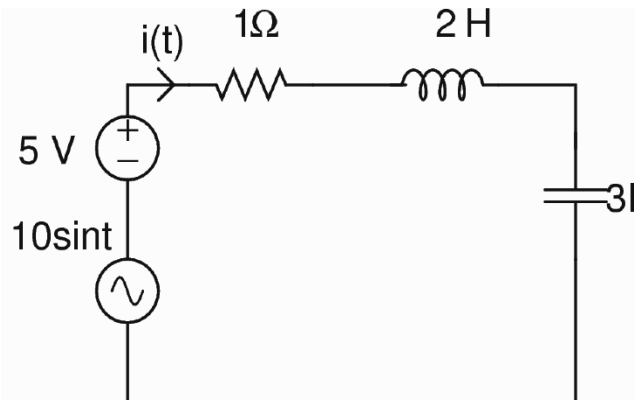


Figure:2

- 3) In the circuit shown below, the supply voltage is  $10 \sin(1000t)$  V. Find the peak value of the steady state current through the  $1 \Omega$  resistor

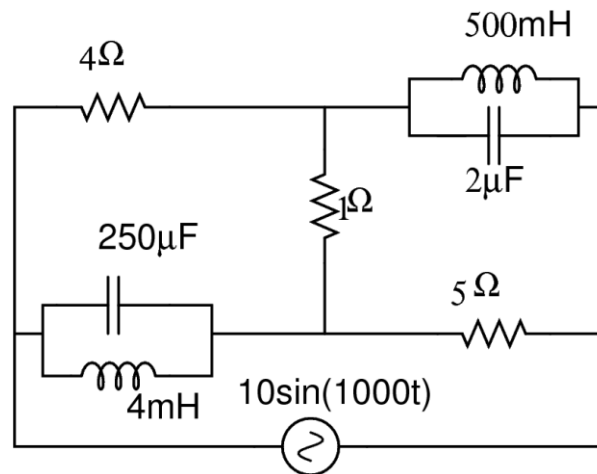


Figure:3

- 4) Find the branch currents  $I_a$ ,  $I_b$  and  $I_x$  as indicated in the circuit shown in figure 4, given that  $I_1 = 10.6 \sin(\omega t)$  A

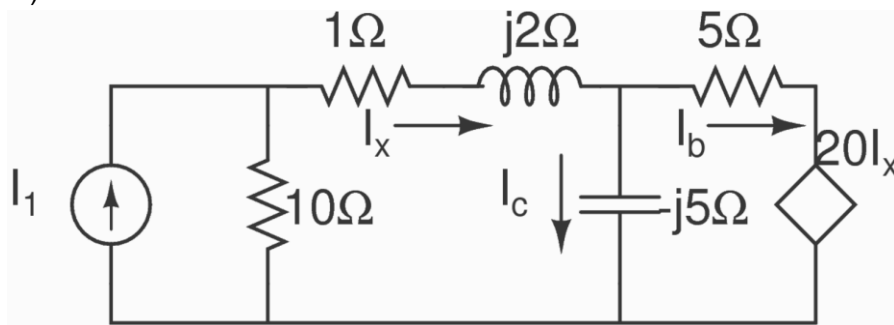


Figure:4

- 5) Find the steady state value of current  $i(t)$  in below circuit diagram

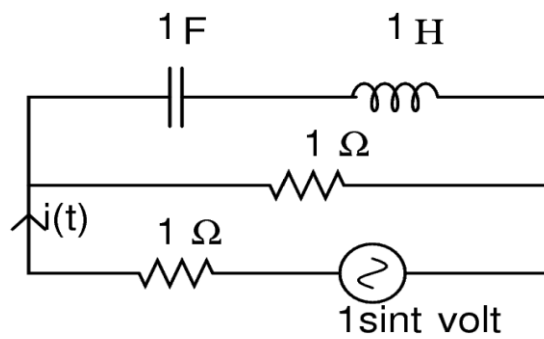


Figure:5