

EE 1100 Basic Electrical Engineering
March-June 2023
Tutorial-1

- 1) In the circuit shown below (Fig1), find v .

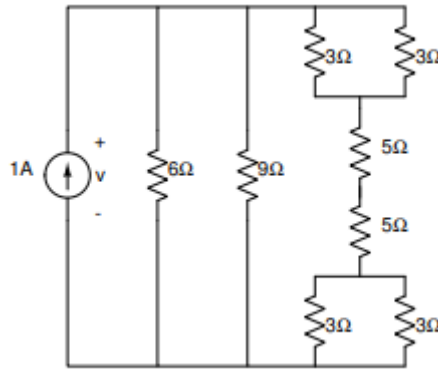


Fig1

- 2) A certain voltage is +10 V for 20 ms and -10 V for the succeeding 20 ms. It continues oscillating in this fashion. The voltage is present across a 50Ω resistor. Over any 40 ms interval find the average values of the voltage, current.
- 3) Find the value of R_A in the circuit below (Fig2).

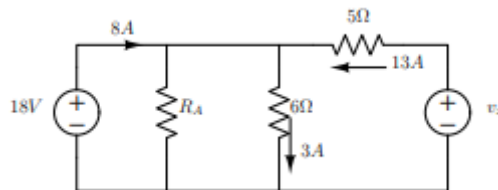


Fig2

- 4) Determine v_x in the circuit (Fig3)

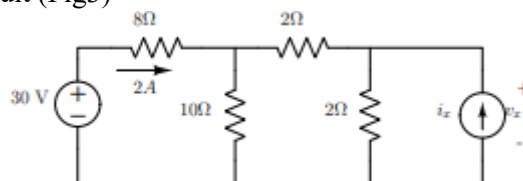


Fig3

- 5) In the following circuit (Fig4), calculate the power dissipated or generated in each element. State clearly whether it is dissipated or generated.

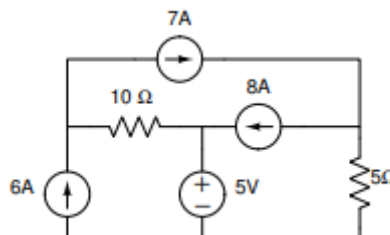


Fig4

- 6) For the given circuit (Fig5) determine the power absorbed by each resistor and the power supplied by each current source

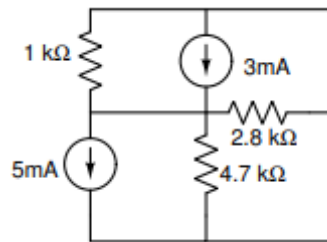


Fig5

- 7) For the following circuit (Fig6), find V_A by nodal analysis

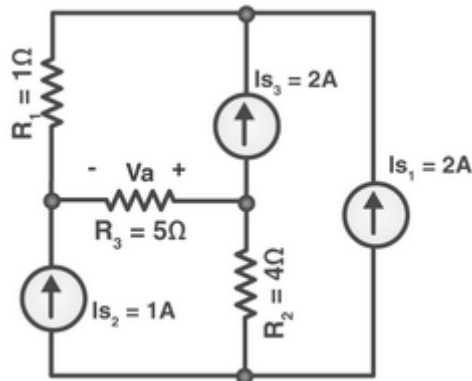


Fig6

- 8) Most homes use solid copper wire having a diameter of 1.63mm to provide electrical distribution to outlets and light sockets. Determine the resistance of 75 meters of solid copper wire having the above diameter.
- 9) A digital voltmeter having an internal resistance of $5\text{M}\Omega$ is used to measure the voltage across terminals a and b in the circuit shown in Fig7. Determine the reading on the meter.

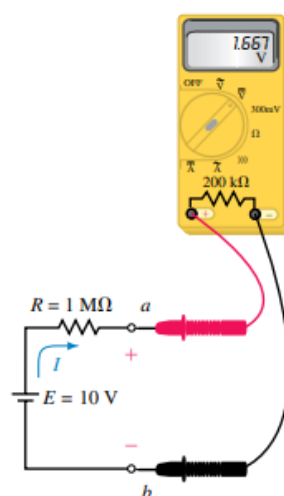


Fig7