
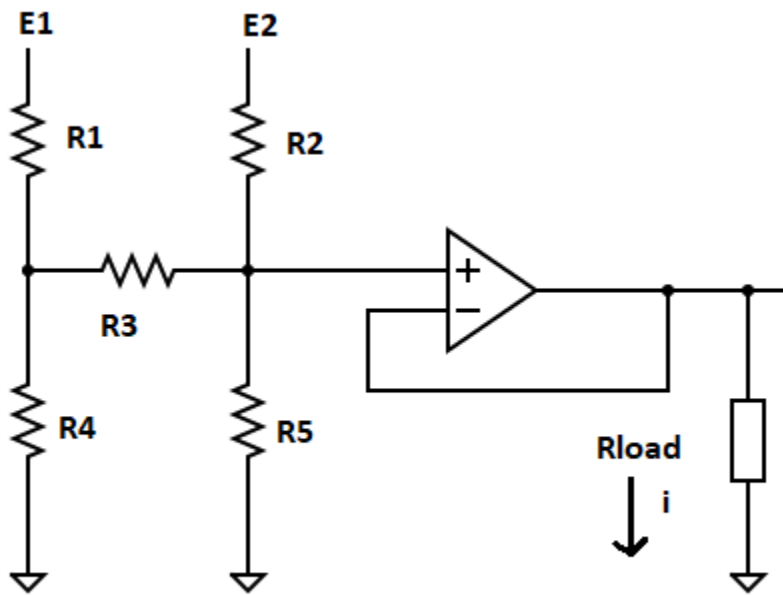


**EE 1100 Basic Electrical Engineering**  
**March – June 2023**  
**Tutorial 8 Opamp Circuits**

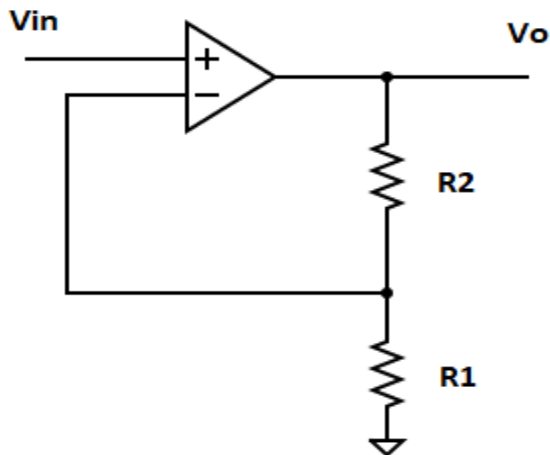
1) Find the expression for current  $i$  through load resistance  $R_{load}$ . Assume opamp is operating in linear region




2) Find the output voltage  $V_o$ . Take  $V_{in} = 5\text{ V}$ ,  $R_1 = 4\text{ ohms}$  and  $R_2 = 8\text{ ohms}$ .



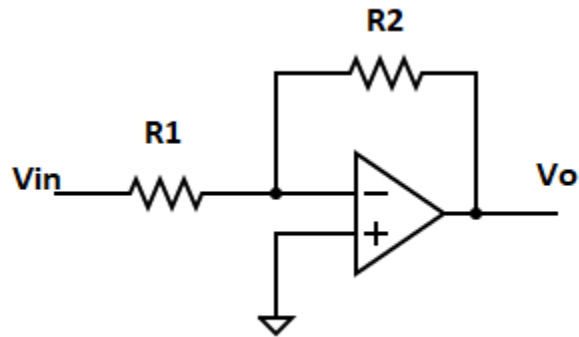
3) Find the output voltage  $V_o$ . Take  $V_{in} = 3\text{ V}$ ,  $R_1 = 5\text{ ohms}$  and  $R_2 = 7\text{ ohms}$ .



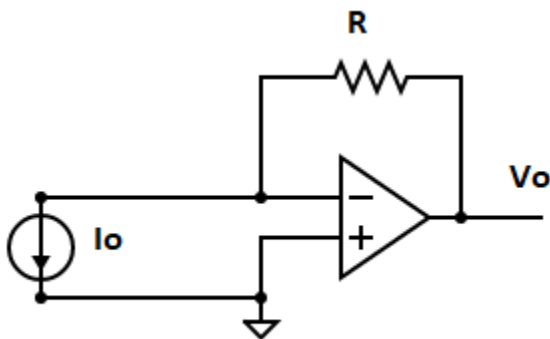
4) What will be the voltage  $V_o$  at the output of the op amp? Take  $I_o = 2\text{ A}$  and  $R = 5\text{ ohms}$ .



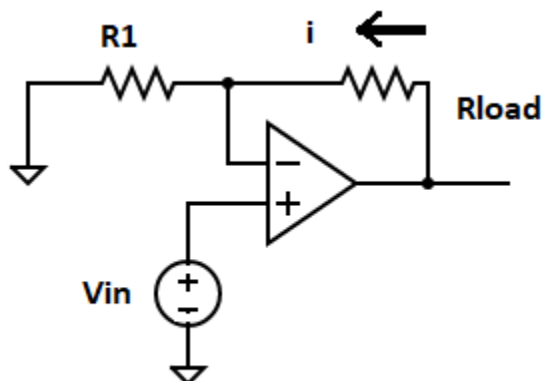
5) What will be the current  $i$  through the load resistance  $R_{load}$ ? Take  $V_{in} = 6\text{ V}$  and  $R_1 = 2\text{ ohms}$ .



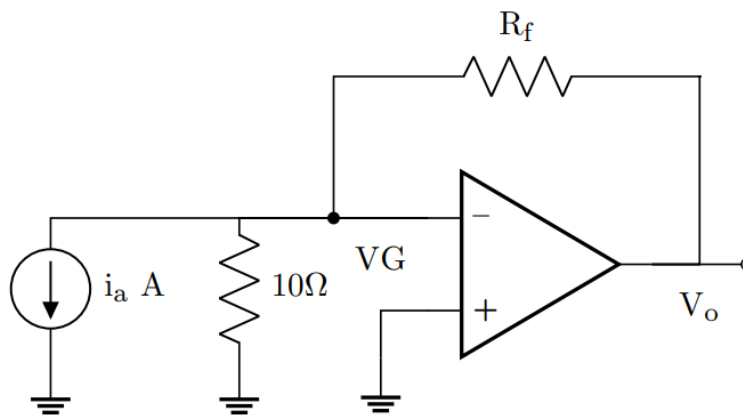6. A third year EE student at IITM wanted to measure the torque of a DC motor. He knew that for that particular motor, the relationship between the torque and the armature current is given by the relationship  $T_a = k_a \cdot i_a$  and  $i_a$  are the torque constant and armature current of the motor respectively.  $k_a = 5 \text{ Nm/A}$ . He knew that the circuit shown in the figure can be used and its output voltage is to be fed to a voltmeter. Instruct him on what the value of the feedback resistance  $R_f$  should be such that the voltmeter shows the magnitude of the torque.



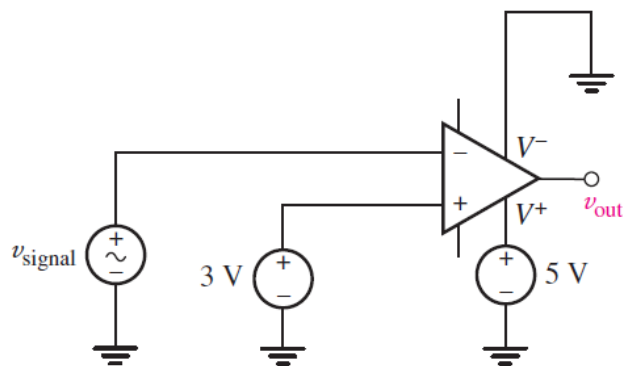7. Consider the input signal to the following circuit is a sine-wave,  $V_{in}(t) = 4 \sin(100t) \text{ V}$ . Plot the shape of the output.



8. Consider that a sine-wave signal is provided to the following circuit at  $V_{in}$ . Analyse and find out the expected shape of the output signal at  $V_{out}$ . Assume that the diodes have a finite forward voltage drop (say 0.7V), and infinite reverse bias resistance.

