
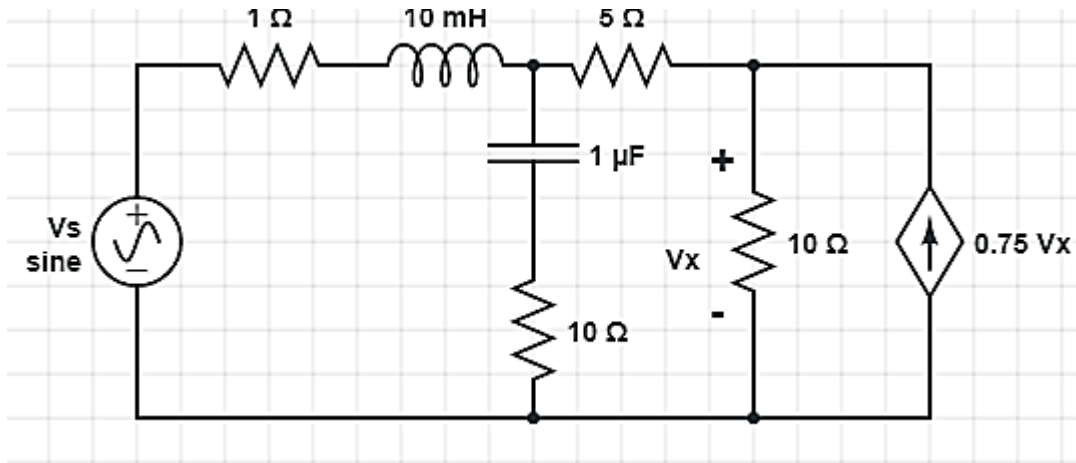


**EE 1100 Basic Electrical Engineering**  
**March – June 2023**  
**Tutorial 5**  
**Single Phase AC Circuits**

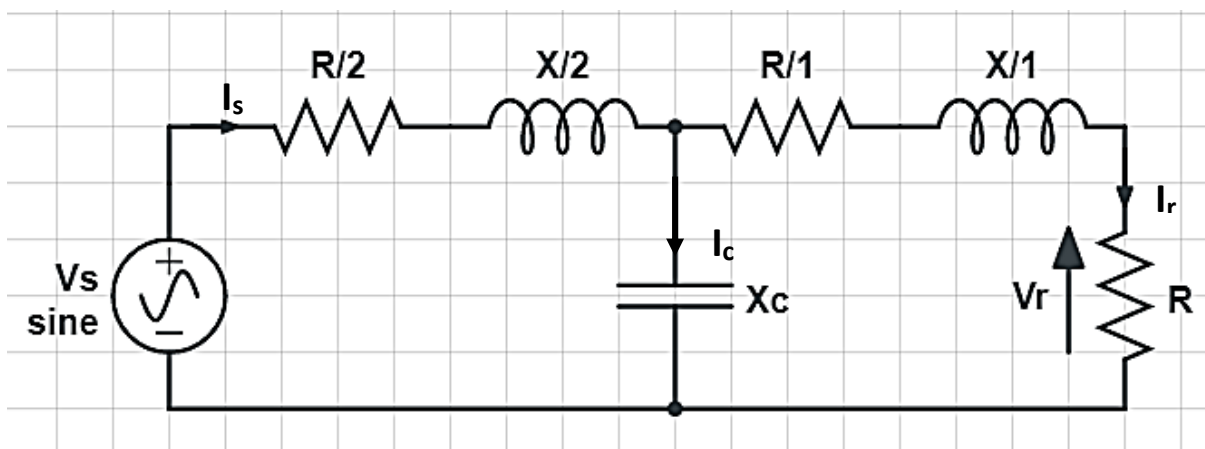1. Determine the current passing through the  $1\ \Omega$  resistor using nodal analysis. Where the supply voltage  $V_s = 110 + j0\text{ V}$ .




2. Draw the phasor diagram keeping  $V_r$  as reference, for the circuit shown below.



3. An iron core inductive coil of resistance and inductance of  $10\ \Omega$  and  $100\text{ mH}$  is connected to  $100\text{ V}$ ,  $60\text{ Hz}$ , 1-phase AC supply.
  - a. Determine the total impedance, current passing through the inductor, power factor, and active power consumed by it.
  - b. If the inductive coil is changed to air core whose inductance of the coil is  $10\text{ mH}$  and power consumed by it is  $250\text{ W}$ . determine its resistance, power factor and current passing through it.
  - c. An iron inductive coil has a resistance  $5\ \Omega$  and the power factor of the coil  $0.8\text{ lag}$ . Determine the current, power and inductance of the coil.

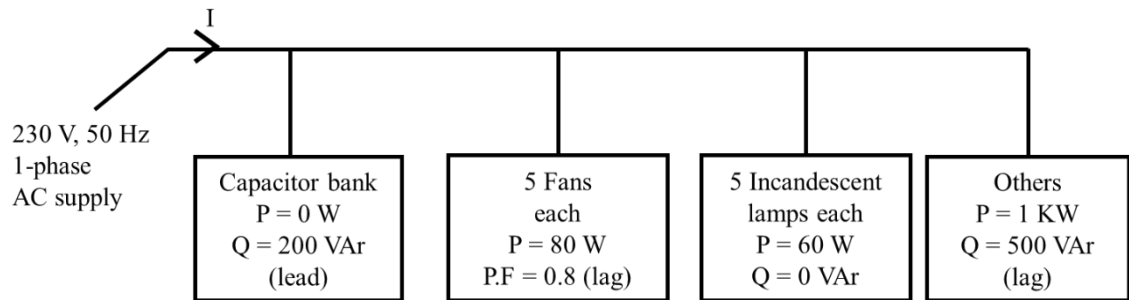4. The following fig.1 shows the electrical appliances used in a house. Determine
- Total active power, reactive power and apparent power
  - Current drawn (I) from the power supply
  - Power factor, and draw the power triangle.



5. Find the value of value of the capacitance needed to correct the load pf to unity in the above given question.